


School of Basic Sciences
Master of Science in Physics
Mid Term Examination - May 2024

Duration : 90 Minutes
Max Marks : 50

Sem II - C1PO204T - Digital Electronics

General Instructions
Answer to the specific question asked
Draw neat, labelled diagrams wherever necessary
Approved data hand books are allowed subject to verification by the Invigilator

 - 1) Represent K2 (2)
 i) $+(7)_{10}$ & $-(7)_{10}$
 ii) $-(8)_{10}$ in 2's complement form
- 2) Design the Ex-OR gate using NAND gates. K1 (3)
- 3) Simply the following Boolean functions using K –Map $F(A, B, C, D)=\sum m(0,1,3,4,5,7,12,13,15)$ K2 (4)
- 4) Simply the following Boolean functions using K –Map $F (X,Y,Z,W) = \Sigma (0, 1, 2, 4, 5, 6, 8 , 9 , 12, 13, 14)$ K2 (6)
- 5) Write the name of logic gate of given circuit shown, diodes $D_1, D_2,$ and D_3 are ideal, and the inputs E_1, E_2 and E_3 K3 (6)



- 6) Simply the following Boolean functions using K –Map $F(A,B,C,D) = \Sigma (0,2,4,6,9,11,13)$ K3 (9)

- 7) Write the truth table of full adder and draw the full adder diagram using NAND gates? K4 (8)
- 8) Explain with logic diagram of 4-bit serial-in, serial-out, shift register K4 (12)

OR

Explain with logic diagram of 4-bit parallel-in, parallel-out, shift register K4 (12)