

## School of Basic Sciences

**Master of Science in Physics  
Semester End Examination - Jun 2024**

**Duration : 180 Minutes  
Max Marks : 100**

### Sem II - C1PO204T - Digital Electronics


General Instructions

*Answer to the specific question asked*

*Draw neat, labelled diagrams wherever necessary*

*Approved data hand books are allowed subject to verification by the Invigilator*

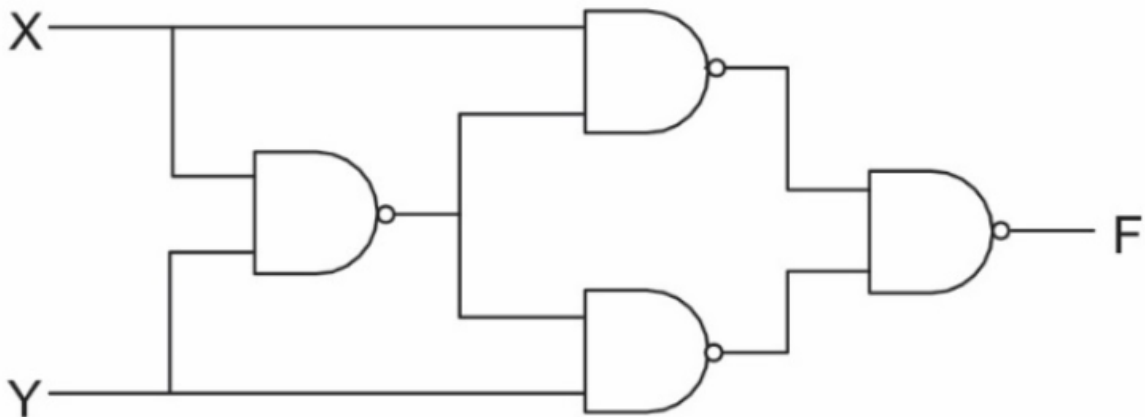- 1) Write K-map for NAND gate and solve to get the Boolean expression of NAND gate K1(3)
- 2) Obtain the excitation table of D flip flop K2(4)
- 3) Explain the 4-bit subtractor with digital circuit diagram. K2(6)
- 4) The Boolean function  $F(X,Y)$  realized by the given circuit is K3(6)



- 5) Discuss the comparator circuit using XOR logic gate K3(6)
- 6) What do you mean by universal gate? Draw the AND gate using transistors and write the truth table. K3(9)
- 7) Explain the quantization and encoding process in A/D converter K3(9)
- 8) What is liquid crystal and what are its the unique properties? K4(8)
- 9) Describe a 8 to 3 binary encoder using truth table and draw its digital circuit K4(12)
- 10) Describe a sample and hold circuit in D/A converter K5(10)

11) Explain the features of 8085 in detail. K5(15)

**OR**

Describe dual slope A/D converter with suitable circuit diagram. K5(15)

12) Design SR flip-flop using JK flip-flop. K6(12)

**OR**

Discuss the working, truth table and Boolean equation using K-map of T- flip flop and D flip flop. K6(12)