

School of Computing Science and Engineering

**Bachelor of Technology in Computer Science and Engineering
Semester End Examination - Jun 2024**

**Duration : 180 Minutes
Max Marks : 100**

Sem II - G2UA120B - Basic Electrical and Electronics Engg.


General Instructions

Answer to the specific question asked


Draw neat, labelled diagrams wherever necessary

Approved data hand books are allowed subject to verification by the Invigilator

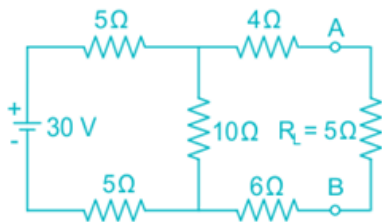
- 1) Tell the biasing of P-N junction diode. K1(2)
- 2) Explain the differences between Thevenin's and Norton's theorem. K2(4)
- 3) Summarize the differences between half wave rectifier and full wave rectifier. K2(6)
- 4) Solve the problem with the help of Norton's theorem and find the current through the RL (5Ω) resistor. K3(9)



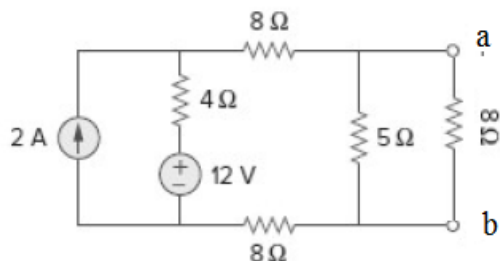- 5) Solve the problem with the help of Norton's theorem and find the current through the 8Ω resistor (terminal a and b). K3(9)



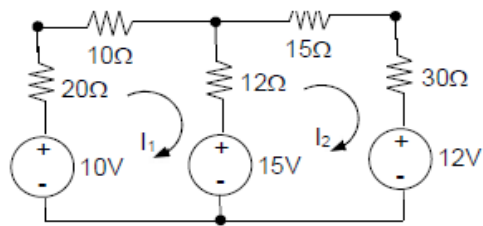- 6) Measure the value of current through 12Ω resistor using mesh current analysis for the given circuit. K5(10)



- 7) Analyze I_{dc} , I_{rms} , ripple factor and rectifier efficiency of a Half Wave rectifier circuit. K4(12)
- 8) Explain parallel RLC resonance network. A parallel resonance network consisting of a resistor of 60Ω , a capacitor of $120\mu F$ and an inductor of $200mH$ is connected across a sinusoidal supply voltage which has a constant output of 100 volts at all frequencies. Determine, the resonant frequency, the quality factor and the bandwidth of the circuit, the circuit current at resonance and current magnification. K5(15)
- 9) Explain Zener voltage regulation circuit. A voltage regulation circuit having a Zener diode with a breakdown voltage of $6V$. If the input voltage varies from $8V$ to $12V$, determine the series resistor value (R_s) required maintaining a constant output voltage of $6V$. Assume the Zener resistance (R_z) is 10 ohms at breakdown region. K5(15)
- 10) (a) Design a pure capacitive AC circuit and derive its current and voltage. (b) A series RLC Circuit connected to a $230V$ AC supply. If at resonance frequency, the current draw by the series circuit is $25A$ and voltage drop across $800\mu F$ capacitor is $40V$. Calculate the overall impedance, power factor and resonance frequency of the circuits. K6(18)