

**School of Biomedical Science**

**B.Tech Biotechnology  
Semester End Examination - Jun 2024**

**Duration : 180 Minutes  
Max Marks : 100**

**Sem II - G2UC101B - BEE01T1005 - Introduction to Digital System - 1**General Instructions

*Answer to the specific question asked*

*Draw neat, labelled diagrams wherever necessary*

*Approved data hand books are allowed subject to verification by the Invigilator*

- 1) Distinguish between Encoders and Decoders K1(2)
- 2) Obtain the 1's & 2's complement of the following binary numbers: (1010) & (10110010). K2(4)
- 3) Simplify the following Boolean expressions and design circuit using logic gates: (ii)  $Y = [(A + B)' \cdot (A + C)']'$ . K2(6)
- 4) Design a logic circuit that has three inputs, A,B and C, and whose output will be HIGH when a majority of the inputs are HIGH. K3(9)
- 5) Prove the following identities using Boolean laws: (i)  $A+A.B=A$  (ii)  $(A + B) \cdot (A + C) = A + B \cdot C$  K3(9)
- 6) Design a logic circuit having three inputs X,Y,Z such that output is 1 when  $X=0$  or whenever  $Y=Z=1$ . K5(10)
- 7) Reduce the expression  $\Sigma m(0,2,3,4,5,6)$  using mapping and implement it in NAND logic. K4(12)
- 8) Simplify the boolean function in sum of products using don't care condition.  $F=x'z' + y'$ ,  $d = yz + xy$ . K5(15)
- 9) Simplify using don't care condition  $F + A'(B'C + B'C' + BCD) + B'D'$  ( $C + A$ ) and  $d = A'B(C'D + CD') + ACD$ . K5(15)
- 10) Differentiate between Flip flop and latch. Discuss the positive triggering in the Flip-flops using suitable example. T flip flop can be designed by using JK flip-flop - Justify? K6(18)