

Introduction to DC Circuits

[1.1] **Electrical Network**


Combination of different electric elements or components which are connected in any way is called electric network.

[1.2] **Complex Networks**

A Circuit which contains on many electrical elements such as resistors, capacitors, inductors, current sources and Voltage source (both AC and DC) is called Complex network. These kinds of networks can't be solved easily by simple ohm's Law or Kirchhoff's laws. I.e. we solve these circuits by specific technique i.e. Norton's Theorem, Thevenin's Theorem, Superposition theorem etc.

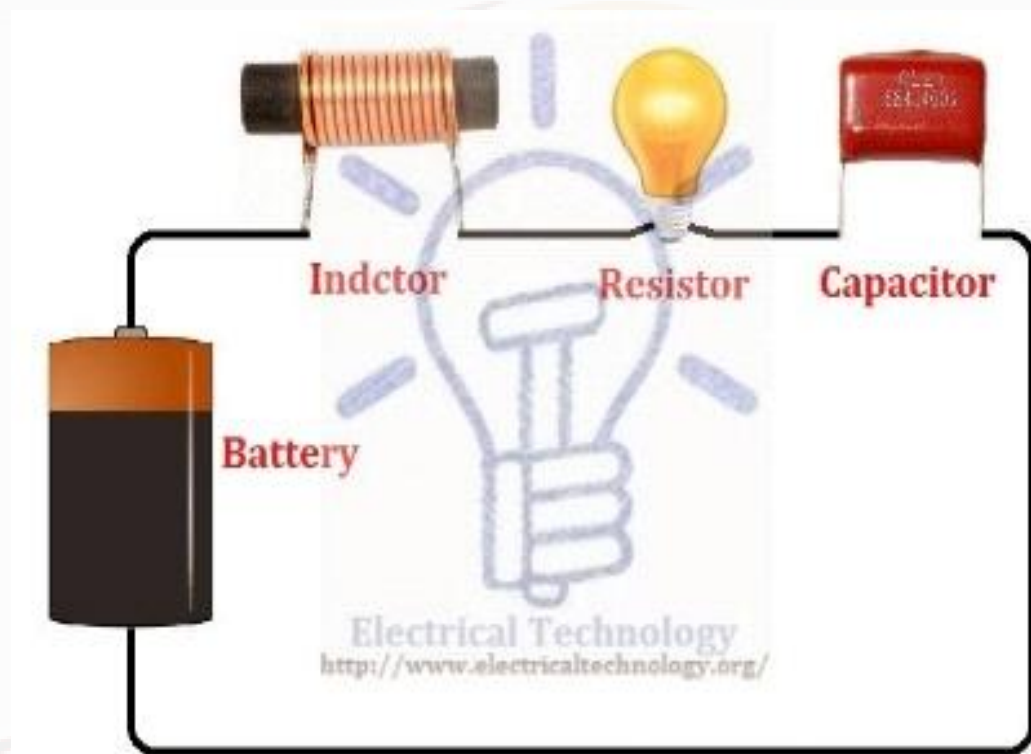[1.3] **Circuit or Electric Circuit**

Circuit is a close loop path giving a return path for the current. Or a close conducting path in which current can flow is called circuit



GALGOTIAS
UNIVERSITY


[1.4] Unilateral and Bilateral circuits

❖ Unilateral circuits


In unilateral circuits, the property of circuit changes with the change of direction of supply voltage or current. In other words, unilateral circuit allows the current to flow only in one direction. Diode rectifier is the best example of unilateral circuit because it does not perform the rectification in both direction of supply.

❖ Bi-lateral circuits

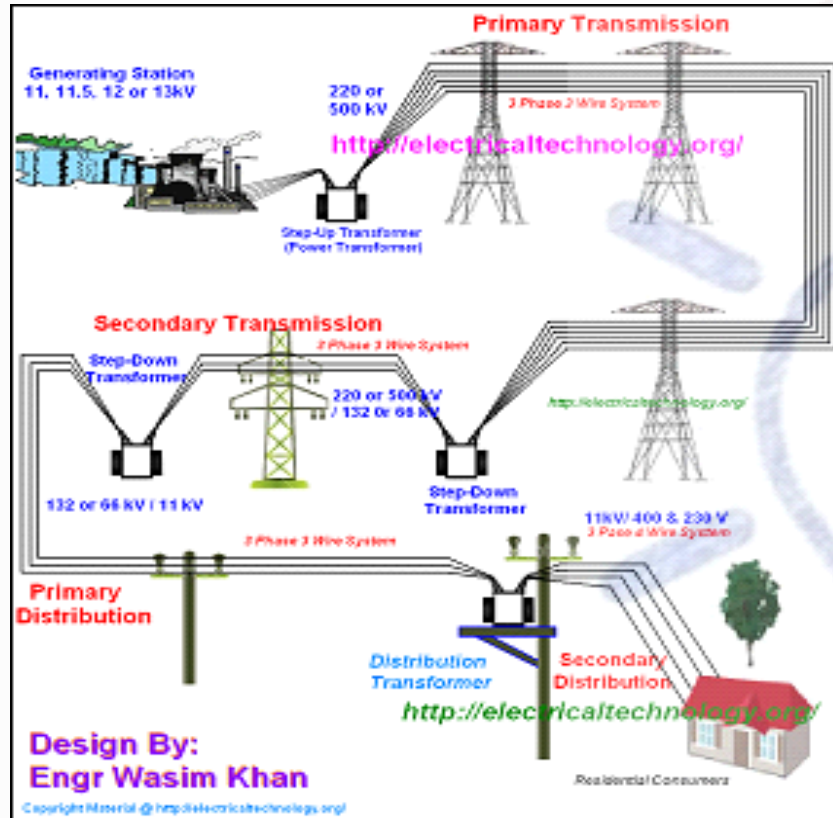In bilateral circuits, the property of circuit does not change with the change of direction of supply voltage or current. In other words, bilateral circuit allows the current to flow in both directions. Transmission line is the best example of bilateral circuit because, if you give supply from any direction, the circuit properties remain constant



Bi-lateral circuits
(Transmission line)

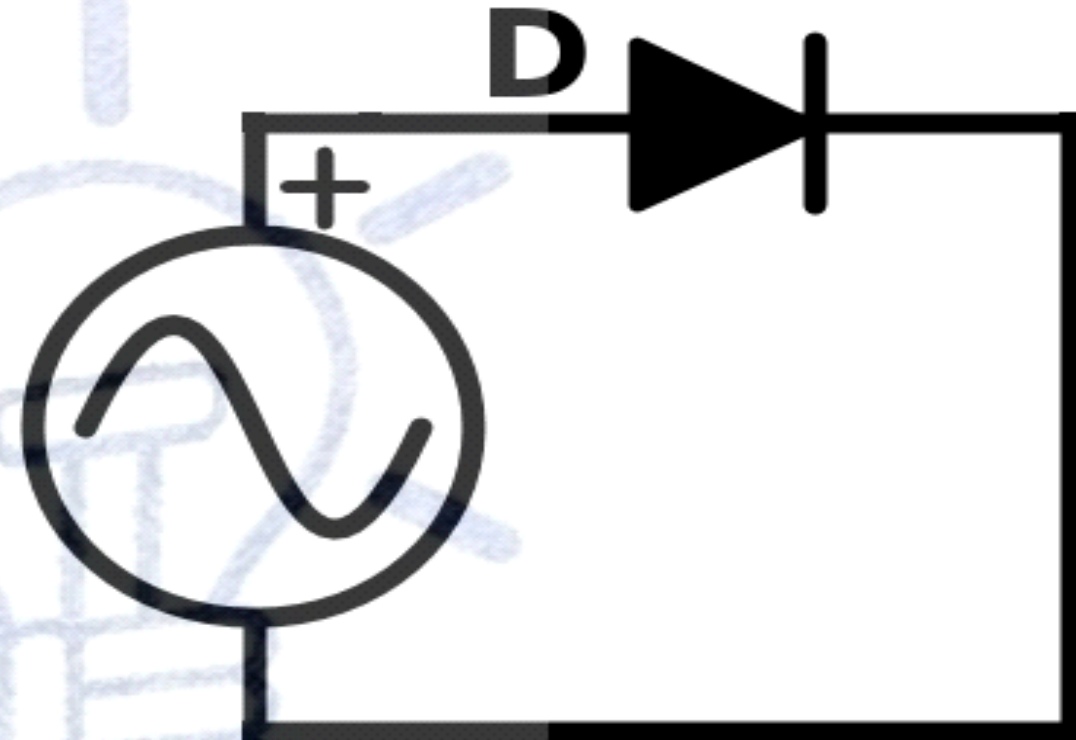

Unilateral circuits
(Diode rectifier)

[1.5] Active and Passive Circuits:

❖ Active Circuit

A circuit which contains one or more E.M.F (Electro motive force) sources is called Active Circuit

❖ Passive Circuit

A circuit in which no EMF source exist is called Passive Circuit

The Main Difference between Active and Passive Components

❖ Active Components:

Those devices or components which required external source for their operation is called Active Components.


For Example: Diode, Transistors, SCR etc...

School of Electrical , Electronics & Communication Engineering

Course Code : BEEL101

Course Name: AC & DC Circuits

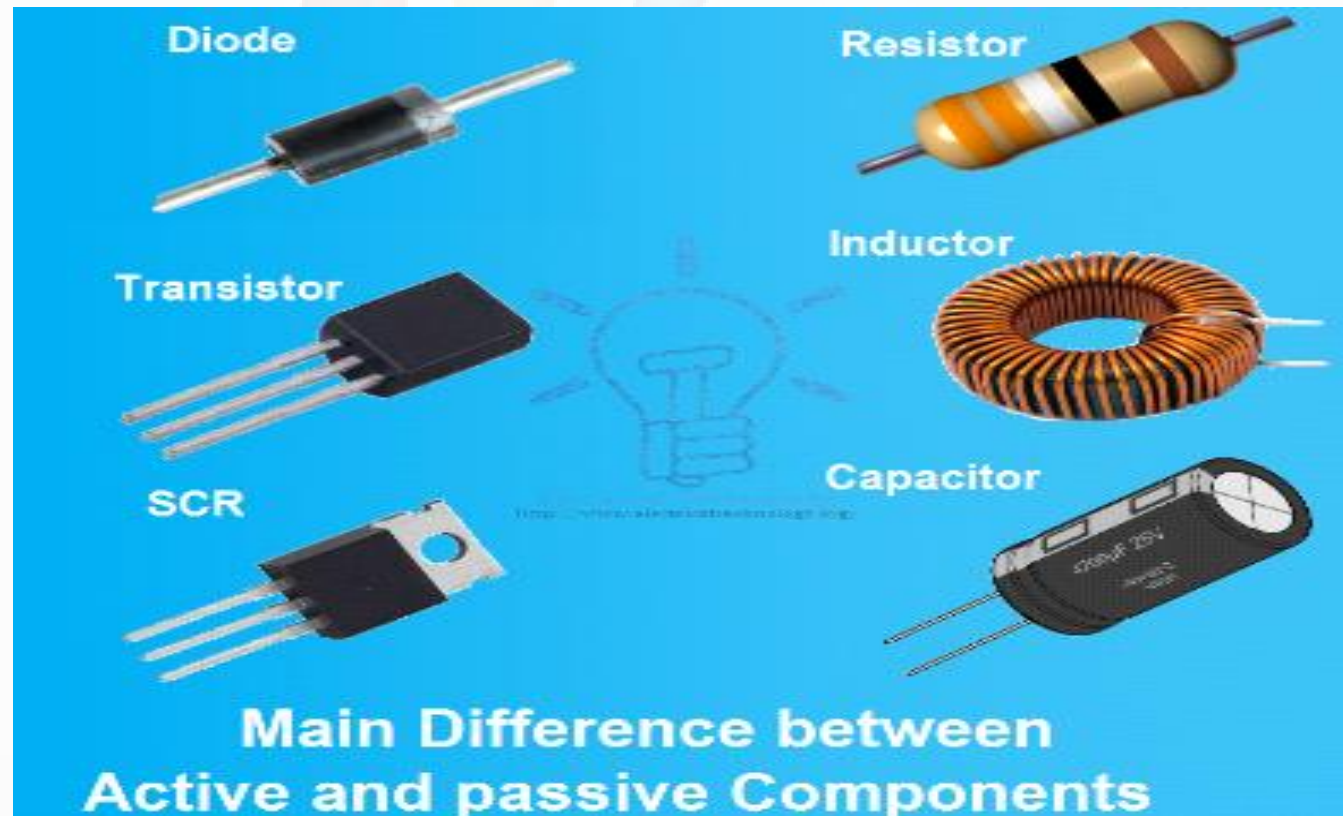Explanation: Diode is an Active Components as it requires an External Source to its operation. If we connect a Diode in a Circuit and then connect this circuit to the Supply voltage., then Diode will not conduct the current until the supply voltage reaches to 0.3V (in case of Germanium) or 0.7V (in case of Silicon).



VIDEO- COMPONENTS

<https://www.youtube.com/watch?v=iHmSj6v7LOE>

GALGOTIAS
UNIVERSITY

❖ **Passive Components:**

Those devices or components which do not required external source to their operation is called Passive Components.

Example: Resistor, Capacitor, Inductor etc...

[1.6] **Other important related terms to Electric Circuits and Networks**

❖ **Node**

A point or junction where two or more circuit's elements (resistor, capacitor, inductor etc) meet is called Node

❖ **Branch**

That part or section of circuit which locate between two junctions is called branch. In branch, one or more elements can be connected and they have two terminals.

❖ Loop


A closed path in circuit where more than two meshes can be occurred is called loop i.e. there may be many meshes in a loop, but a mesh does not contain on one loop.

❖ Mesh

A closed loop which contains no other loop within it or a path which does not contain on other paths is called Mesh.

GALGOTIAS
UNIVERSITY

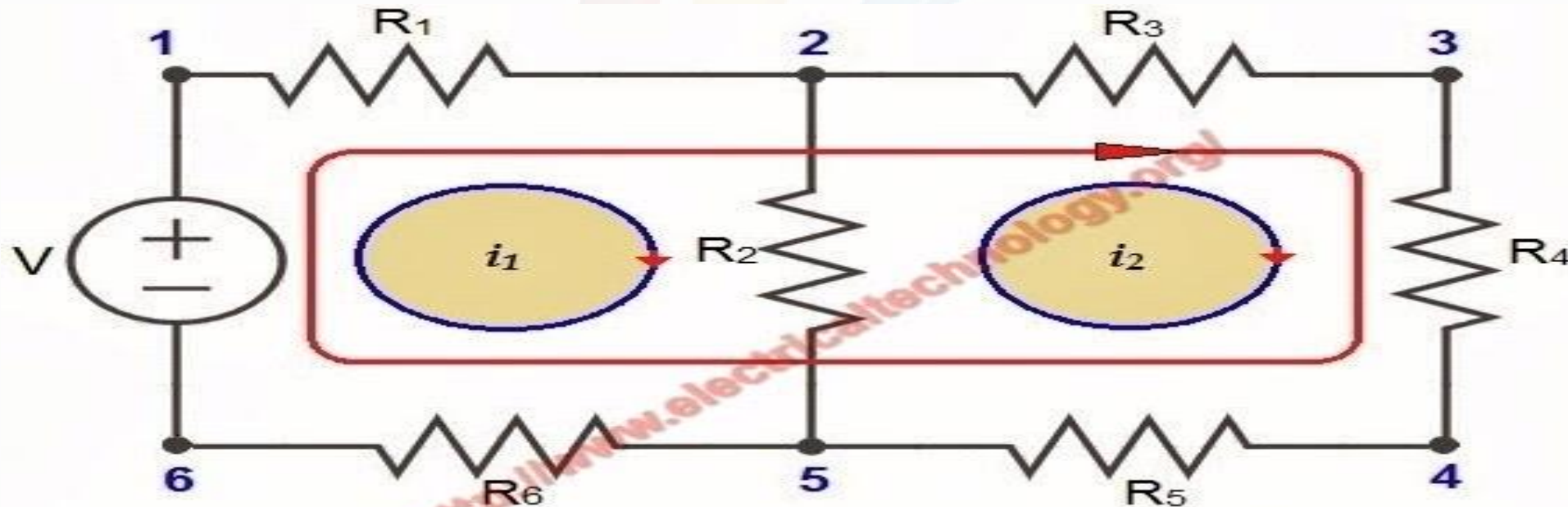- Determine the number of Nodes, Branches, Loops and Meshes in a Circuit:



**How to determine the number of Nodes,
Branches, Loops and Meshes in a Circuit**
6 Nodes, 7 Branches, 3 Loops, & 2 Meshes,