

IC555 as Astable multivibrator


Contents:

1. Introduction
2. Circuit diagram
3. Working and applications

GALGOTIAS
UNIVERSITY


Introduction

One popular application of the 555 timer IC is as an astable multivibrator or clock circuit. An astable multivibrator, often called a free-running multivibrator, is a rectangular-wave generating circuit. Unlike the monostable multivibrator, this circuit does not require any external trigger to change the state of the output, hence the name free-running. An astable multivibrator can be produced by adding resistors and a capacitor to the basic timer IC, as illustrated in figure. The timing during which the output is either high or low is determined by the externally connected two resistors and a capacitor. The details of the astable multivibrator circuit are given in figure .

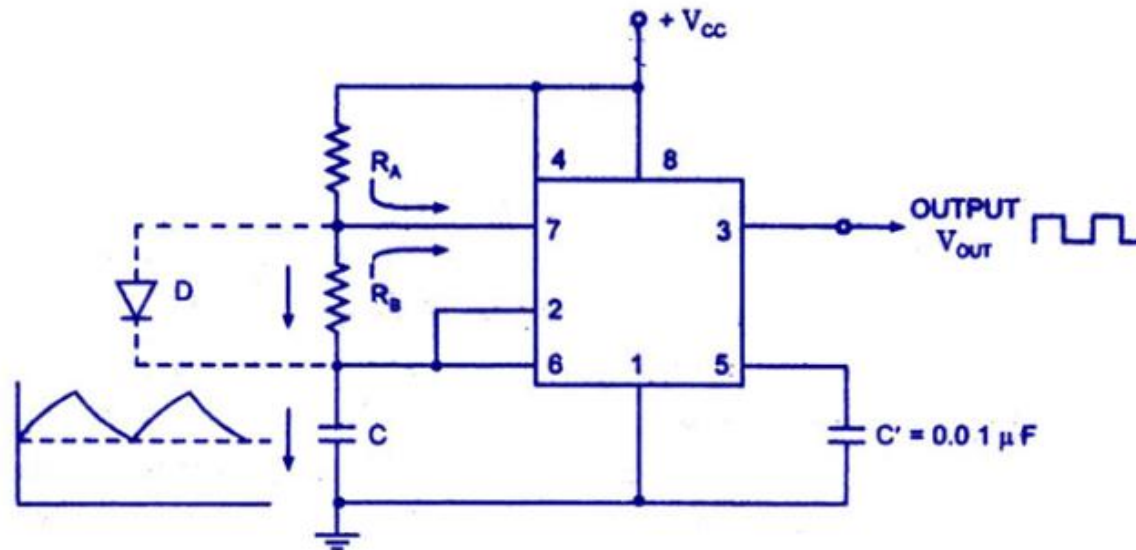


Circuit of The Timer 555 as an Astable Multivibrator

Introduction

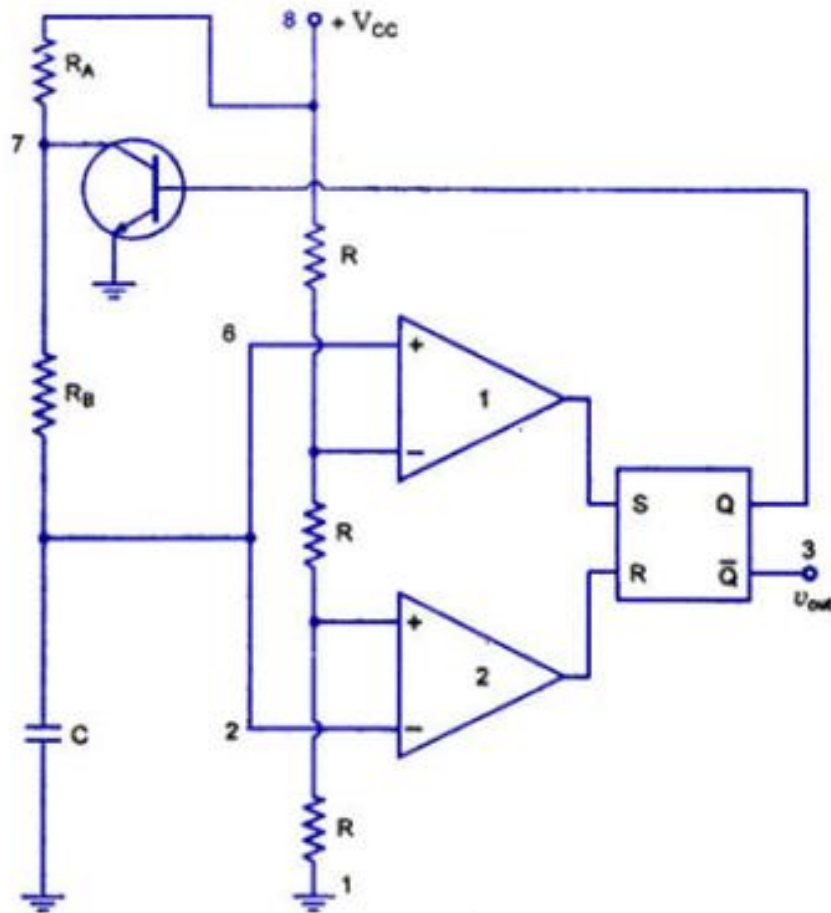


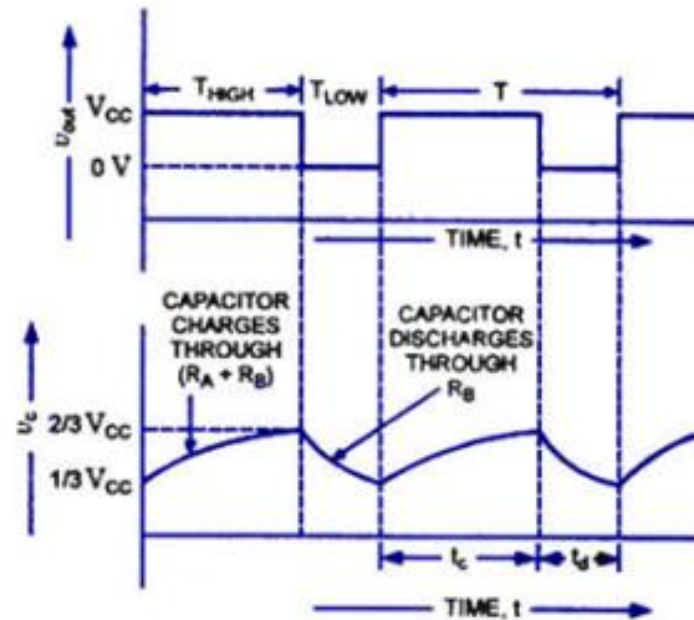Internal Circuitry With External Connections



Capacitor and Output Voltage Waveforms

Astable Operation

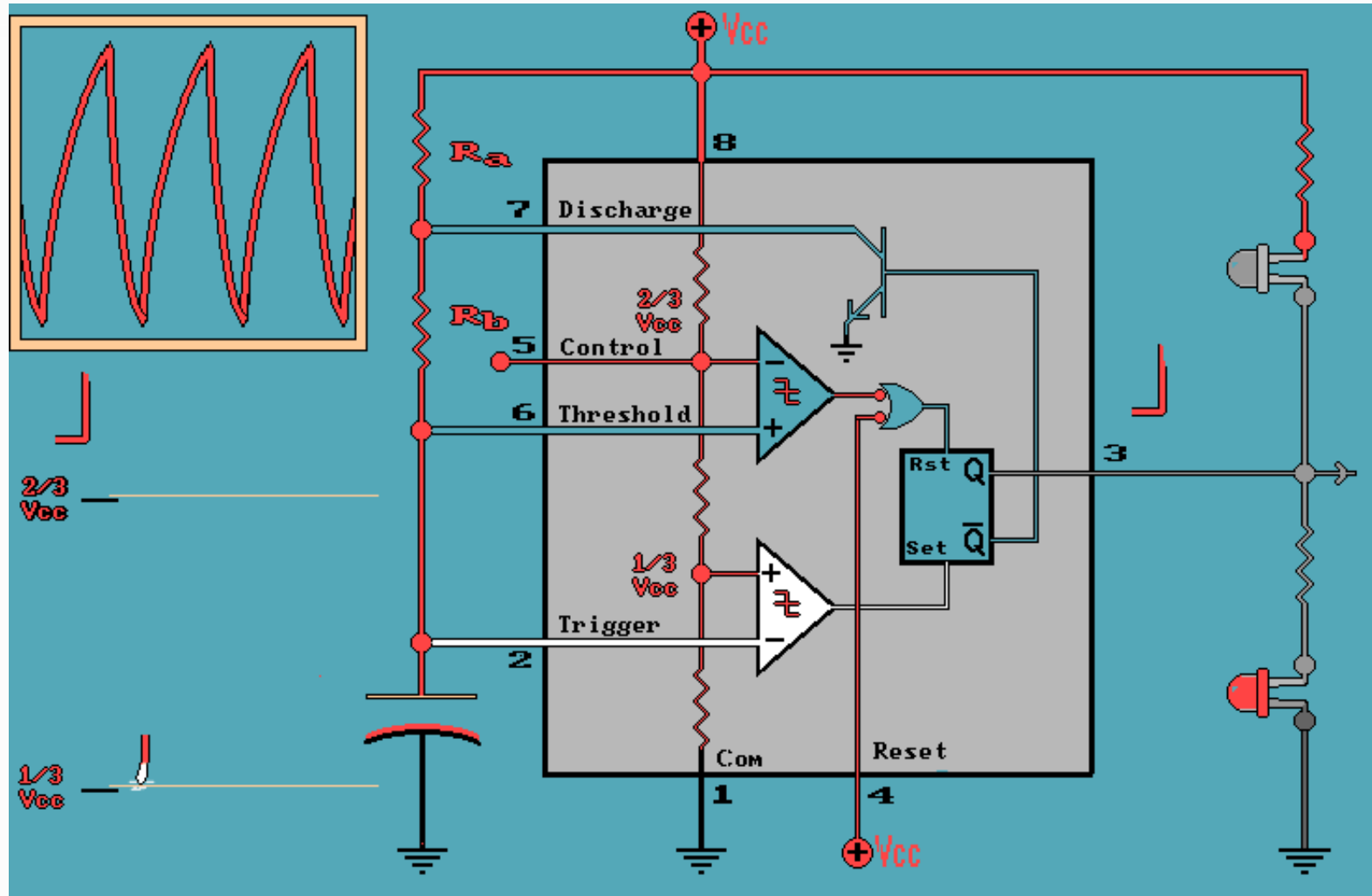


Working:

In the circuit, when Q is low, the discharging transistor is cut-off and the capacitor C begins charging toward V_{CC} through resistances R_A and R_B . Because of this, the charging time constant is $(R_A + R_B) C$.

Eventually, the threshold voltage exceeds $+2/3 V_{CC}$, the comparator 1 has a high output and triggers the flip-flop so that its Q is high and the timer output is low. With Q high, the discharge transistor saturates and pin 7 grounds so that the capacitor C discharges through resistance R_B with a discharging time constant $R_B C$.

With the discharging of capacitor, trigger voltage at inverting input of comparator 2 decreases. When it drops below $1/3 V_{CC}$, the output of comparator 2 goes high and this reset the flip-flop so that Q is low and the timer output is high. This proves the auto-transition in output from low to high and then to low as, illustrated in figures. Thus the cycle repeats. The time during which the capacitor C charges from $1/3 V_{CC}$ to $2/3 V_{CC}$ is equal to the time the output is high and is given as:
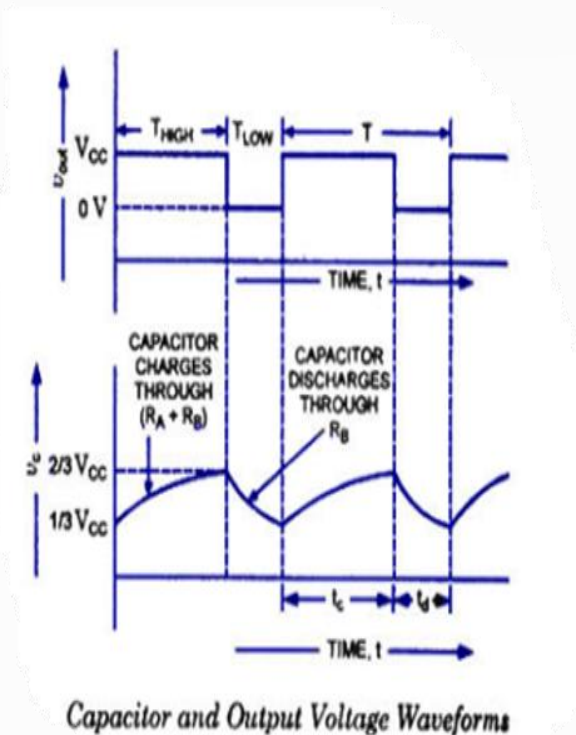
$$t_c \text{ or } T_{HIGH} = 0.693 (R_A + R_B) C.$$


Capacitor and Output Voltage Waveforms

Working:

Voltage across the capacitor at any instant during charging period is given as,

$$V_C = V_{CC}(1 - \exp^{-t/RC})$$

The time taken by the capacitor to charge from 0 to $+1/3 V_{CC}$:

$$1/3 V_{CC} = V_{CC} (1 - \exp^{-t_1/RC})$$

$$t_1 = RC \log_e 1.5 = 0.405 RC$$

Similarly, the time taken by the capacitor to charge from 0 to $+2/3 V_{CC}$ is given by:

$$t_2 = RC \log_e 3 = 1.0986 RC$$

So the time taken by the capacitor to charge from $+1/3 V_{CC}$ to $+2/3 V_{CC}$:

$$t_c = (t_2 - t_1) = (1.0986 - 0.405) RC = 0.693 RC$$

Substituting $R = (R_A + R_B)$ in above equation we have,

$$T_{HIGH} = t_c = 0.693 (R_A + R_B) C$$

where R_A and R_B are in ohms and C is in farads. The time during which the capacitor discharges from $+2/3 V_{CC}$ to $+1/3 V_{CC}$ is equal to the time the output is low and is given as:

$$t_d \text{ or } T_{LOW} = 0.693 R_B C \text{ where } R_B \text{ is in ohms and } C \text{ is in farads.}$$

Working:

The above equation is worked out as follows: Voltage across the capacitor at any instant during discharging period is given as: $V_C = (2/3)V_{CC} \exp^{-t/R_B C}$

Substituting $V_C = 1/3 V_{CC}$ and $t = t_d$ in above equation we have $+1/3 V_{CC} = +2/3 V_{CC} \exp^{-t_d/R_B C}$

$$\text{Or } t_d = 0.693 R_B C$$

Overall period of oscillations,

$$T = T_{HIGH} + T_{LOW} = 0.693 (R_A + 2R_B) C$$

The frequency of oscillations being the reciprocal of the overall period of oscillations T is given as:

$$f = 1/T = 1.44 / (R_A + 2R_B) C$$

Equation indicates that the frequency of oscillation f is independent of the collector supply voltage $+V_{CC}$.

Often the term duty cycle is used in conjunction with the astable multivibrator.



References:

- Digital Principles and Applications, A.P. Malvino, D. P. Leach and Saha, 7th Ed., 2011, Tata McGraw Hill
- Digital Fundamentals, Thomas L. Floyd, 11th Ed., 2015, Pearson Education Limited
- Modern Digital Electronics, R P Jain, 4th Ed., 2010, Tata McGraw Hill

GALGOTIAS
UNIVERSITY