Course Code: BTEE2002 Course Name: Network Analysis and Synthesis

UNIT 1 Graph Theory


GALGOTIAS UNIVERSITY

Course Code: BTEE2002 Course Name: Network Analysis and Synthesis

Contents

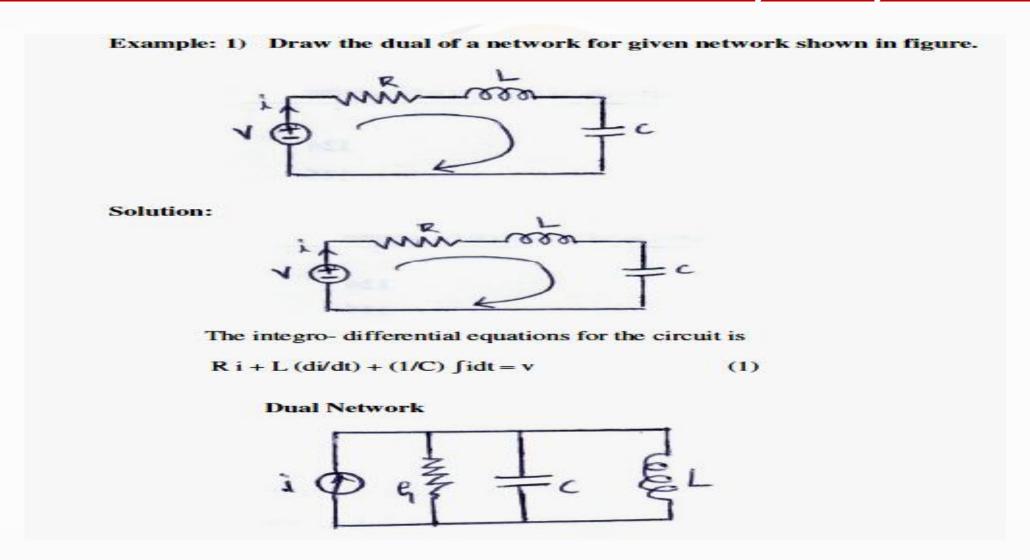- 1. Graph of a Network definitions
- 2. Tree and co tree
- 3. Link, basic loop
- 4. Basic cut set
- 5. Incidence matrix
- 6. Cut set matrix
- 7. Tie set matrix
- 8. Duality
- 9. Loop and Nodal methods of analysis.


Course Code: BTEE2002 Course Name: Network Analysis and Synthesis



Course Code: BTEE2002 Course Name: Network Analysis and Synthesis

The integro- differential equations for the circuit is

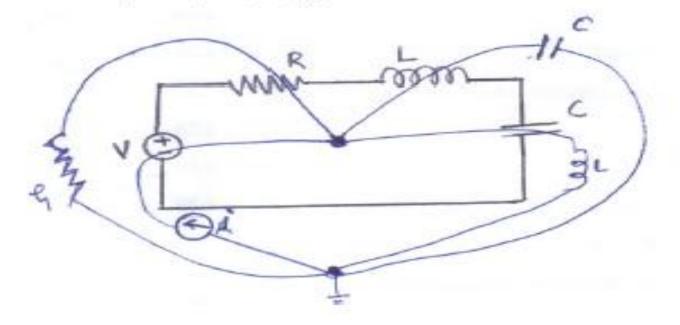
$$(1/R) v + C (dv/dt) + (1/L) \int v dt = i$$
 (2)
 OR
 $G v + C (dv/dt) + (1/L) \int v dt = i$




Course Code: BTEE2002 Course Name: Networ

Course Name: Network Analysis and Synthesis

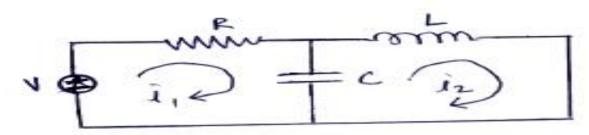Example: 2) Draw the dual of the network shown in figure.



Solution:

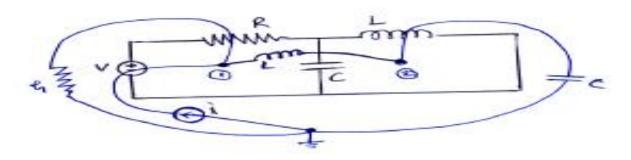


The integro- differential equations for the network is

$$R i_1 + (1/C) \int (i_1-i_2) dt = v(t)$$

$$L(di_2/dt) + (1/C) \int (i_2-i_1) dt = 0$$

Course Code: BTEE2002

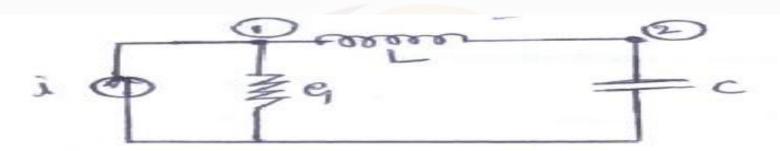Course Name: Network Analysis and Synthesis



The integro- differential equations for the network is


$$G v_1 + (1/L) \int (v_1 - v_2) dt = i$$

(1)

$$C (dv_2/dt) + (1/L) \int (v_2-v_1) dt = 0$$

(2)

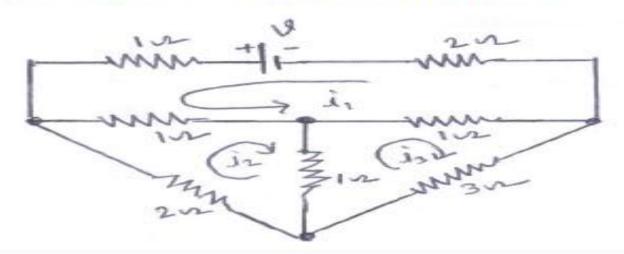Example: 3) Draw the dual of the network shown in figure.



Course Code: BTEE2002

Course Name: Network Analysis and Synthesis



Basic loop matrix (B-matrix)

The B-matrix describes the way the basic loop is chosen.

Each column corresponds to a branch (*b* columns).

Each row corresponds to a basic loop (b-t rows).


Construction

For each row:

Put a "+1" in the entry corresponding to the loop co-tree branch.

Put a "0" in the entry corresponding to other co-tree branches.

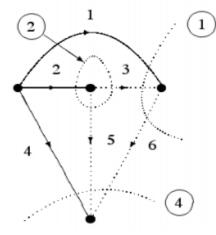Put a "+1" or "-1" in the entry corresponding to each loop tree branch; "+" if it is consistent with the co-tree branch direction and "-" otherwise.



$$B = \begin{bmatrix} 1 & 2 & 4 & 3 & 5 & 6 \\ -1 & 1 & 0 & 1 & 0 & 0 \\ 5 & 0 & 1 & -1 & 0 & 1 & 0 \\ 1 & 0 & -1 & 0 & 0 & 1 \end{bmatrix}$$

$$B = [B_1 \mid \mathbf{1}]$$

Course Code: BTEE2002 Course Name: Network Analysis and Synthesis



The basic cutset and loop matrices will be used to formulate independent Kirchhoff's law equations. This will give much more efficient solution to circuit analysis problems.

Mesh —enhanced— General loop analysis

Nodal —enhanced— General cutset analysis

Course Code: BTEE2002 Course Name: Network Analysis and Synthesis

References

- 1. M. E. Van Valkenburg, "Network Analysis", Prentice Hall, 2006.
- 2. D. Roy Choudhury, "Networks and Systems", New Age International Publications, 1998.
- 3. W. H. Hayt and J. E. Kemmerly, "Engineering Circuit Analysis", McGraw Hill Education, 2013.
- 4. C. K. Alexander and M. N. O. Sadiku, "Electric Circuits", McGraw Hill Education, 2004.
- 5. K. V. V. Murthy and M. S. Kamath, "Basic Circuit Analysis", Jaico Publishers, 1999. Syllabus
- 6. K.M. Soni, "Network Theory", S.K. Kataria Publication