

# **UNIT 4**

## **Two Port Networks**


**GALGOTIAS**  
**UNIVERSITY**

## Contents

1. Introduction to two port networks
2. Z –Parameters
3. Y- Parameters
4. ABCD – Parameters
5. Inverse ABCD – Parameters
6. h-Parameters
7. Inverse h-Parameters
8. Condition for reciprocity
9. Condition for symmetry
10. Inter-relationships between the parameters
11. Inter-connections of two port networks

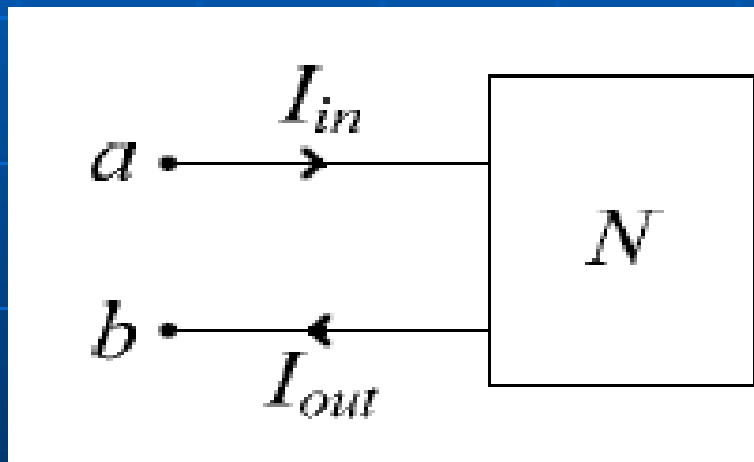
## 1. Introduction to two port networks

Consider a linear two-terminal circuit  $N$  consisting of no independent sources as follows :




For  $a, b$  two terminals, if  $I_{in} = I_{out}$ , then it constitutes a port.

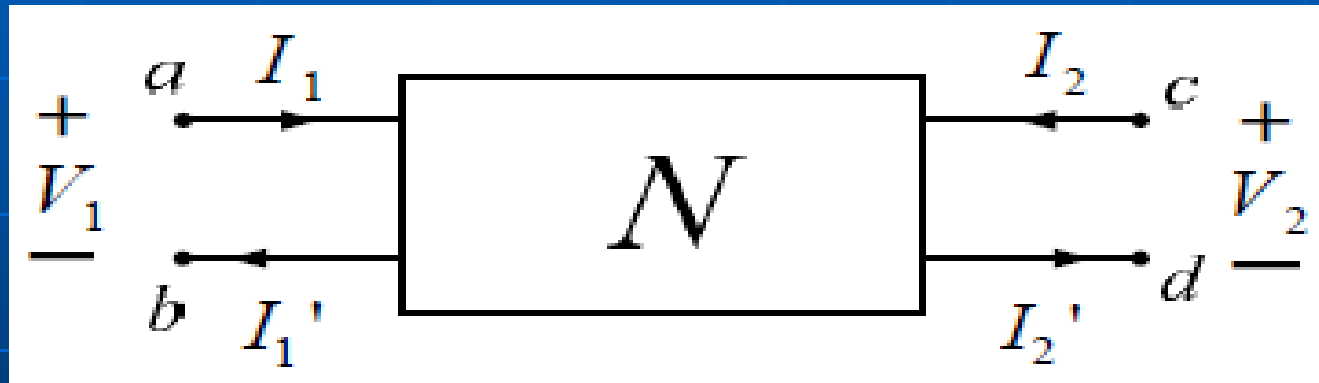Now consider the following linear four-terminal circuit containing no independent sources.



with  $I_1 = I_1'$   
 $I_2 = I_2'$

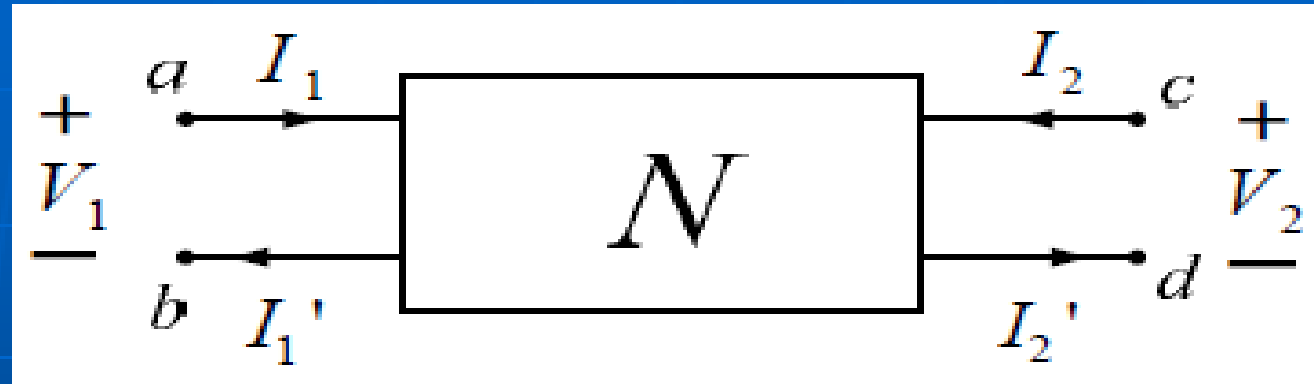Then terminals  $a$ ,  $b$  constitute the input port and terminals  $c$ ,  $d$  constitute the output port.



No external connections exist between the input and output ports.

The two-port model is used to describe the performance of a circuit in terms of the voltage and current at its input and output ports.

Two-port circuits are useful in communications, control systems, power systems, and electronic systems.

They are also useful for facilitating cascaded design of more complex systems.

## Z Parameters


Z – parameter also called as impedance parameter and the units is ohm ( $\Omega$ )

Impedance parameters is commonly used in the synthesis of filters and also useful in the design and analysis of impedance matching networks and power distribution networks.


The two – port network may be voltage – driven or current – driven.

GALGOTIAS  
UNIVERSITY

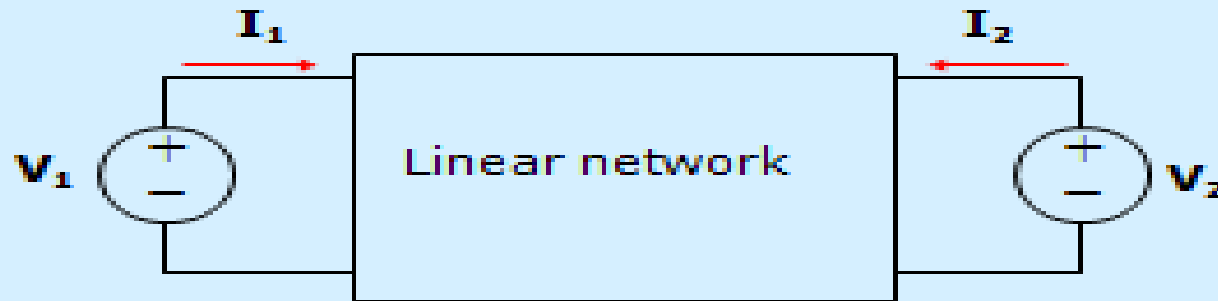- Two – port network driven by voltage source.




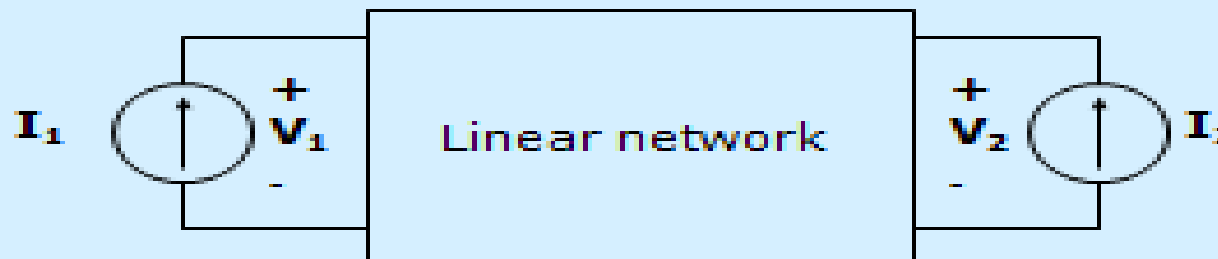- Two – port network driven by current sources.





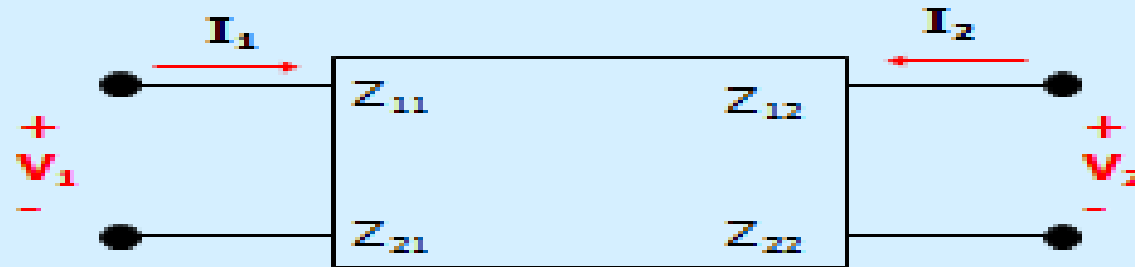
- The "black box" is replaced with Z-parameter as shown below.



- The terminal voltage can be related to the terminal current as:

$$V_1 = z_{11}I_1 + z_{12}I_2 \quad \text{————— (1)}$$
 
$$V_2 = z_{21}I_1 + z_{22}I_2 \quad \text{————— (2)}$$



- In matrix form as:

$$\begin{bmatrix} V_1 \\ V_2 \end{bmatrix} = \begin{bmatrix} z_{11} & z_{12} \\ z_{21} & z_{22} \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \end{bmatrix}$$

- The Z-parameter that we want to determine are  $z_{11}$ ,  $z_{12}$ ,  $z_{21}$ ,  $z_{22}$ .
- The value of the parameters can be evaluated by setting:
  1.  $I_1 = 0$  (input port open – circuited)
  2.  $I_2 = 0$  (output port open – circuited)

$$Z_{11} = \frac{V_1}{I_1} \Big|_{I_2=0}$$

$$Z_{12} = \frac{V_1}{I_2} \Big|_{I_1=0}$$

$$Z_{21} = \frac{V_2}{I_1} \Big|_{I_2=0}$$

$$Z_{22} = \frac{V_2}{I_2} \Big|_{I_1=0}$$

Where;

$z_{11}$  = open – circuit input impedance.

$z_{12}$  = open – circuit transfer impedance from port 1 to port 2.

$z_{21}$  = open – circuit transfer impedance from port 2 to port 1.

$z_{22}$  = open – circuit output impedance.

GALGOTIAS  
UNIVERSITY

## References

1. M. E. Van Valkenburg, "Network Analysis", Prentice Hall, 2006.
2. D. Roy Choudhury, "Networks and Systems", New Age International Publications, 1998.
3. W. H. Hayt and J. E. Kemmerly, "Engineering Circuit Analysis", McGraw Hill Education, 2013.
4. C. K. Alexander and M. N. O. Sadiku, "Electric Circuits", McGraw Hill Education, 2004.
5. K. V. V. Murthy and M. S. Kamath, "Basic Circuit Analysis", Jaico Publishers, 1999. Syllabus
6. K.M. Soni, " Network Theory", S.K. Kataria Publication

