

Analog Electronics Circuit

Course Code	BEEE3021
-------------	----------



GALGOTIAS
UNIVERSITY

BJT Review -2



GALGOTIAS
UNIVERSITY

Source & References:



The materials presented in this lecture has been taken from various books and internet websites. This instruction materials is for instructional purposes only.

Referred book: R. Boylestad, Electronic Devices and Circuit Theory, 11th edition, Prentice Hall.

Common–Emitter Configuration


The emitter is common to both input (base-emitter) and output (collector- emitter).

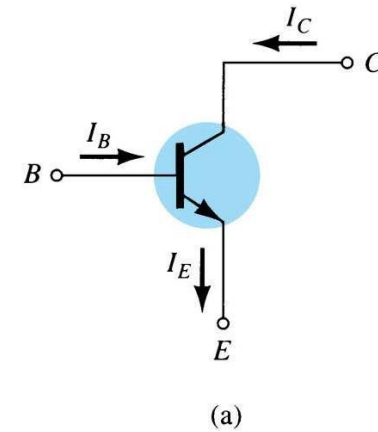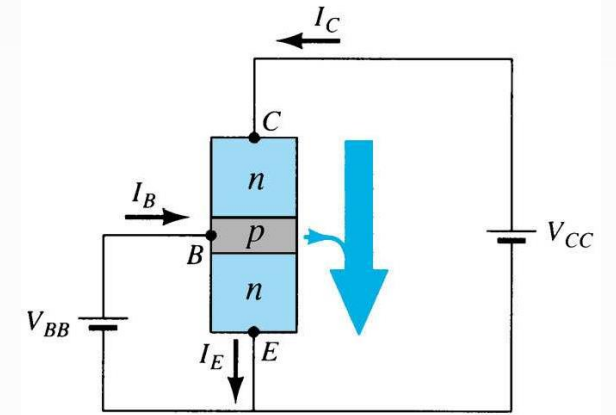The input is on the base and the output is on the collector.




GALGOTIA
UNIVERSITY

Common-Emitter Characteristics

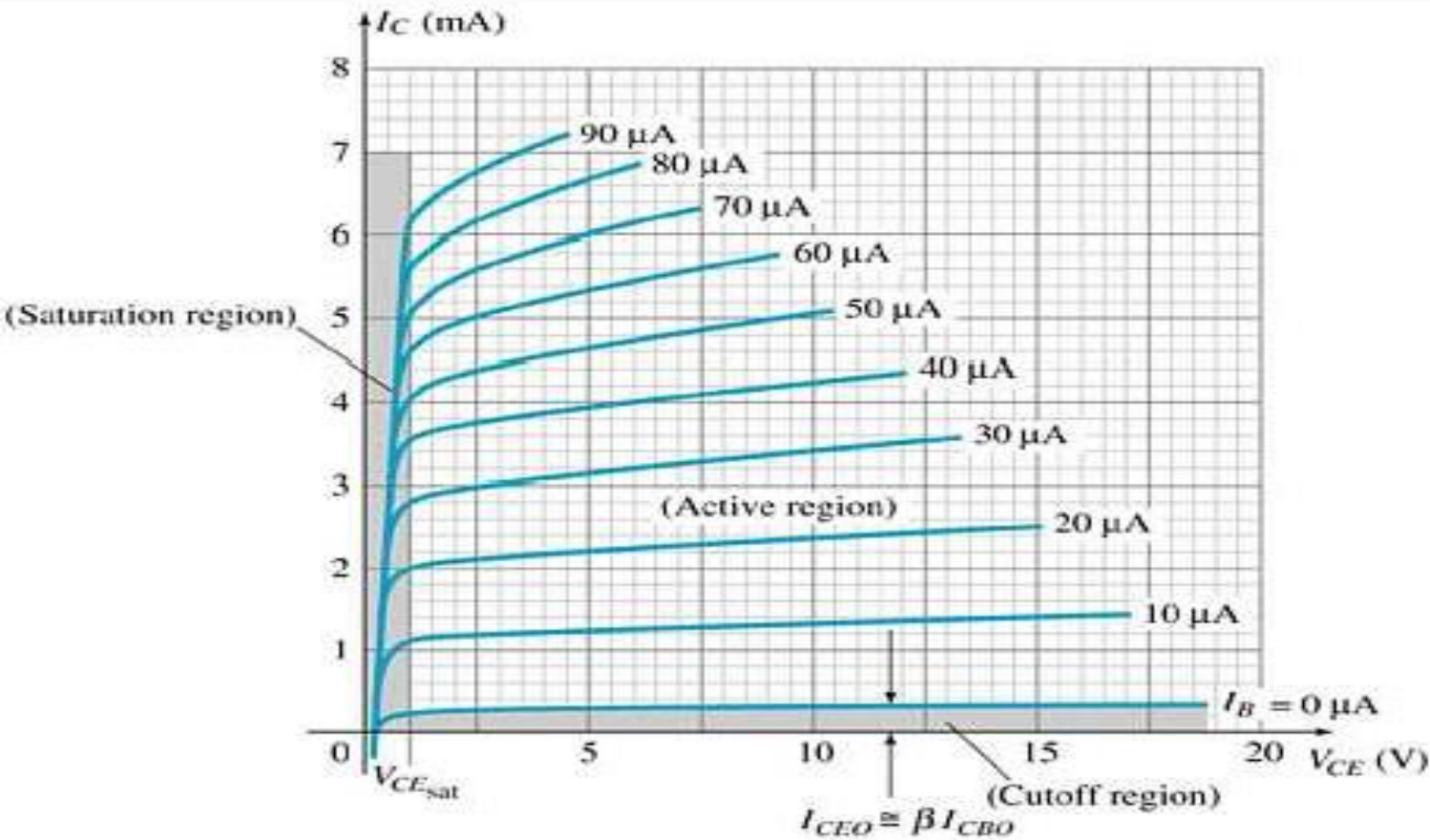

Collector Characteristics

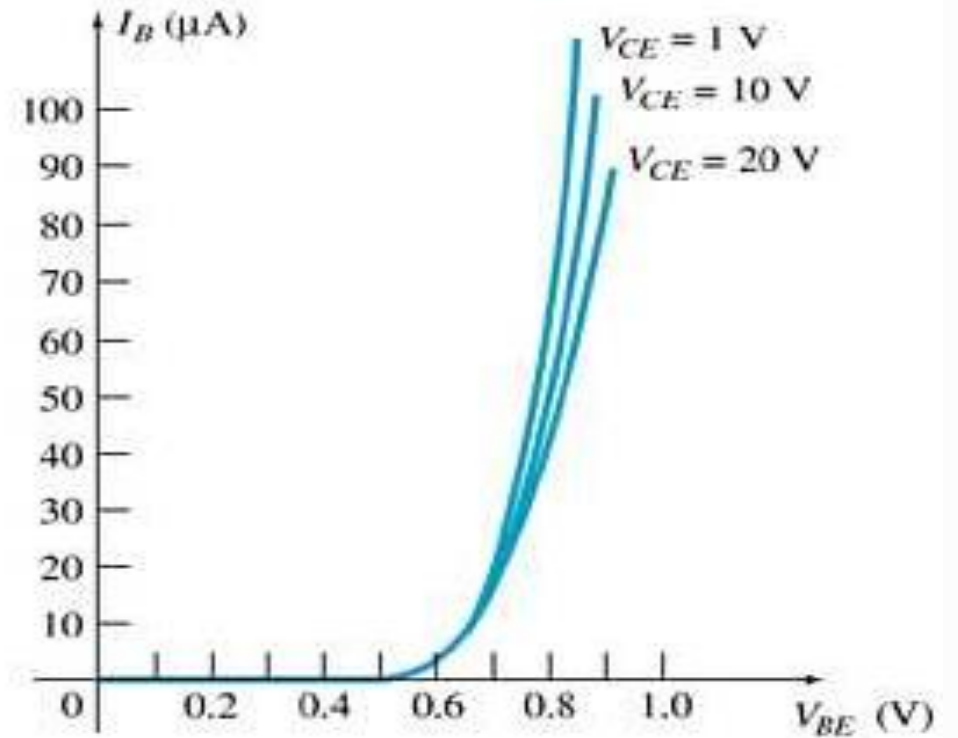

Base Characteristics

Common-Emitter Amplifier Currents

Ideal Currents

$$I_E = I_C + I_B$$

$$I_C = \alpha I_E$$

Actual Currents

$$I_C = \alpha I_E + I_{CBO}$$

where I_{CBO} = minority collector current

I_{CBO} is usually so small that it can be ignored, except in high power transistors and in high temperature environments.

When $I_B = 0 \mu\text{A}$ the transistor is in cutoff, but there is some minority current flowing called I_{CEO} .

$$I_{CEO} = \frac{I_{CBO}}{1 - \alpha} \Big|_{I_B = 0 \mu\text{A}}$$

Beta (β)

β represents the amplification factor of a transistor. (β is sometimes referred to as h_{fe} , a term used in transistor modeling calculations)

In DC mode:

$$\beta_{dc} = \frac{I_C}{I_B}$$

In AC mode:

$$\beta_{ac} = \left. \frac{\Delta I_C}{\Delta I_B} \right|_{V_{CE} = \text{constant}}$$


GALGOTIAS
UNIVERSITY

Beta (β)

Determining β from a Graph

$$\begin{aligned}\beta_{AC} &= \frac{(3.2\text{mA} - 2.2\text{mA})}{(30\mu\text{A} - 20\mu\text{A})} \\ &= \frac{1\text{mA}}{10\mu\text{A}} \Big|_{V_{CE}=7.5} \\ &= 100\end{aligned}$$

$$\begin{aligned}\beta_{DC} &= \frac{2.7\text{mA}}{25\mu\text{A}} \Big|_{V_{CE}=7.5} \\ &= 108\end{aligned}$$

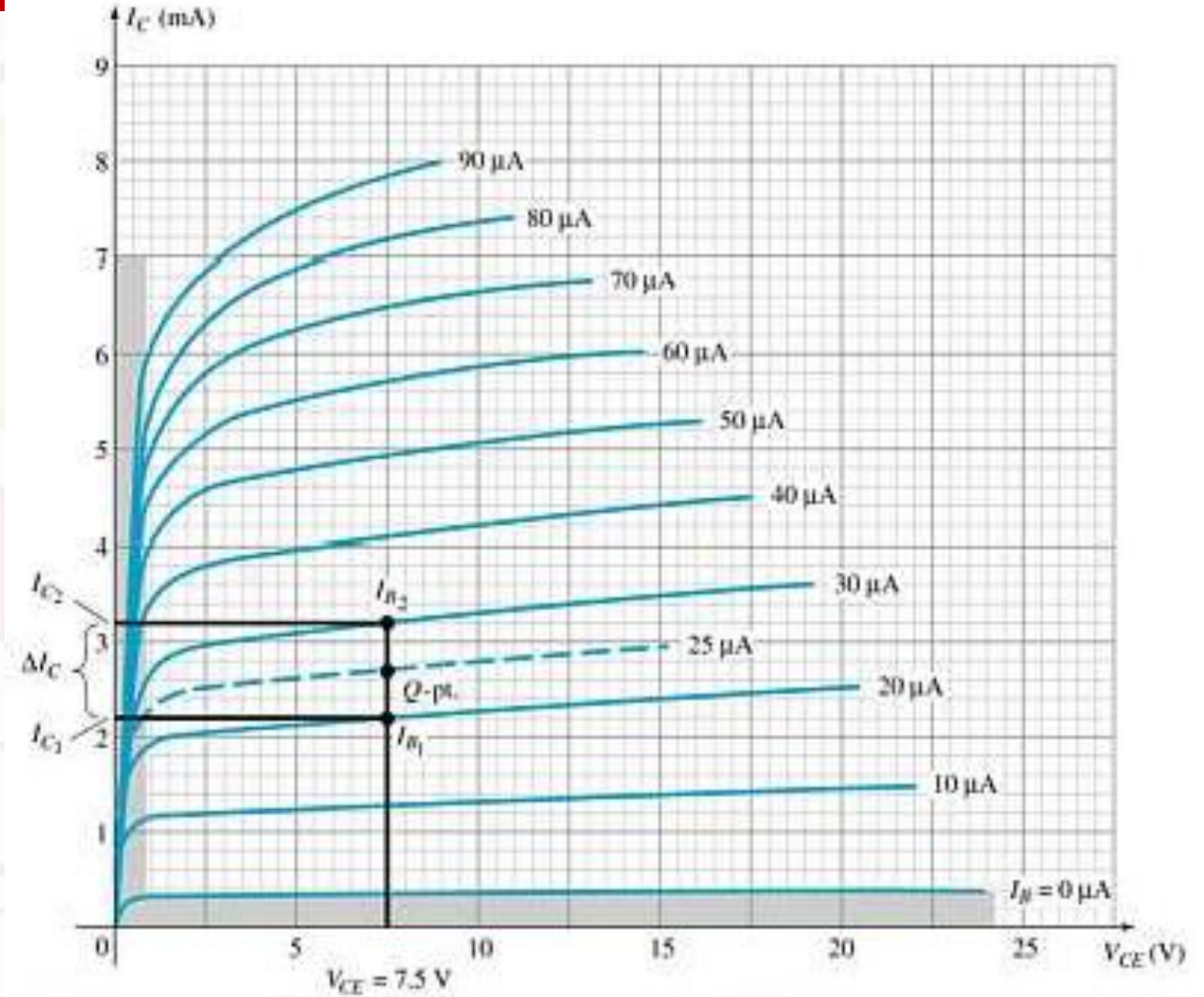

Beta (β)

Relationship between amplification factors β and α

$$\alpha = \frac{\beta}{\beta + 1} \qquad \beta = \frac{\alpha}{\alpha - 1}$$


Relationship Between Currents

$$I_C = \beta I_B \qquad I_E = (\beta + 1) I_B$$

GALGOTIAS
UNIVERSITY

Common-Collector Configuration

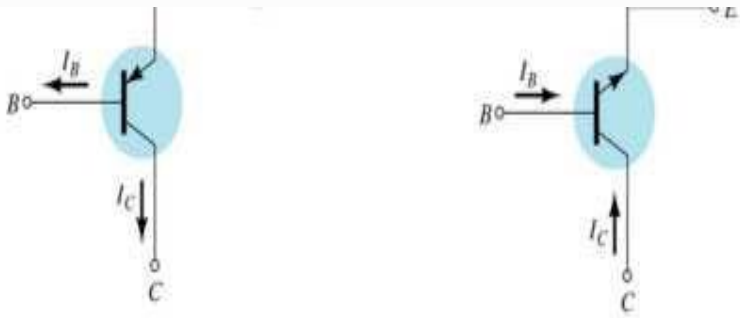
The input is on the base and the output is on the emitter.



GALGOTIAS
UNIVERSITY

Common–Collector Configuration

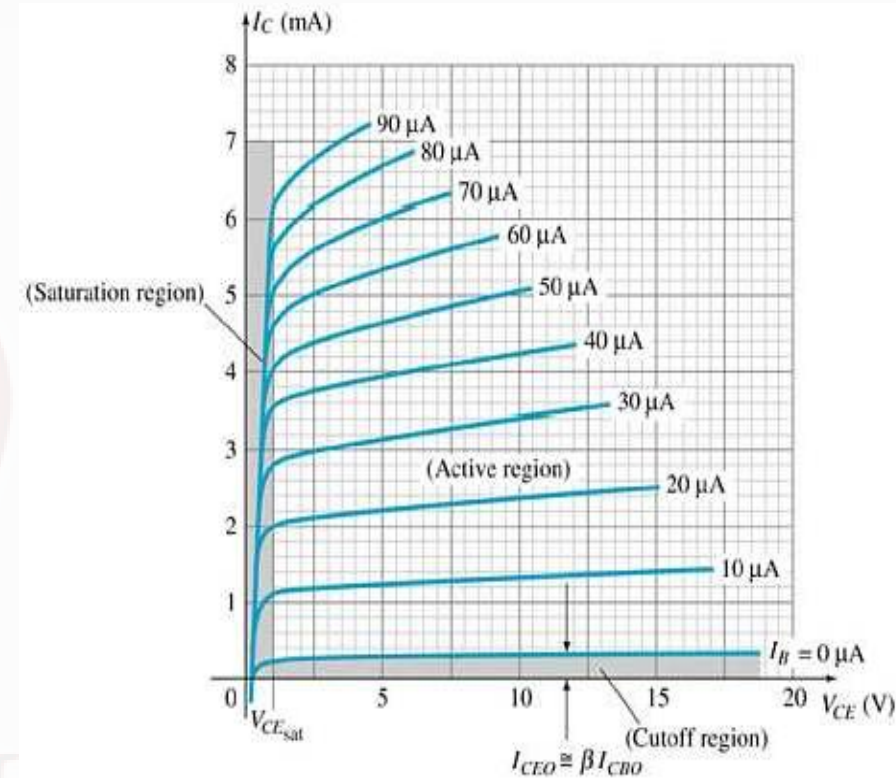The characteristics are similar to those of the common-emitter configuration, except the vertical axis is I_E .




GALGOTIAS
UNIVERSITY

Operating Limits for Each Configuration

V_{CE} is at maximum and I_C is at minimum ($I_{Cmax} = I_{CEO}$) in the cutoff region.

I_C is at maximum and V_{CE} is at minimum ($V_{CEmax} = V_{CEsat} = V_{CEO}$) in the saturation region.

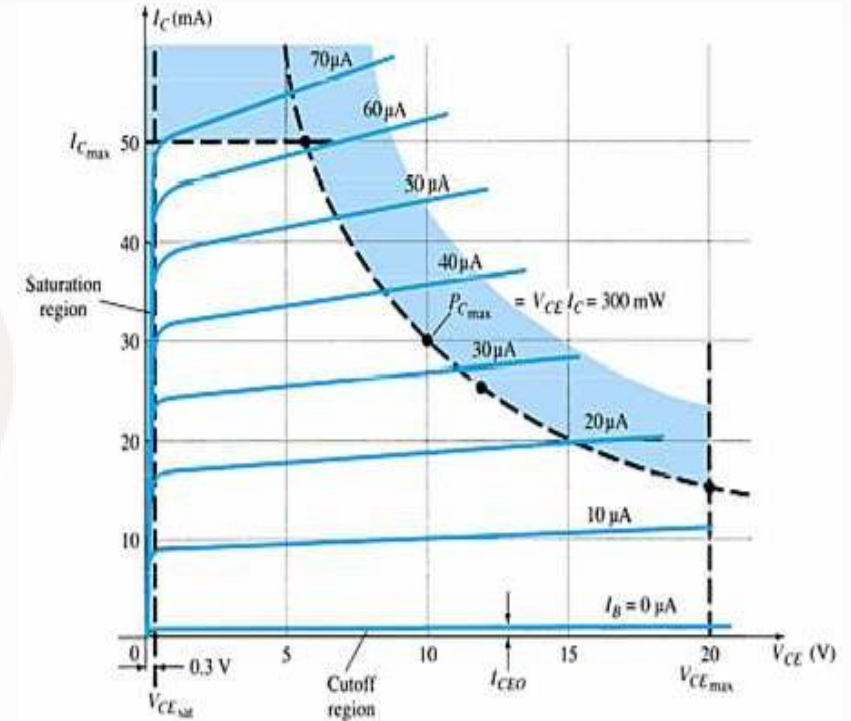The transistor operates in the active region between saturation and cutoff.



GALGOTIAS
UNIVERSITY

Power Dissipation

Common-base:

$$P_{Cmax} = V_{CB}I_C$$

Common-emitter:

$$P_{Cmax} = V_{CE}I_C$$

Common-collector:

$$P_{Cmax} = V_{CE}I_E$$

GALGOTIAS
UNIVERSITY

Transistor Specification Sheet

MAXIMUM RATINGS

Rating	Symbol	2N4123	Unit
Collector-Emitter Voltage	V_{CE0}	30	Vdc
Collector-Base Voltage	V_{CB0}	40	Vdc
Emitter-Base Voltage	V_{EB0}	5.0	Vdc
Collector Current - Continuous	I_C	200	mAdc
Total Device Dissipation @ $T_A = 25^\circ\text{C}$ Derate above 25°C	P_D	625 5.0	mW mW/°C
Operating and Storage Junction Temperature Range	T_j, T_{stg}	-55 to +150	°C

THERMAL CHARACTERISTICS

Characteristic	Symbol	Max	Unit
Thermal Resistance, Junction to Case	$R_{\theta JC}$	83.3	°C/W
Thermal Resistance, Junction to Ambient	$R_{\theta JA}$	200	°C/W

2N4123
CASE 29-04, STYLE 1
TO-92 (TO-226AA)

3 Collector
2 Base
1 Emitter

**GENERAL PURPOSE
TRANSISTOR
NPN SILICON**

Transistor Specification Sheet

ELECTRICAL CHARACTERISTICS ($T_A = 25^\circ\text{C}$ unless otherwise noted)


Characteristic	Symbol	Min	Max	Unit
OFF CHARACTERISTICS				
Collector-Emitter Breakdown Voltage (1) ($I_C = 1.0\text{ mAdc}$, $I_E = 0$)	$V_{(BR)CEO}$	30		Vdc
Collector-Base Breakdown Voltage ($I_C = 10\text{ }\mu\text{Adc}$, $I_E = 0$)	$V_{(BR)CBO}$	40		Vdc
Emitter-Base Breakdown Voltage ($I_E = 10\text{ }\mu\text{Adc}$, $I_C = 0$)	$V_{(BR)EB0}$	5.0	-	Vdc
Collector Cutoff Current ($V_{CE} = 20\text{ Vdc}$, $I_E = 0$)	I_{CBO}	-	50	nAde
Emitter Cutoff Current ($V_{BE} = 3.0\text{ Vdc}$, $I_C = 0$)	I_{EBO}	-	50	nAde
ON CHARACTERISTICS				
DC Current Gain(1) ($I_C = 2.0\text{ mAde}$, $V_{CE} = 1.0\text{ Vdc}$) ($I_C = 50\text{ mAde}$, $V_{CE} = 1.0\text{ Vdc}$)	h_{FE}	50 25	150 -	-
Collector-Emitter Saturation Voltage(1) ($I_C = 50\text{ mAde}$, $I_B = 5.0\text{ mAde}$)	$V_{CE(sat)}$	-	0.3	Vdc
Base-Emitter Saturation Voltage(1) ($I_C = 50\text{ mAde}$, $I_B = 5.0\text{ mAde}$)	$V_{BE(sat)}$	-	0.95	Vdc
SMALL-SIGNAL CHARACTERISTICS				
Current-Gain – Bandwidth Product ($I_C = 10\text{ mAde}$, $V_{CE} = 20\text{ Vdc}$, $f = 100\text{ MHz}$)	f_T	250		MHz
Output Capacitance ($V_{CE} = 5.0\text{ Vdc}$, $I_C = 0$, $f = 100\text{ MHz}$)	C_{ob}	-	4.0	pF
Input Capacitance ($V_{BE} = 0.5\text{ Vdc}$, $I_C = 0$, $f = 100\text{ kHz}$)	C_{ib}	-	8.0	pF
Collector-Base Capacitance ($I_C = 0$, $V_{CB} = 5.0\text{ V}$, $f = 100\text{ kHz}$)	C_{cb}	-	4.0	pF
Small-Signal Current Gain ($I_C = 2.0\text{ mAde}$, $V_{CE} = 10\text{ Vdc}$, $f = 1.0\text{ kHz}$)	h_{fe}	50	200	-
Current Gain – High Frequency ($I_C = 10\text{ mAde}$, $V_{CE} = 20\text{ Vdc}$, $f = 100\text{ MHz}$) ($I_C = 2.0\text{ mAde}$, $V_{CE} = 10\text{ V}$, $f = 1.0\text{ kHz}$)	h_{fe}	25 50	- 200	-
Noise Figure ($I_C = 100\text{ }\mu\text{Ade}$, $V_{CE} = 5.0\text{ Vdc}$, $R_S = 1.0\text{ k ohm}$, $f = 1.0\text{ kHz}$)	NF	-	6.0	dB

(1) Pulse Test: Pulse Width = 300 μs . Duty Cycle = 2.0%


Transistor Testing

- **Curve Tracer**
Provides a graph of the characteristic curves.
- **Digital Meters**
Some DMMs measure β_{DC} or h_{FE} .
- **Ohmmeter**

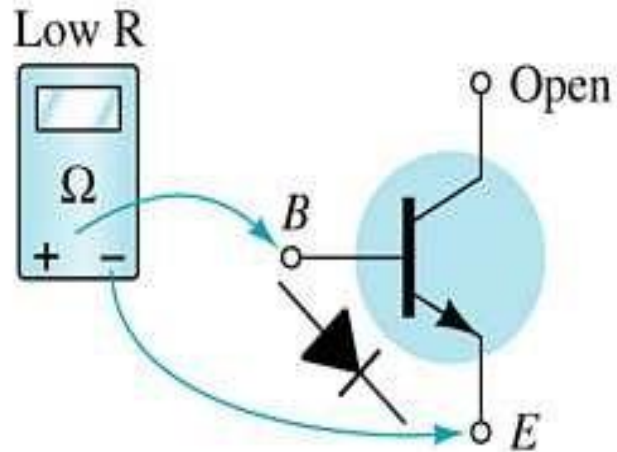- Checking the forward-biased base-to-emitter junction of an *npn* transistor.




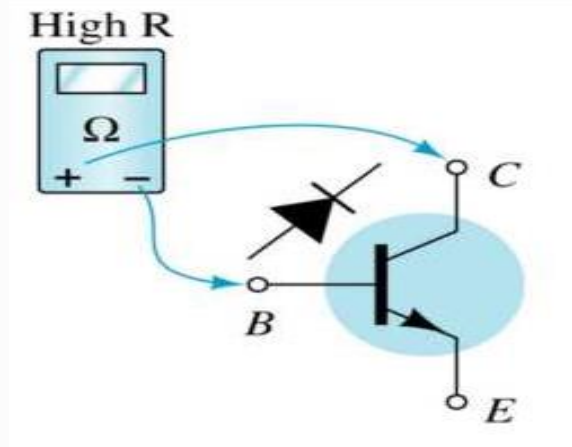- Checking the reverse-biased base-to-collector junction of an *npn* transistor.




Transistor Casing

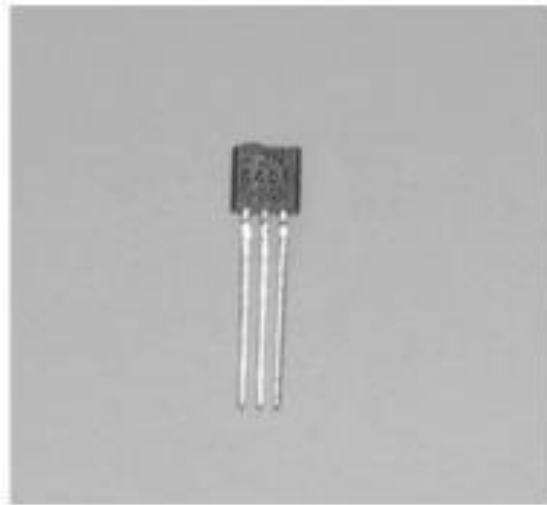- Various types of general-purpose or switching transistors:
 - (a) low power
 - (b) medium power
 - (c) medium to high power.



(a)

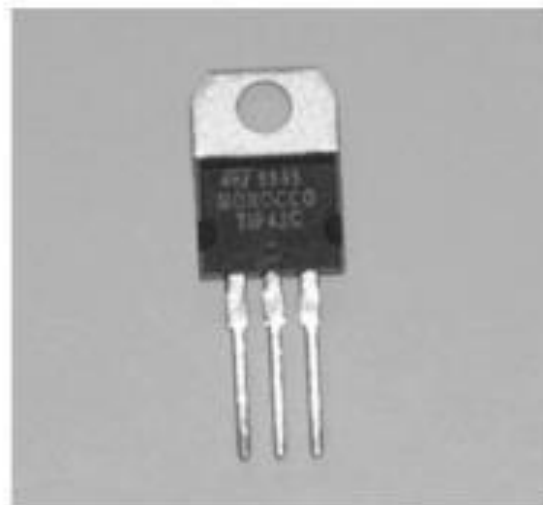


(b)




(c)

Transistor Terminal Identification

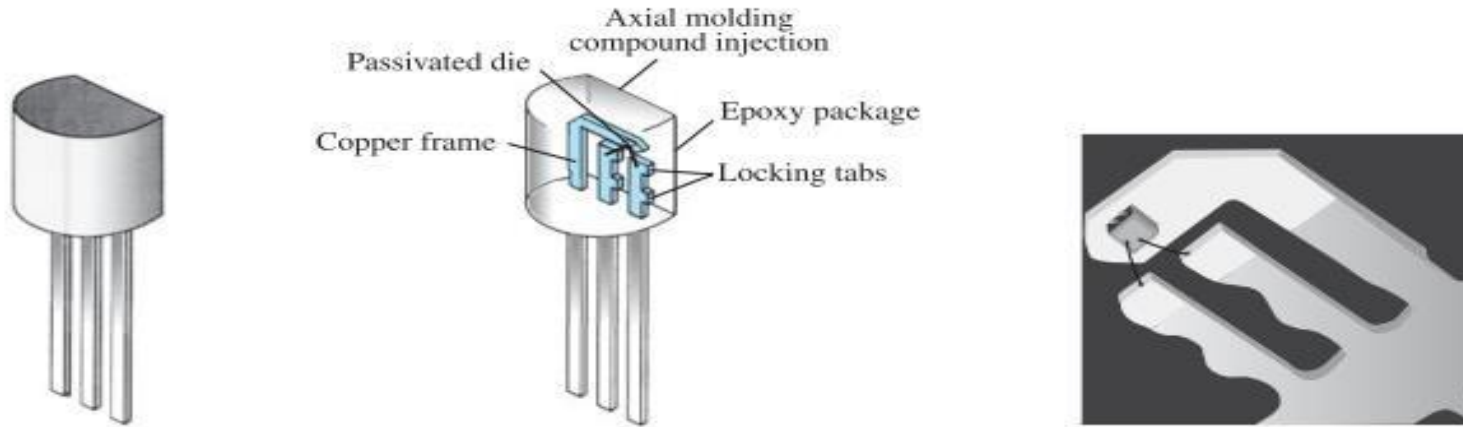- Internal construction of a Fairchild transistor in a TO-92 package.



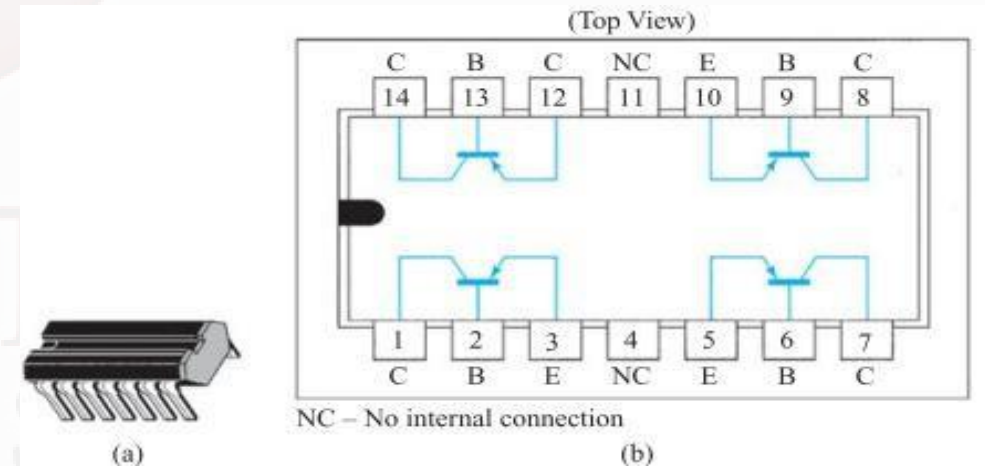- Type Q2T2905 Texas Instruments quad pnp silicon transistor:
 - (a) Appearance
 - (b) pin connections.



THANK YOU



GALGOTIAS
UNIVERSITY