

Analog Electronics Circuit

Course Code	BEEE3021
-------------	----------



GALGOTIAS
UNIVERSITY

Analog Electronics Circuit

BJT Biasing Circuits and Stabilization



Source & References:

The materials presented in this lecture has been taken from various books and internet websites. This instruction materials is for instructional purposes only.

Referred book: R. Boylestad, Electronic Devices and Circuit Theory, 11th edition, Prentice Hall.

Contents:


- Voltage-Divider bias configuration
- Collector Feedback bias Configuration
- Emitter-Follower bias configuration
- Common-Base Configuratio
- Miscellaneous bias configuration
- Bias Stabilization

The logo of Galgotias University is a stylized 'G' composed of three curved, overlapping bands in shades of yellow, blue, and red, set against a light grey circular background.


GALGOTIAS
UNIVERSITY

Voltage-Divider Configuration




- Voltage-divider bias configuration.

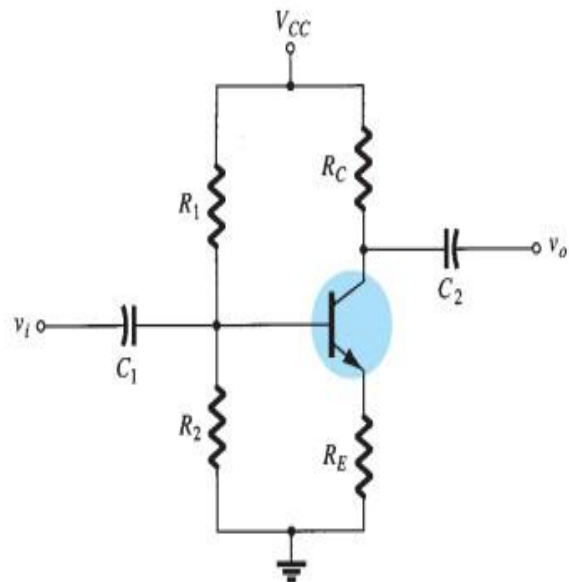

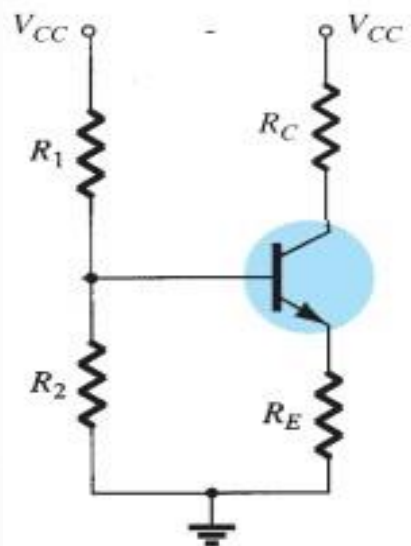- DC components of the voltage-divider configuration.




- Exact Analysis

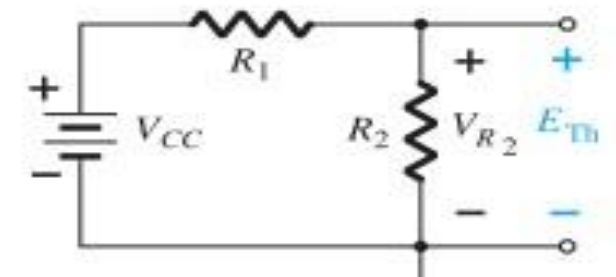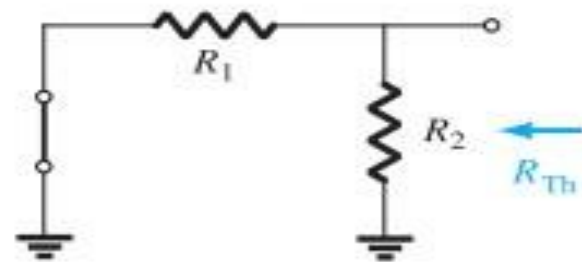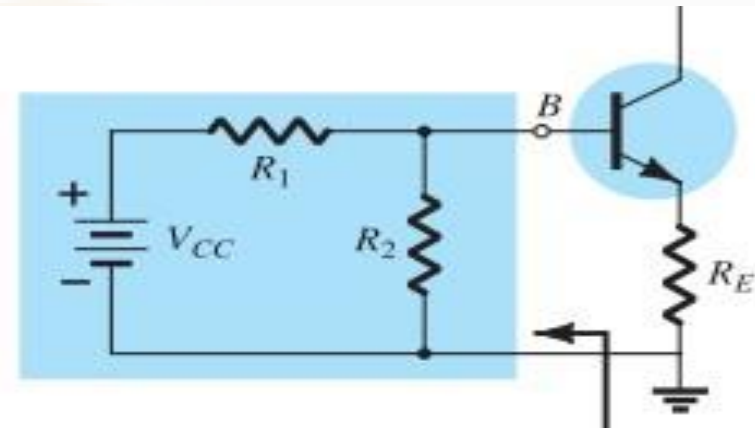

$$E_{Th} = V_{R_2} = \frac{R_2 V_{CC}}{R_1 + R_2}$$



$$R_{Th} = R_1 \parallel R_2$$

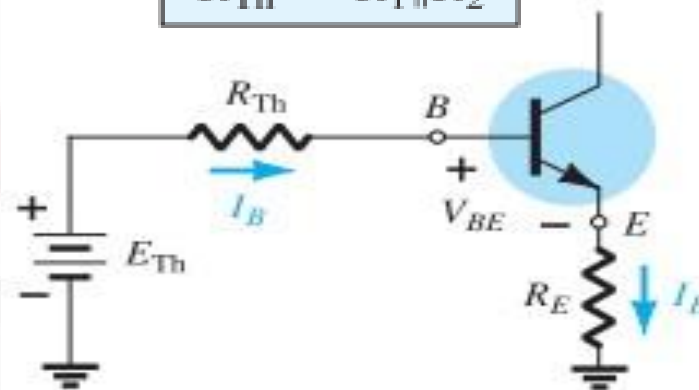

$$I_B = \frac{E_{Th} - V_{BE}}{R_{Th} + (\beta + 1)R_E}$$

$$V_{CE} = V_{CC} - I_C(R_C + R_E)$$

Fig. 1 shows the voltage divider bias method. Draw the d.c. load line and determine the operating point. Assume the transistor to be of silicon.

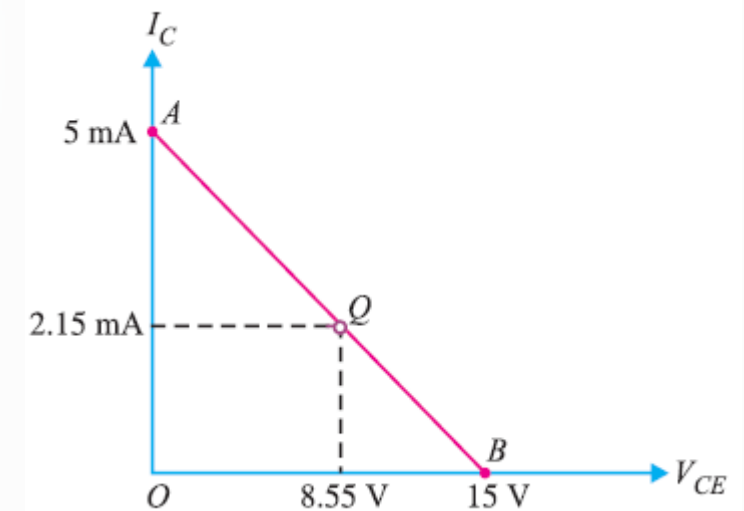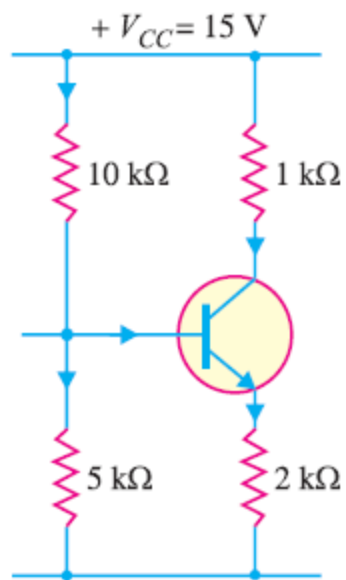

$$V_{CE} = V_{CC} - I_C(R_C + R_E)$$

When $I_C = 0$, $V_{CE} = V_{CC} = 15\text{V}$. This locates the first point B ($OB = 15\text{V}$) of the load line on the collector-emitter voltage axis.

$$\text{When } V_{CE} = 0, I_C = \frac{V_{CC}}{R_C + R_E} = \frac{15\text{V}}{(1 + 2)\text{k}\Omega} = 5\text{mA}$$

UNIVERSITY

Voltage across $5\text{ k}\Omega$ is

$$V_2 = \frac{V_{CC}}{10 + 5} \times 5 = \frac{15 \times 5}{10 + 5} = 5\text{ V}$$

$$\therefore \text{Emitter current, } I_E = \frac{V_2 - V_{BE}}{R_E} = \frac{5 - 0.7}{2\text{ k}\Omega} = \frac{4.3\text{ V}}{2\text{ k}\Omega} = 2.15\text{ mA}$$

\therefore Collector current is

$$I_C \approx I_E = 2.15\text{ mA}$$

$$\begin{aligned} \text{Collector-emitter voltage, } V_{CE} &= V_{CC} - I_C (R_C + R_E) \\ &= 15 - 2.15\text{ mA} \times 3\text{ k}\Omega = 15 - 6.45 = 8.55\text{ V} \end{aligned}$$


\therefore Operating point is **8.55 V, 2.15 mA.**

the operating point Q on the load line has co-ordinates are $I_C = 2.15\text{ mA}$, $V_{CE} = 8.55\text{ V}$.


GALGOTIAS
UNIVERSITY

Collector Feedback Configuration


- DC bias circuit with voltage feedback.

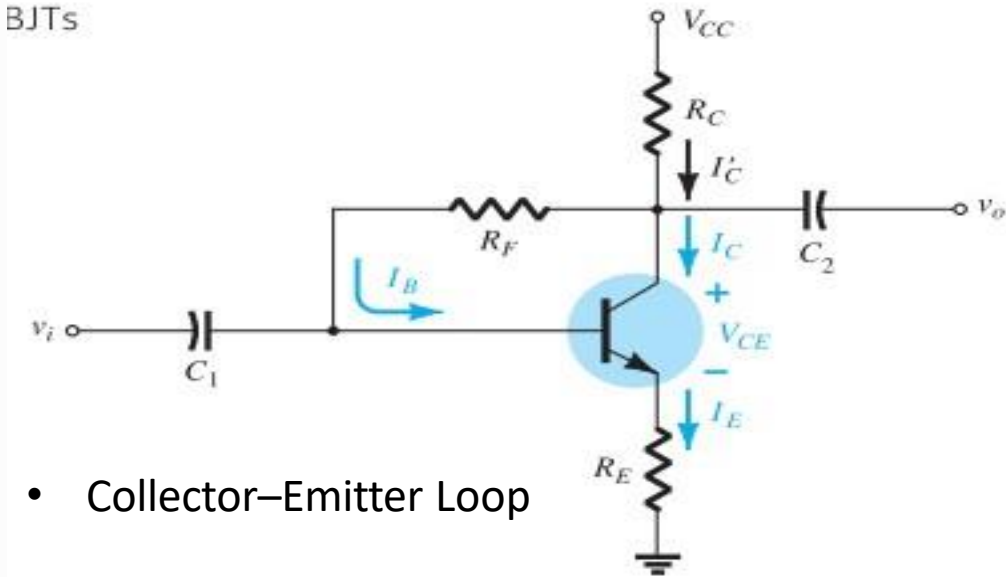

- Collector–Emitter Loop

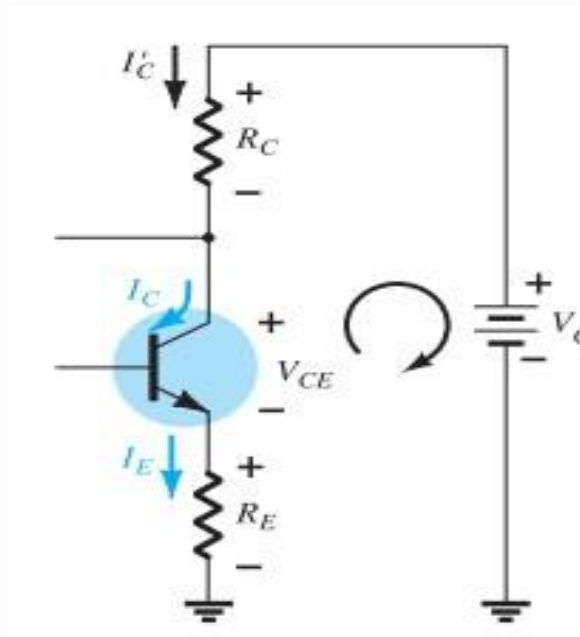

- Base–Emitter Loop

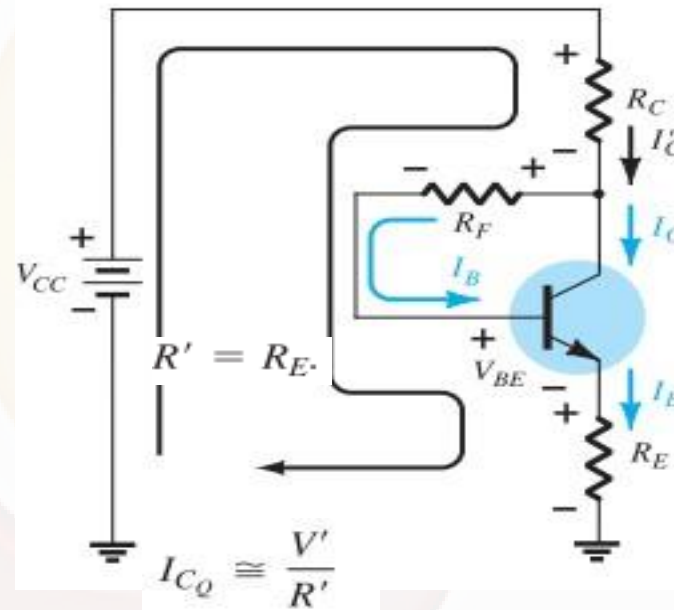

$$I_B = \frac{V_{CC} - V_{BE}}{R_F + \beta(R_C + R_E)}$$

$$I_B = \frac{V'}{R_F + \beta R'}$$

$$I_{CQ} = \frac{\beta V'}{R_F + \beta R'} = \frac{V'}{\frac{R_F}{\beta} + R'}$$

$$I_E R_E + V_{CE} + I'_C R_C - V_{CC} = 0$$

Because $I'_C \cong I_C$ and $I_E \cong I_C$, we have


$$I_C(R_C + R_E) + V_{CE} - V_{CC} = 0$$

and

$$V_{CE} = V_{CC} - I_C(R_C + R_E)$$

Emitter-Follower Configuration

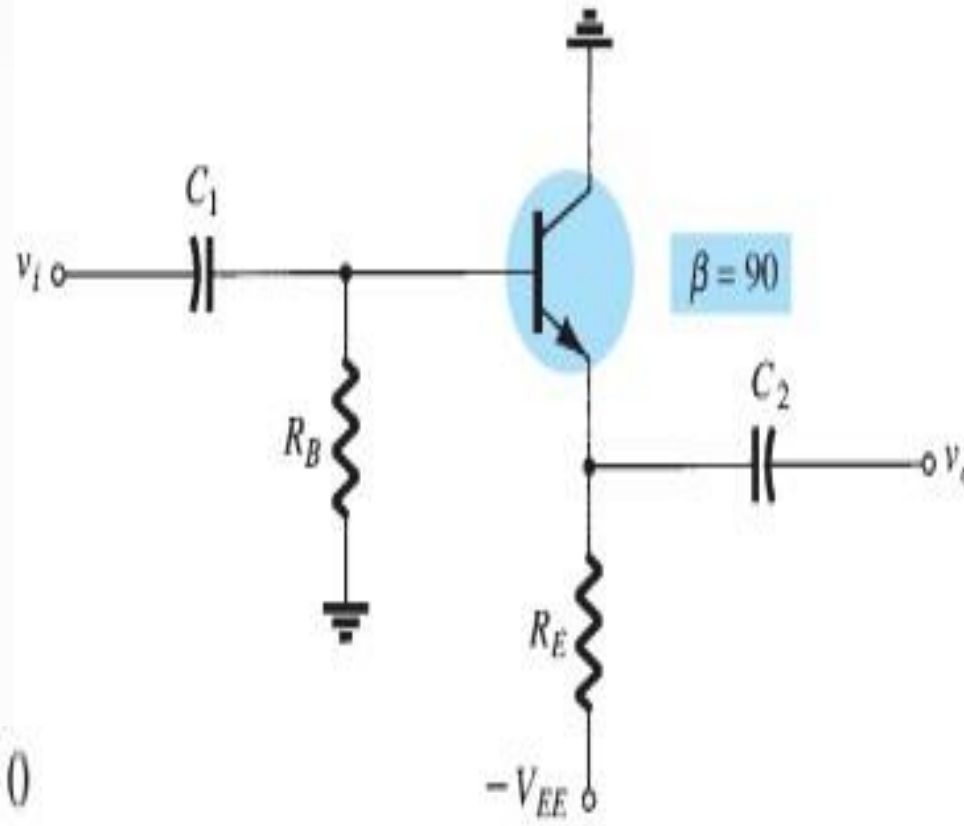- Common-collector (emitter-follower) configuration.




- dc equivalent circuit
- Input circuit

$$-I_B R_B - V_{BE} - I_E R_E + V_{EE} = 0$$

$$I_B R_B + (\beta + 1) I_B R_E = V_{EE} - V_{BE}$$
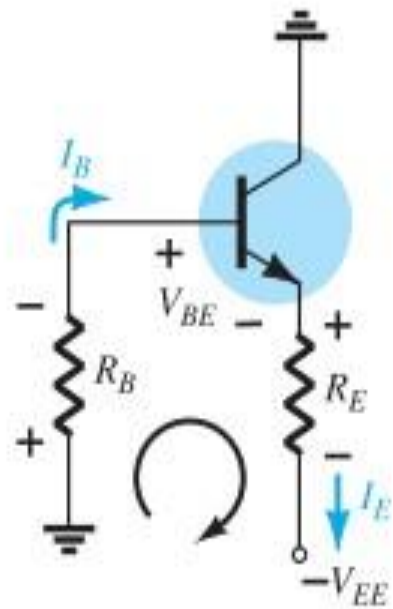
$$I_B = \frac{V_{EE} - V_{BE}}{R_B + (\beta + 1) R_E}$$



o/p ct


$$-V_{CE} - I_E R_E + V_{EE} = 0$$

$$V_{CE} = V_{EE} - I_E R_E$$

GALGOTIAS
UNIVERSITY

Emitter-Follower Configuration

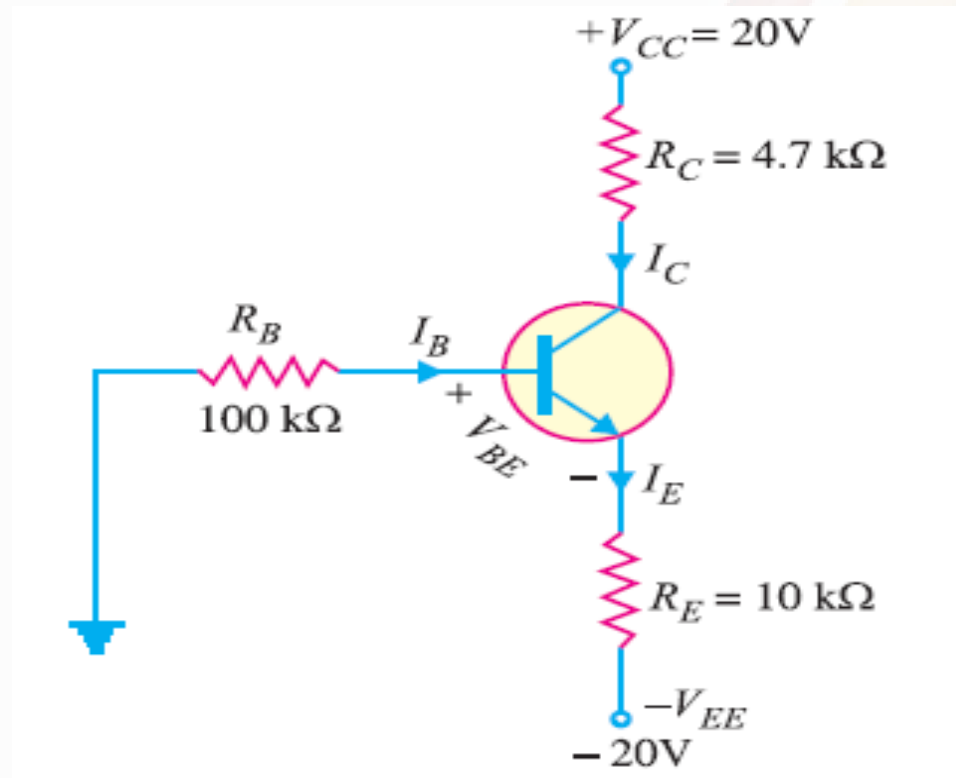Problem: For the emitter bias circuit shown in Fig. 10, find I_E , I_C , V_C and V_{CE} for $\beta = 85$ and $V_{BE} = 0.7V$.



GALGOTIAS
UNIVERSITY

Emitter-Follower Configuration

$$I_C \approx I_E = \frac{V_{EE} - V_{BE}}{R_E + R_B / \beta} = \frac{20V - 0.7V}{10 \text{ k}\Omega + 100 \text{ k}\Omega / 85} = \mathbf{1.73 \text{ mA}}$$

$$V_C = V_{CC} - I_C R_C = 20V - (1.73 \text{ mA})(4.7 \text{ k}\Omega) = \mathbf{11.9V}$$


$$V_E = -V_{EE} + I_E R_E = -20V + (1.73 \text{ mA})(10 \text{ k}\Omega) = \mathbf{-2.7V}$$

$$\therefore V_{CE} = V_C - V_E = 11.9 - (-2.7V) = \mathbf{14.6V}$$

Note that operating point (or Q – point) of the circuit is 14.6V, 1.73 mA.

Common-Base Configuration


- Common-base configuration

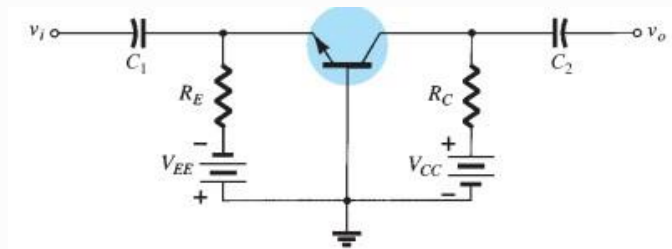

$$-V_{EE} + I_E R_E + V_{BE} = 0$$

$$I_E = \frac{V_{EE} - V_{BE}}{R_E}$$

- i/p ct

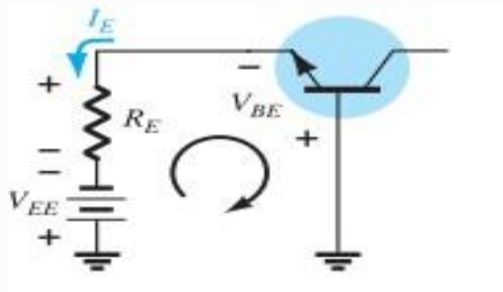


$$-V_{EE} + I_E R_E + V_{CE} + I_C R_C - V_{CC} = 0$$

$$V_{CE} = V_{EE} + V_{CC} - I_E R_E - I_C R_C$$

$$I_E \cong I_C$$

$$V_{CE} = V_{EE} + V_{CC} - I_E (R_C + R_E)$$

- Determining V_{CB} & V_{CE}

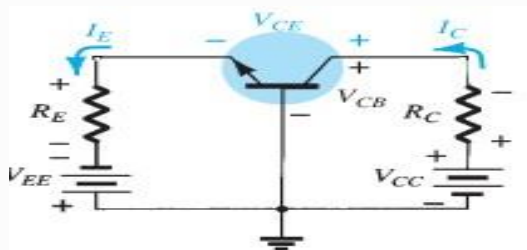

$$V_{CB} + I_C R_C - V_{CC} = 0$$

$$V_{CB} = V_{CC} - I_C R_C$$


$$I_C \cong I_E$$

$$V_{CB} = V_{CC} - I_C R_C$$

GALGOTIAS
UNIVERSITY

Common-Base Configuration

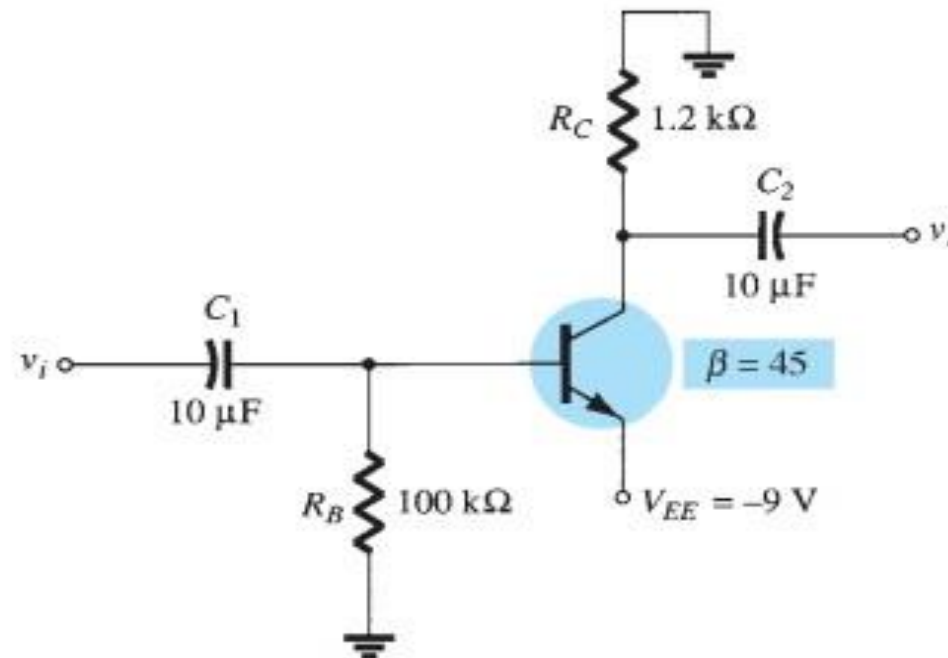EXAMPLE 4.19 Determine V_C and V_B for the network of Fig. 4.54.



Solution: Applying Kirchhoff's voltage law in the clockwise direction for the base-emitter loop results in

$$-I_B R_B - V_{BE} + V_{EE} = 0$$

and

$$I_B = \frac{V_{EE} - V_{BE}}{R_B}$$

Substitution yields

$$\begin{aligned} I_B &= \frac{9 \text{ V} - 0.7 \text{ V}}{100 \text{ k}\Omega} \\ &= \frac{8.3 \text{ V}}{100 \text{ k}\Omega} \\ &= 83 \mu\text{A} \end{aligned}$$

$$\begin{aligned} I_C &= \beta I_B \\ &= (45)(83 \mu\text{A}) \\ &= 3.735 \text{ mA} \end{aligned}$$

$$\begin{aligned} V_C &= -I_C R_C \\ &= -(3.735 \text{ mA})(1.2 \text{ k}\Omega) \\ &= -4.48 \text{ V} \end{aligned}$$

$$\begin{aligned} V_B &= -I_B R_B \\ &= -(83 \mu\text{A})(100 \text{ k}\Omega) \\ &= -8.3 \text{ V} \end{aligned}$$



Thank You

GALGOTIAS
UNIVERSITY