



Auto Transformer

GALGOTIAS
UNIVERSITY

Acknowledgement: The materials presented in this lecture has been taken from open source, reference books etc. This can be used only for student welfare and academic purpose.

Recap

- Transformer efficiency
- Condition for maximum efficiency
- Voltage regulations for lagging, leading and unity power factor load
- Conditions for zero and maximum voltage regulation
- All day efficiency and its needs
- Sumpner's Test or back to back test
- Polarity test

GALGOTIAS
UNIVERSITY

Auto Transformer

Lecture-7 Objectives

- Needs of auto transformer
- Comparison with two winding ordinary transformer
- Electrical power transfer capability of the auto transformer
- Copper saving of the auto transformer
- Advantages and disadvantages
- Applications

GALGOTIAS
UNIVERSITY

Auto Transformer

Auto Transformer


- Primary and secondary windings are connected electrically as well as magnetically.
- Therefore, power from the primary is transferred to the secondary conductively as well as inductively (transformer action).
- The voltage transformation ratio K of an ideal autotransformer is,

$$\frac{E_1}{E_2} = \frac{N_1}{N_2} = \frac{V_1}{V_2} = \frac{I_2}{I_1} = K$$

Auto Transformer

Theory of Autotransformer

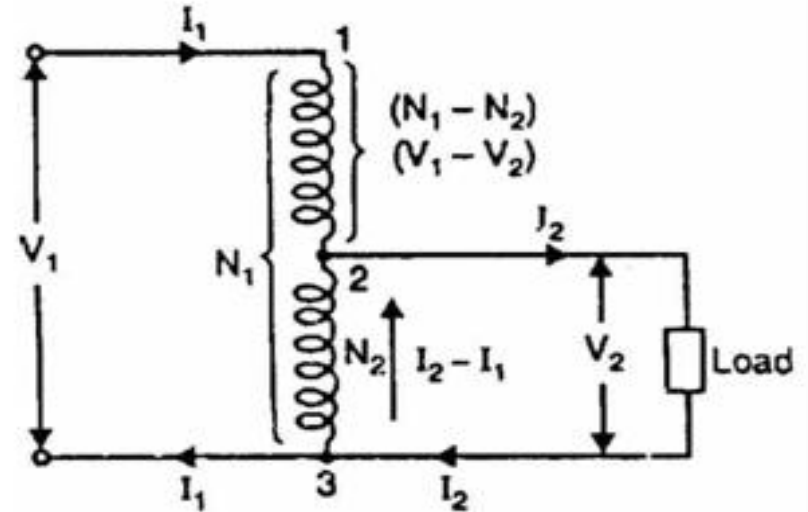- Winding 1-3 - N_1 turns - pri winding
- winding 2-3 - N_2 turns - sec winding
- Input current is I_1
- Output current is I_2
- Portion 1-2 of the wdg has $N_1 - N_2$ turns and voltage across this portion of the winding is $V_1 - V_2$.
- The current through the common portion of the winding is $I_2 - I_1$.



GALGOTIAS
UNIVERSITY

Auto Transformer

Theory of Autotransformer

- The equivalent circuit of the autotransformer.
- From this equivalent circuit, we have,


$$\frac{V_1 - V_2}{V_2} = \frac{N_1 - N_2}{N_2}$$

$$(N_1 - N_2)V_2 = (V_1 - V_2)N_2$$

$$V_2N_1 - V_2N_2 = V_1N_2 - V_2N_2$$

$$V_2N_1 = V_1N_2$$
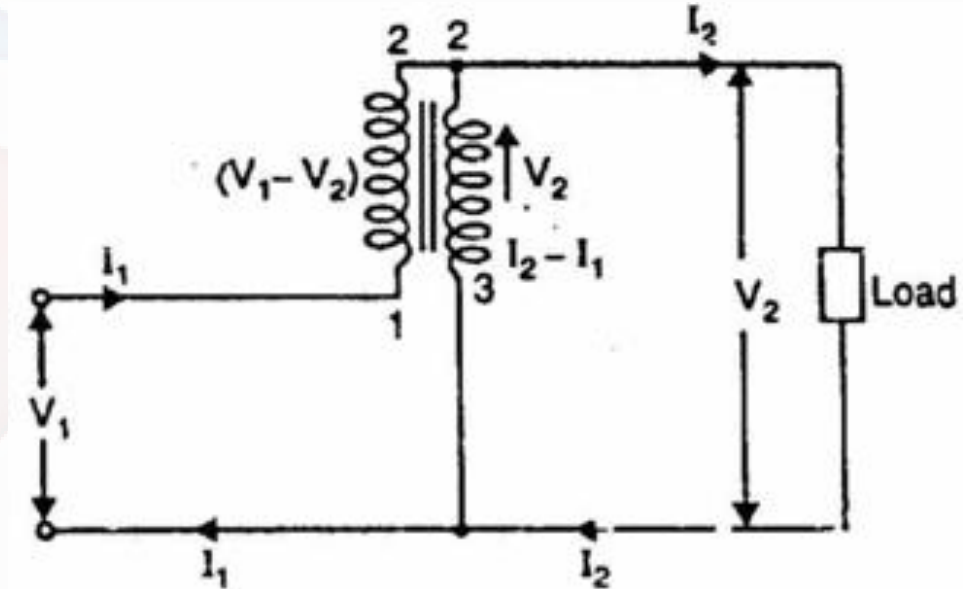
$$\frac{N_2}{N_1} = \frac{V_2}{V_1} = K$$



Auto Transformer

Output of Autotransformer


- Output apparent power = $V_2 I_2$
Apparant power transferred inductively

$$= V_2 (I_2 - I_1) = K \cdot V_1 \left(\frac{I_1}{K} - I_1 \right)$$

$$= K \cdot V_1 I_1 \left(\frac{1}{K} - 1 \right)$$

$$= K \cdot V_1 I_1 \left(\frac{1 - K}{K} \right) = V_1 I_1 (1 - K)$$

$$= \text{Input} \times (1 - K)$$

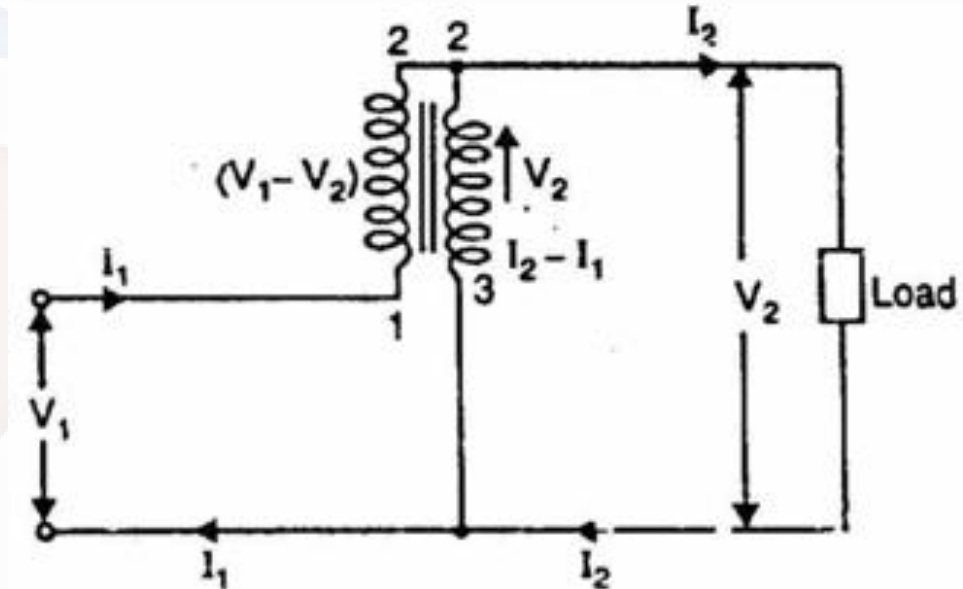

Auto Transformer

$$\begin{aligned}\text{Apparant power transferred conductively} &= \text{Input} - \text{Input} \times (1 - K) \\ &= \text{Input}[1 - (1 - K)] = \text{Input} \times K\end{aligned}$$


- Suppose the input power to an ideal autotransformer is 1000 W and its voltage transformation ratio $K = 0.25$. Then,

$$\begin{aligned}\text{Apparant power transferred inductively} &= \text{Input} \times (1 - K) = 1000 \times (1 - 0.25) \\ &= 750 \text{ W}\end{aligned}$$

$$\text{Apparant power transferred conductively} = \text{Input} \times K = 1000 \times 0.25 = 250 \text{ W}$$

Auto Transformer

Saving of Copper in Auto Transformer

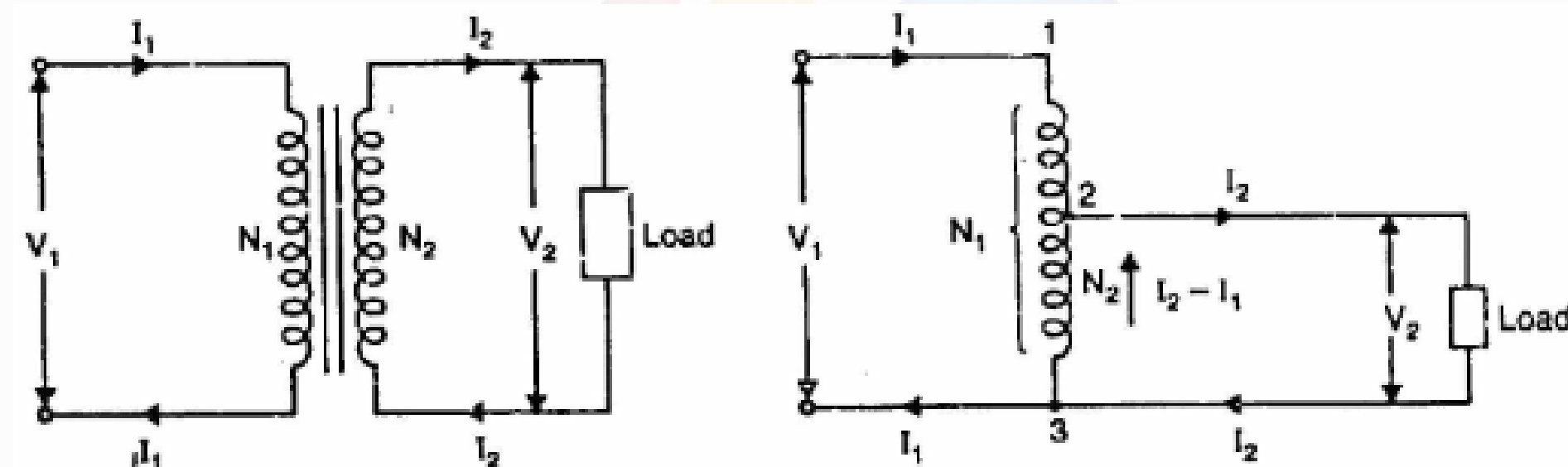

- For the same output and voltage transformation ratio, an autotransformer requires less copper than an ordinary 2-winding transformer.
- Weight of Cu required in a winding is \propto current \times turns

Auto Transformer

Saving of Copper in Auto Transformer

Two winding transformer

- Weight of Cu required $\propto (I_1 N_1 + I_2 N_2)$

Autotransformer

- Weight of Cu required in section 1-2 $\propto I_1 (N_1 - N_2)$
- Weight of Cu required in section 2-3 $\propto (I_2 - I_1) N_2$
- Total weight of Cu required $\propto I_1 (N_1 - N_2) + (I_2 - I_1) N_2$

$$\frac{\text{Weight of Cu in autotransformer}}{\text{Weight of Cu in ordinary transformer}} = \frac{I_1(N_1 - N_2) + (I_2 - I_1)N_2}{I_1 N_1 + I_2 N_2}$$

Auto Transformer

Saving of Copper in Auto Transformer

$$\begin{aligned}\frac{\text{Weight of Cu in autotransformer}}{\text{Weight of Cu in ordinary transformer}} &= \frac{I_1(N_1 - N_2) + (I_2 - I_1)N_2}{I_1N_1 + I_2N_2} \\ &= \frac{N_1I_1 - N_2I_1 + N_2I_2 - N_2I_1}{N_1I_1 + N_2I_2} = \frac{N_1I_1 + N_2I_2 - 2N_2I_1}{N_1I_1 + N_2I_2} \\ &= 1 - \frac{2N_2I_1}{N_1I_1 + N_2I_2} = 1 - \frac{2N_2I_1}{2N_1I_1} \quad (\because N_2I_2 = N_1I_1) \\ &= 1 - \frac{N_2}{N_1} = 1 - K\end{aligned}$$

$$\text{Weight of Cu. in auto tfr } (W_a) = (1 - K) \times \text{weight of Cu. in ordinary tfr } (W_o)$$

Auto Transformer

Saving of Copper in Auto Transformer

$$W_a = (1 - K) \times W_o$$

$$\therefore \text{Saving in Cu} = W_o - W_a = W_o - (1 - K)W_o = K W_o$$

Saving in Cu = $K \times$ Wt. of Cu in ordinary transformer

- Thus if $K = 0.1$, the saving of Cu is only 10% but if $K = 0.9$, saving of Cu is 90%.
- Therefore, saving of Cu is more when K is nearer to 1.

Auto Transformer

Advantages of Autotransformers

- An autotransformer requires less Cu than a two-winding transformer of similar rating.
- Autotransformer operates at a higher efficiency than a two-winding transformer of similar rating.
- An autotransformer has better voltage regulation than a two-winding transformer of the same rating.
- An autotransformer has smaller size than a two-winding transformer of the same rating.

Auto Transformer

Advantages of Autotransformers

- An autotransformer requires smaller exciting current than a two-winding transformer of the same rating.
- These advantages decrease as the ratio of transformation increases. So an autotransformer has advantages only for low values of transformation ratio.

GALGOTIAS
UNIVERSITY

Auto Transformer

Disadvantages of Autotransformers

- There is a direct connection between the primary and secondary. Therefore, the output is no longer isolated from the input.
- It is not safe for stepping down a high voltage to a low voltage.
- The short - circuit current is much larger than for the two-winding transformer of the same rating.
- This reduces the effective resistance and reactance.

Auto Transformer

Applications of Autotransformers

- Autotransformers are used to compensate for voltage drops in transmission and distribution lines. When used for this purpose, they are known as booster transformers.
- Autotransformers are used for reducing the voltage supplied to a.c. motors during the starting period.
- Autotransformers are used for continuous variable supply.

Auto Transformer

Summary

- Needs of auto transformer
- Comparison with two winding ordinary transformer
- Electrical power transfer capability of the auto transformer
- Copper saving of the auto transformer
- Advantages and disadvantages
- Applications

GALGOTIAS
UNIVERSITY