



# **DC Generator Induced EMF and Classification**

**GALGOTIAS  
UNIVERSITY**

*Acknowledgement: The materials presented in this lecture has been taken from open source, reference books etc. This can be used only for student welfare and academic purpose.*

# Recap

- Constructional details of DC Machines
- Fleming's Right Hand Rule
- Operation of the generator and motor
- Induced EMF
- Armature Winding

GALGOTIAS  
UNIVERSITY

## Lecture-13 Objectives

- Induced EMF
- Generating mode and motoring mode
- Methods of excitation
- Classification of DC machines

GALGOTIAS  
UNIVERSITY

# EMF Equation of DC Generator

- Whether a DC machine working as generator or a motor, its armature rotates in the magnetic field in the air-gap.
- Armature conductors cut the magnetic flux and therefore EMF is induced in them.
- In case of generator, this emf supplies the load.
- In case of motor, this emf opposes the applied voltage.
- The expression for induced emf is same for both motor and generator.

# EMF Equation of DC Generator

- Let  $\phi$  – flux available under each pole.
  - $Z$  – total no. of conductors in the armature
  - $P$  – No. of poles
  - $A$  – No. of parallel paths
  - $N$  – Speed of armature in rpm
  - $E_g$  – Generated or Induced emf

## EMF Equation of DC Generator

- As per Faraday's law, EMF induced in a coil is,

$$E = N \frac{d\phi}{dt}$$

- Flux cut by one conductor in one revolution of the armature,


$$d\phi = P\phi \text{ webers}$$

- Time taken to complete one revolution,

$$dt = \frac{60}{N} \text{ seconds}$$

- EMF induced in one conductor is,
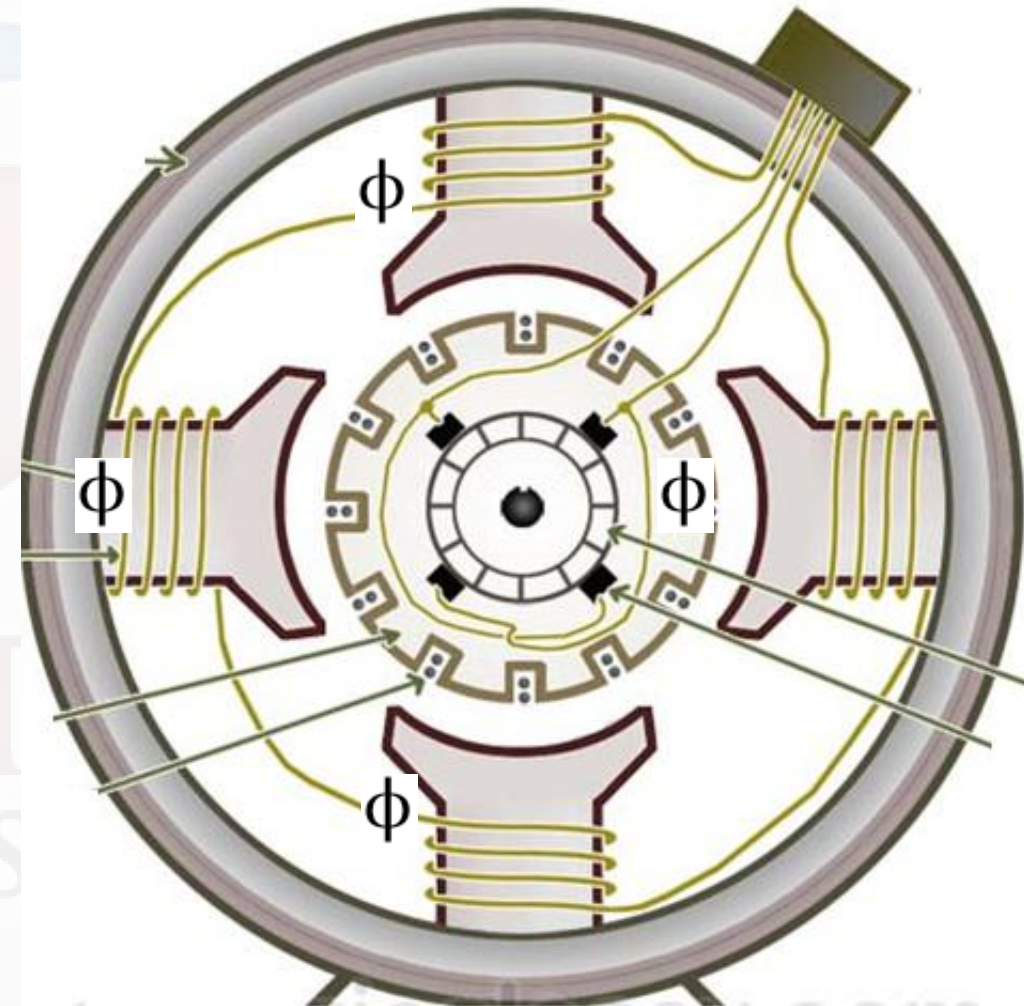
$$E_g = \frac{d\phi}{dt} = \frac{P\phi}{60/N} = \frac{P\phi N}{60} \text{ volts}$$



# EMF Equation of DC Generator

- EMF generated in whole armature is,



$$E_g = \frac{P\phi N}{60} \times Z \text{ volts}$$

- EMF per parallel path,

$$E_g = \frac{P\phi NZ}{60 A} = \frac{\phi Z N}{60} \times \frac{P}{A}$$
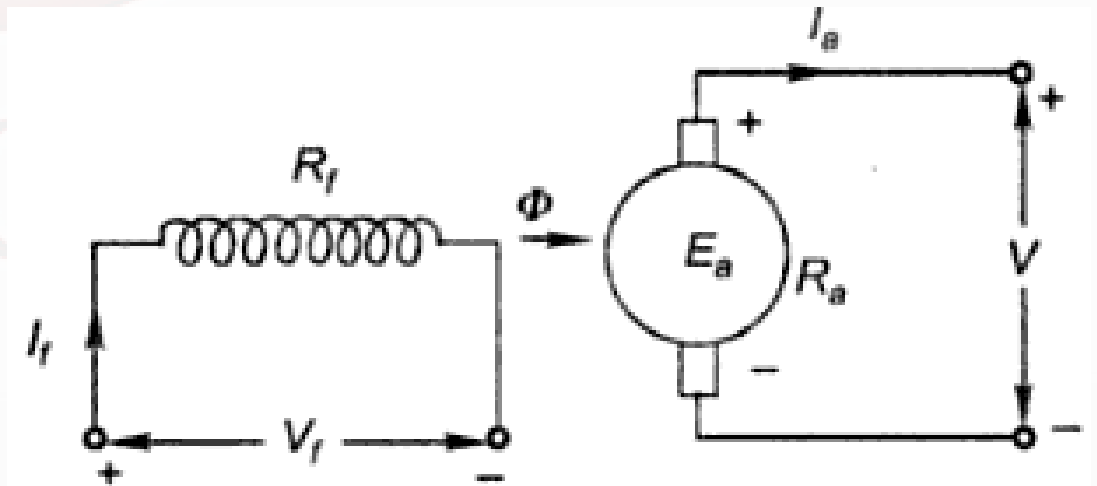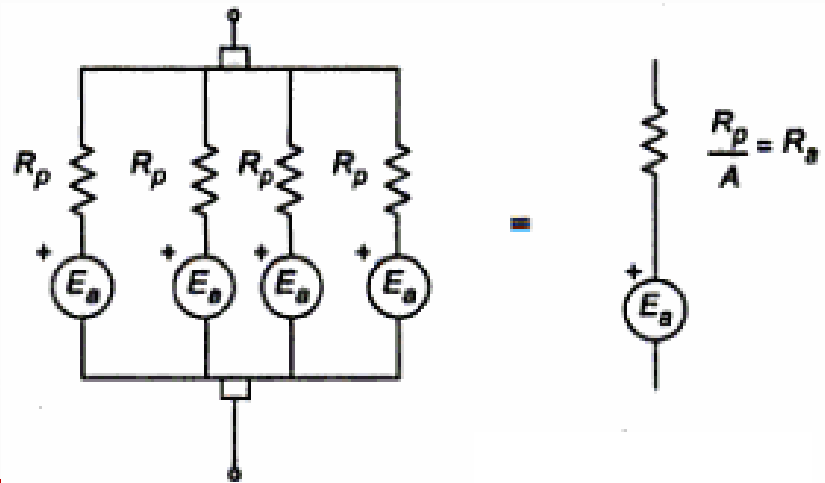
## Circuit Model of a DC Machine


- Each parallel path of a DC machine has an induced voltage of  $E_g$  & resistance of  $R_p$ .
- Hence the equivalent armature resistance is  $(R_p/A)$  which is very small to limit copper loss to a low value.
- The voltage drop at brush – commutator contact is fixed (1 – 2V) and this effect is included with  $R_a$  itself.




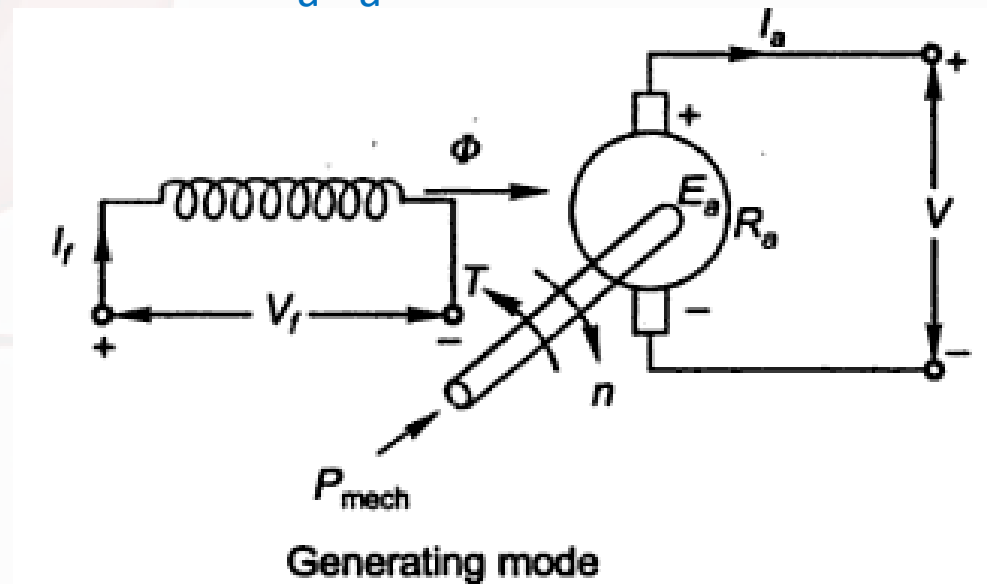
## Generating Mode


- The m/c operates in generating mode when the  $I_a$  in the direction of  $E_g$ .
- For the armature circuit,  $V_t = E_g - I_a \cdot R_a$ ;  $E_g > V_t$
- The electrical power generated from mech power is,  $E_a \cdot I_a$
- The net electrical power output is,  $P_O = V_t \cdot I_a$
- $E_a \cdot I_a - V_t \cdot I_a = I_a^2 \cdot R_a = \text{Armature copper loss.}$



GALGO  
UNIVER
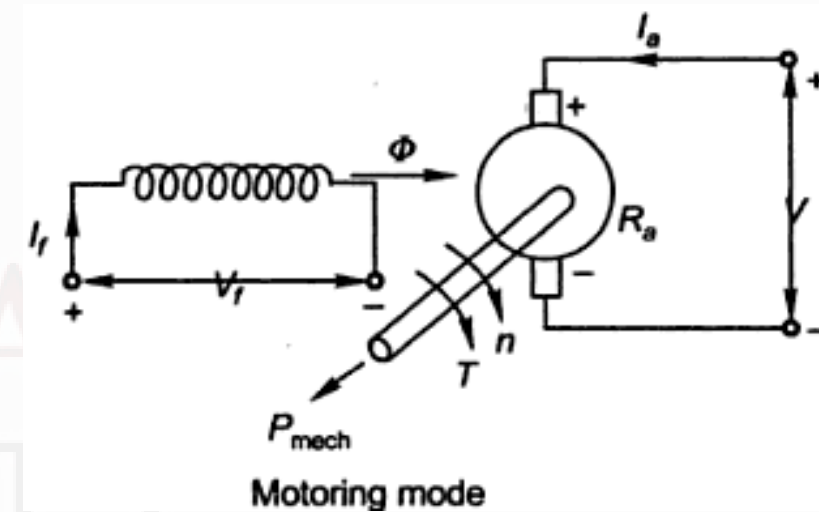
## Motoring Mode

- Here  $I_a$  flows in opposite to back emf  $E_b$ . This  $E_b$  opposes the supply voltage.
- Hence for the armature circuit,  $V_t = E_b + I_a \cdot R_a$ ;  $E_b < V_t$
- The electrical power input is,  $P_i = V_t \cdot I_a$
- Hence  $V_t \cdot I_a - E_a \cdot I_a = I_a^2 \cdot R_a = \text{Armature copper loss}$



GALGOTIA  
UNIVERSITY


# Methods of Excitation

- The magnetic field in a d.c. generator is normally produced by electromagnets rather than permanent magnets.
- Generators are generally classified according to their methods of field excitation.
  - Separately excited d.c. generators
  - Self-excited d.c. generators
- The behaviour of a d.c. generator on load depends upon the method of field excitation adopted.
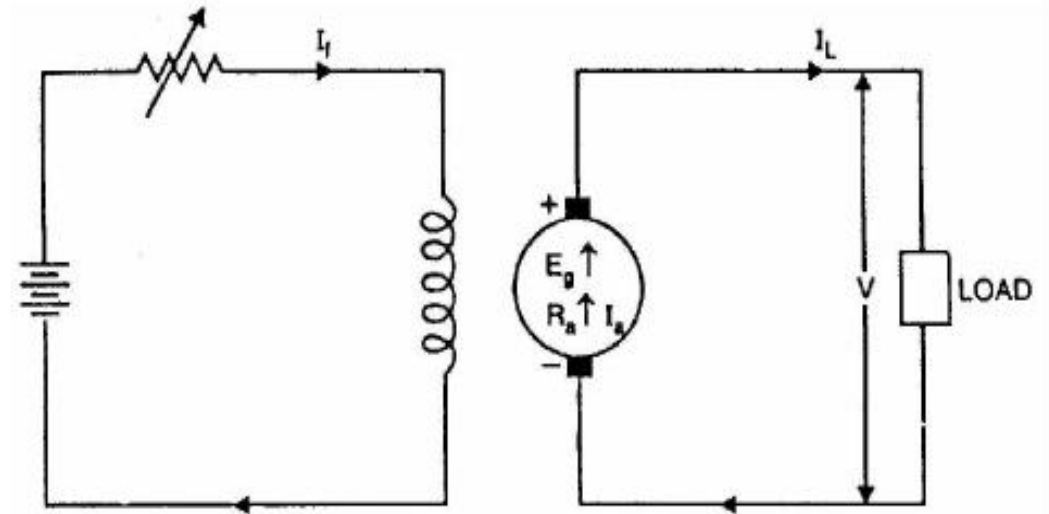
# Separately Excited DC generator

- Here the field is excited from a separate source independent of armature circuit.

- Armature current,  $I_a = I_L$
- Terminal voltage,  $V_t = E_g - I_a R_a$
- Electric power developed =  $E_g I_a$
- Power delivered to load =  $E_g I_a - I_a^2 R_a = I_a (E_g - I_a R_a)$




# Self Excited DC Generators

- A d.c. generator whose field winding is supplied current from the output of the generator itself is called a self-excited generator.
- There are three types of self-excited generators depending upon the manner in which the field winding is connected to the armature, namely;
  - Series generator
  - Shunt generator
  - Compound generator
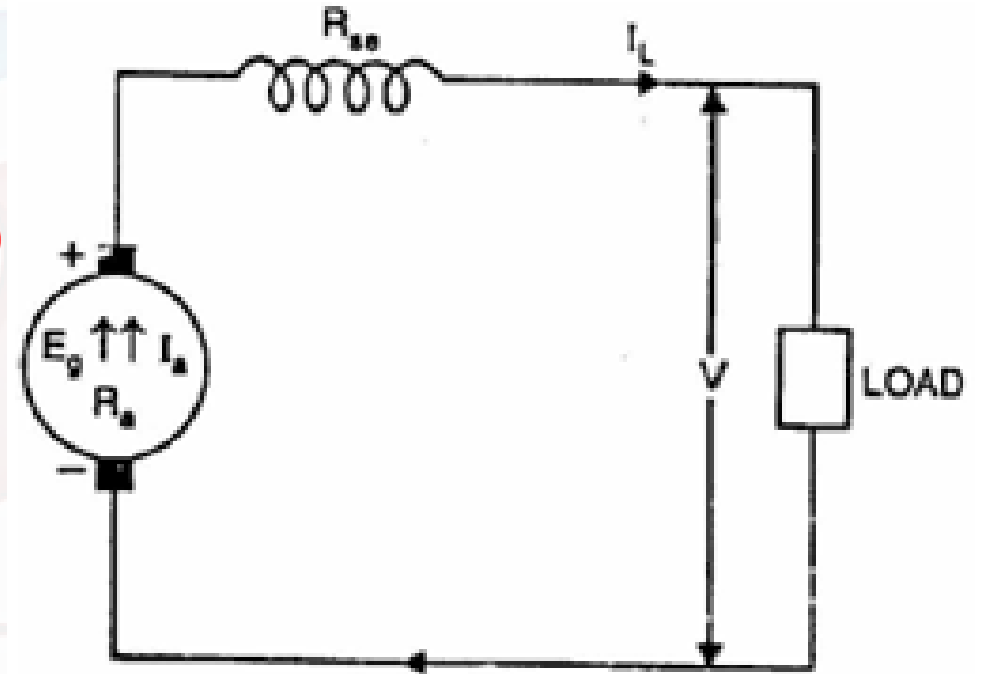
## Series Generator


- Armature current,  $I_a = I_{se} = I_L$
- Terminal voltage,  $V = E_g - I_a(R_a + R_{se})$
- Power developed in armature =  $E_g I_a$



- Power delivered to load =  $E_g I_a - I_a^2 R_a - I_a^2 R_{se} =$    
 $= I_a [E_g - I_a (R_a + R_{se})] = V \cdot I_a = V \cdot I_L$
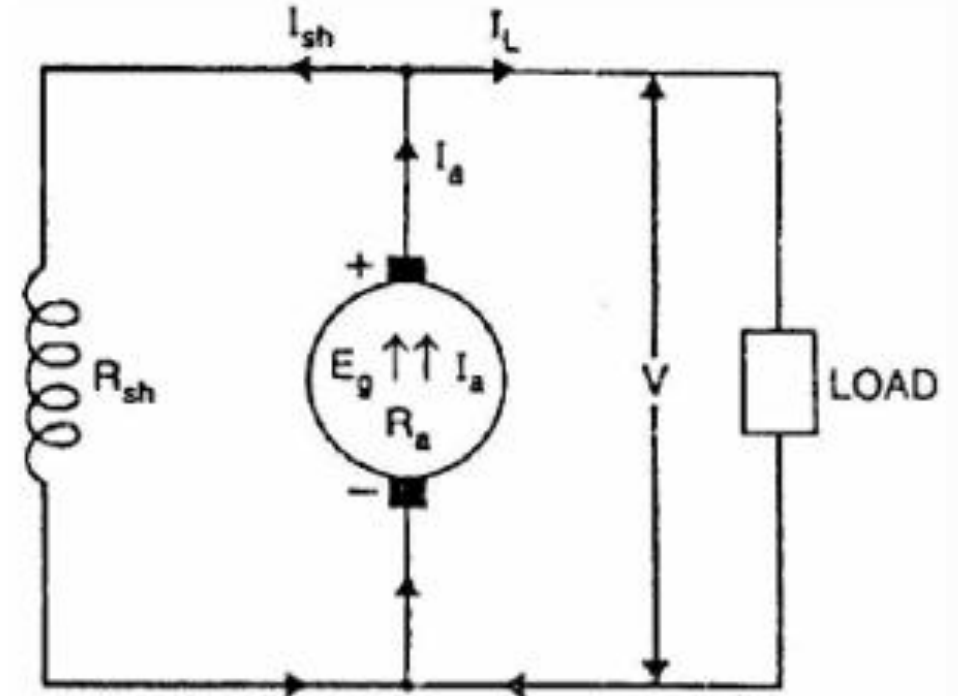
## Shunt Generator

- Shunt field current,  $I_{sh} = \frac{V}{R_{sh}}$
- Armature current,  $I_a = I_L + I_{sh}$
- Terminal voltage,  $V = E_g - I_a R_a$
- Power developed in armature =  $E_g I_a$
- Power delivered to load =  $V \cdot I_L$





# Compound Generator

- In a compound-wound generator, there are two sets of field windings on each pole—one is in series and the other in parallel with the armature.
- Short Shunt CG – Shunt field winding alone is in parallel with the armature winding.
- Long Shunt CG – series field and armature winding are connected in series. Shunt field winding is connected in parallel with them.



## Compound Generator

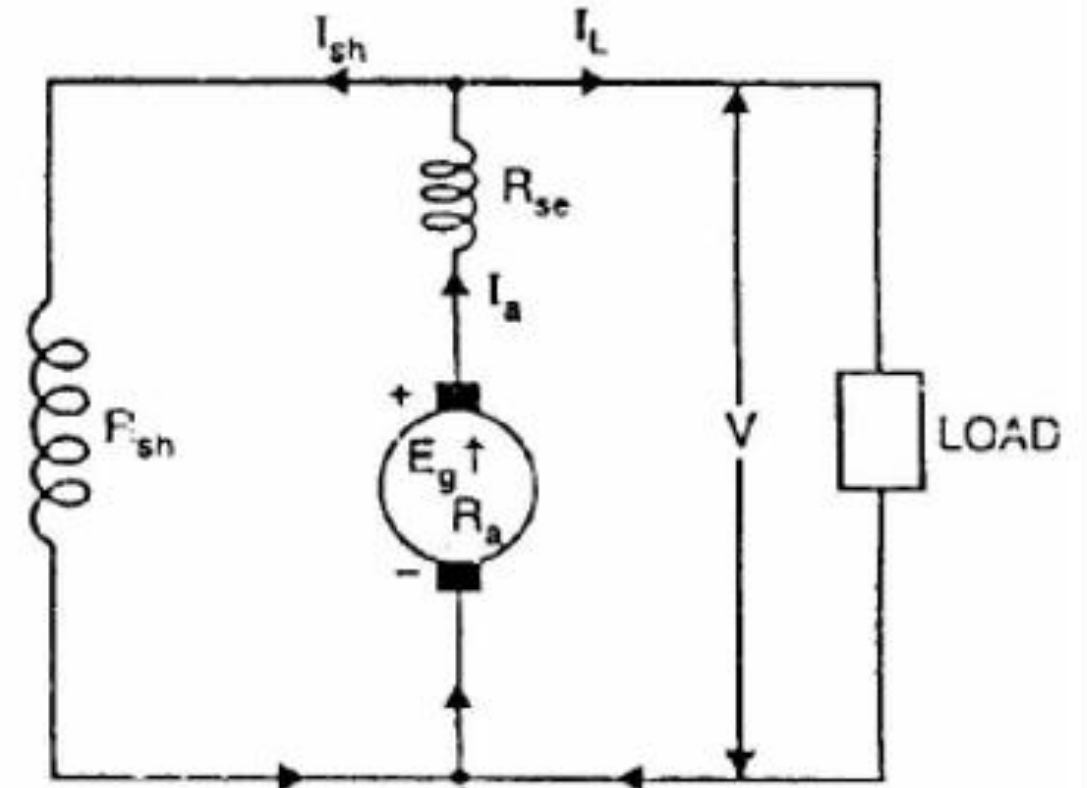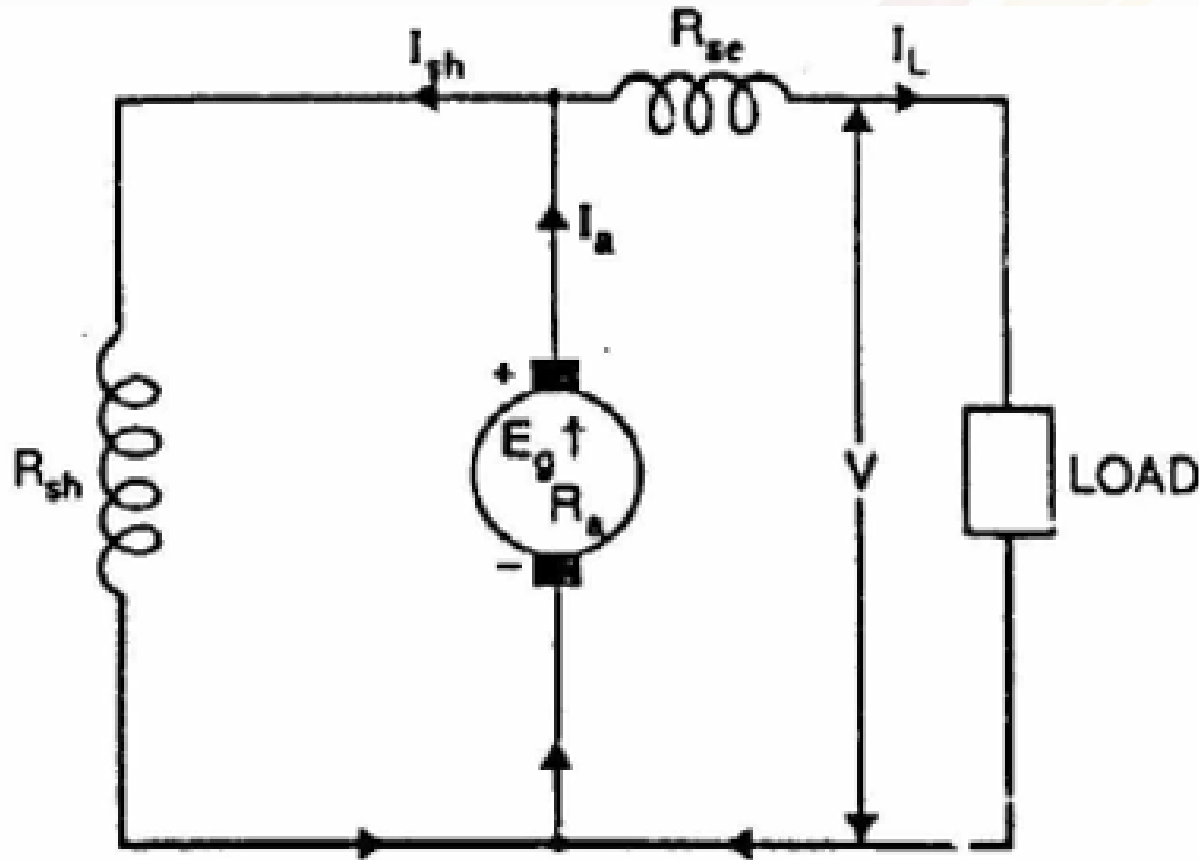

# Short Shunt Compound Generator


Series field current,  $I_{se} = I_L$

Shunt field current,  $I_{sh} = \frac{V + I_{se}R_{se}}{R_{sh}}$

Terminal voltage,  $V = E_g - I_a R_a - I_{se} R_{se}$

Power developed in armature =  $E_g I_a$

Power delivered to load =  $V \cdot I_L$

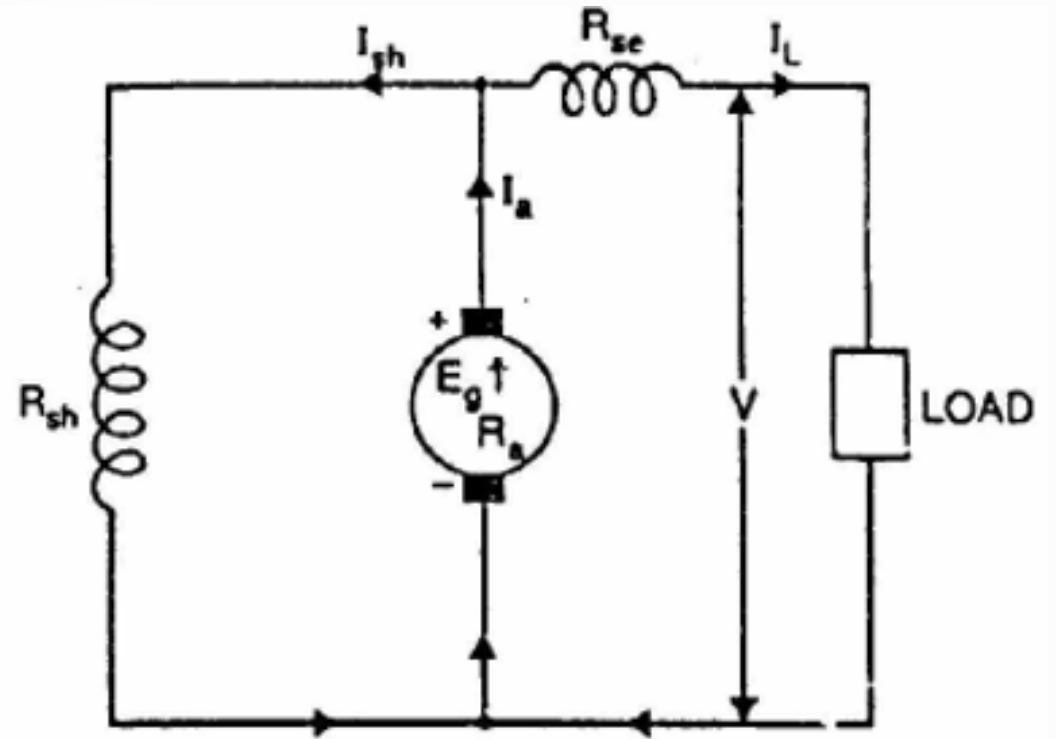

# Long Shunt Compound Generator


Series field current,  $I_{se} = I_a = I_L + I_{sh}$

$$\text{Shunt field current, } I_{sh} = \frac{V}{R_{sh}}$$

Terminal voltage,  $V = E_g - I_a(R_a + R_{se})$

Power developed in armature =  $E_g I_a$

Power delivered to load =  $V \cdot I_L$

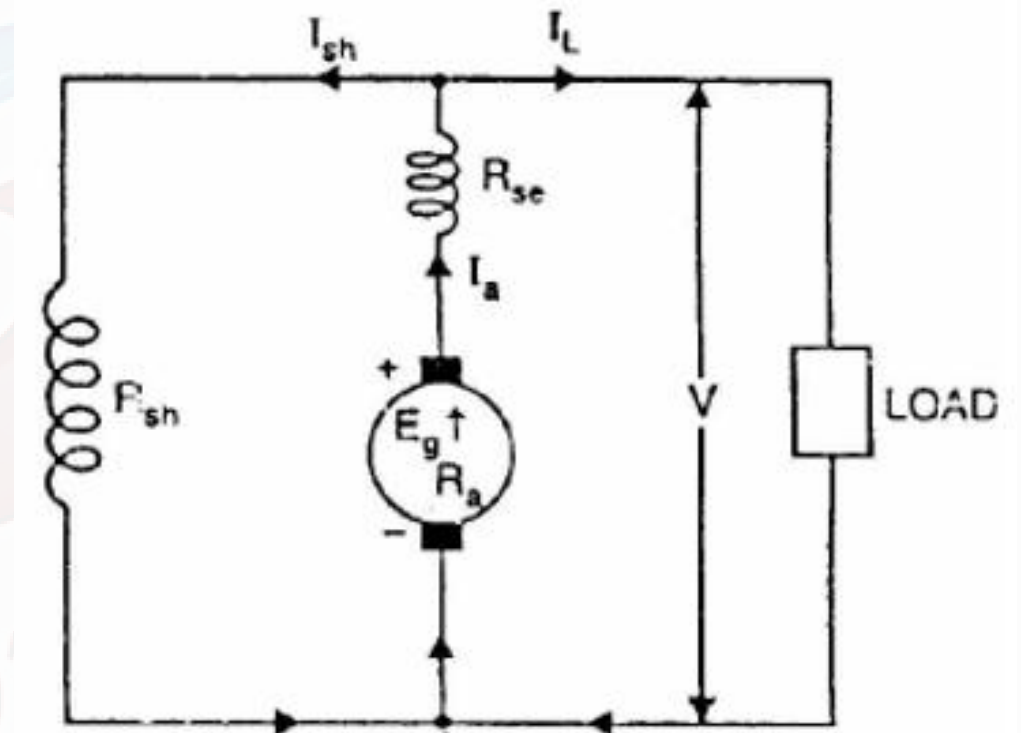


## D.C. Generator Characteristics

- The relation between excitation, terminal voltage and load can be understood graphically.
- These characteristics show the behaviour of the generator under different load conditions.
- The following are the three most important characteristics of a d.c. generator:
  - Open Circuit Characteristic (O.C.C.) –  $E_g$   $V_s$   $I_f$
  - Internal characteristics –  $E_g$   $V_s$   $I_a$
  - External characteristics –  $V_t$   $V_s$   $I_L$

# DC Generator Induced EMF and Classification

## Characteristics of a Separately Excited D.C. Generator


### ▪ Open Circuit Characteristics

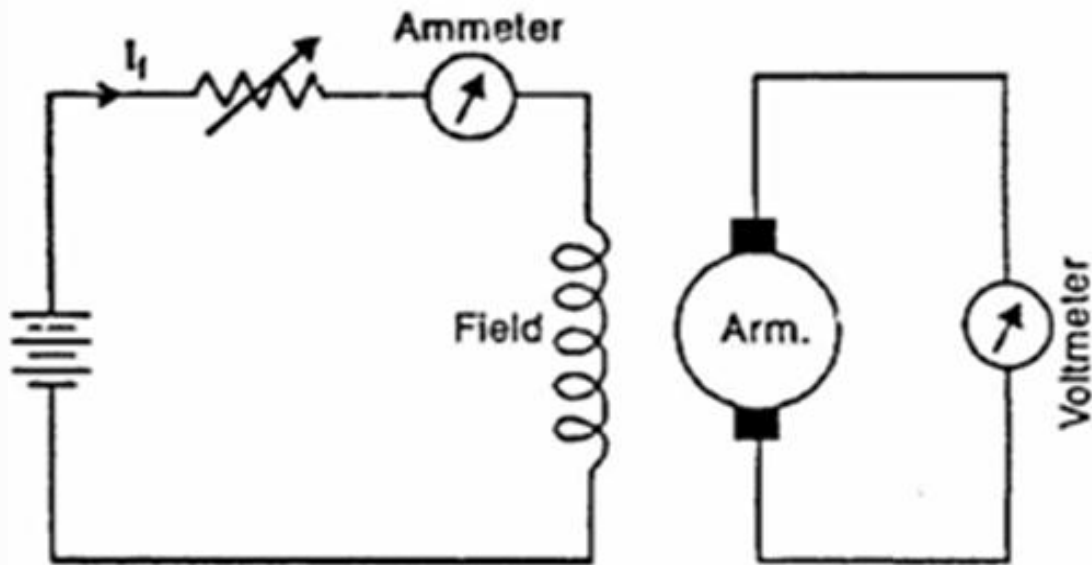

OA – Due to residual magnetism



AB –  $R_i$  is negligible and  $R_g$  is constant

BC – B is high. Hence  $R_i$  increases

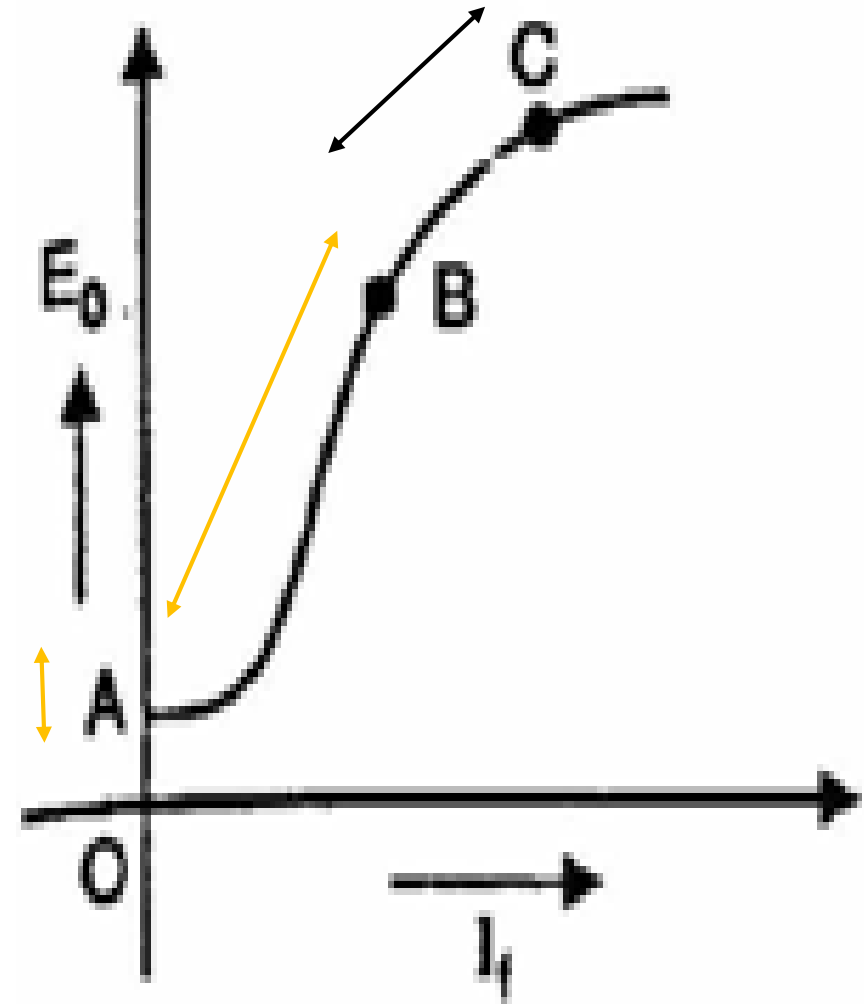

# DC Generator Induced EMF and Classification
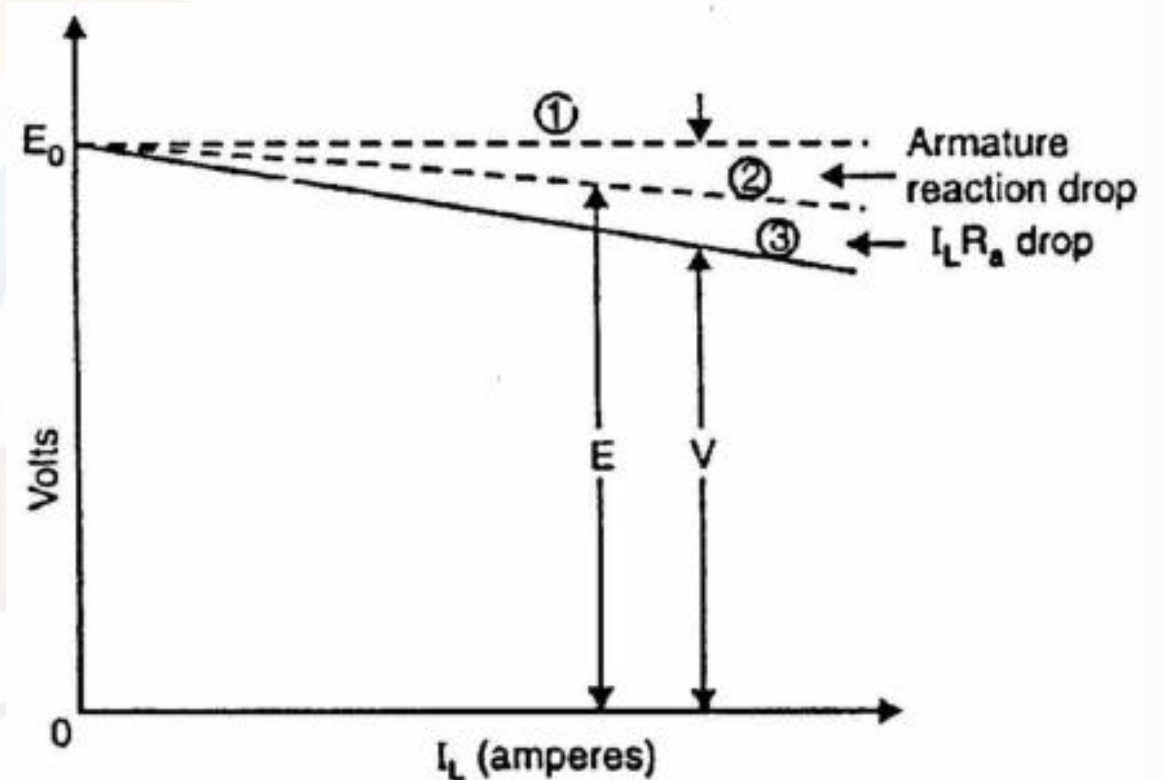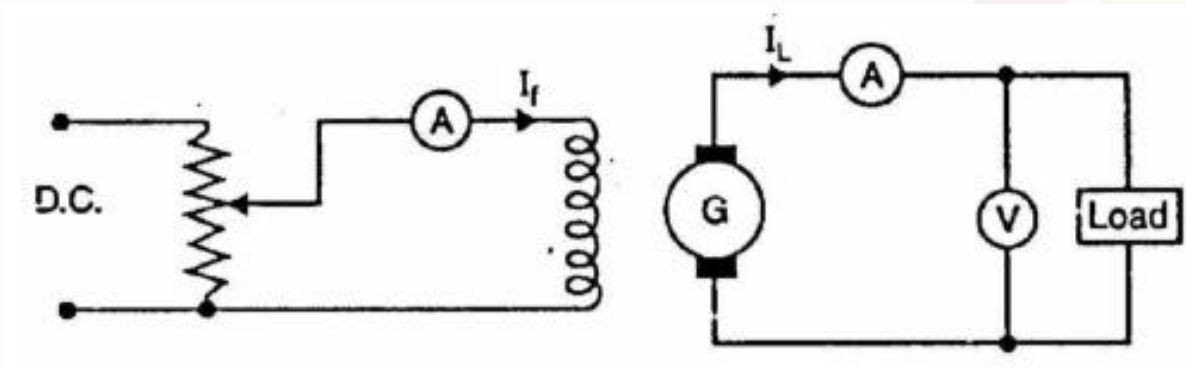
## Characteristics of a Separately Excited D.C. Generator Internal and External Characteristics





Terminal voltage falls due to

- ✓ Armature reaction
- ✓ Voltage drop in armature resistance

Hence drooping curve

## Characteristics of Series Generator

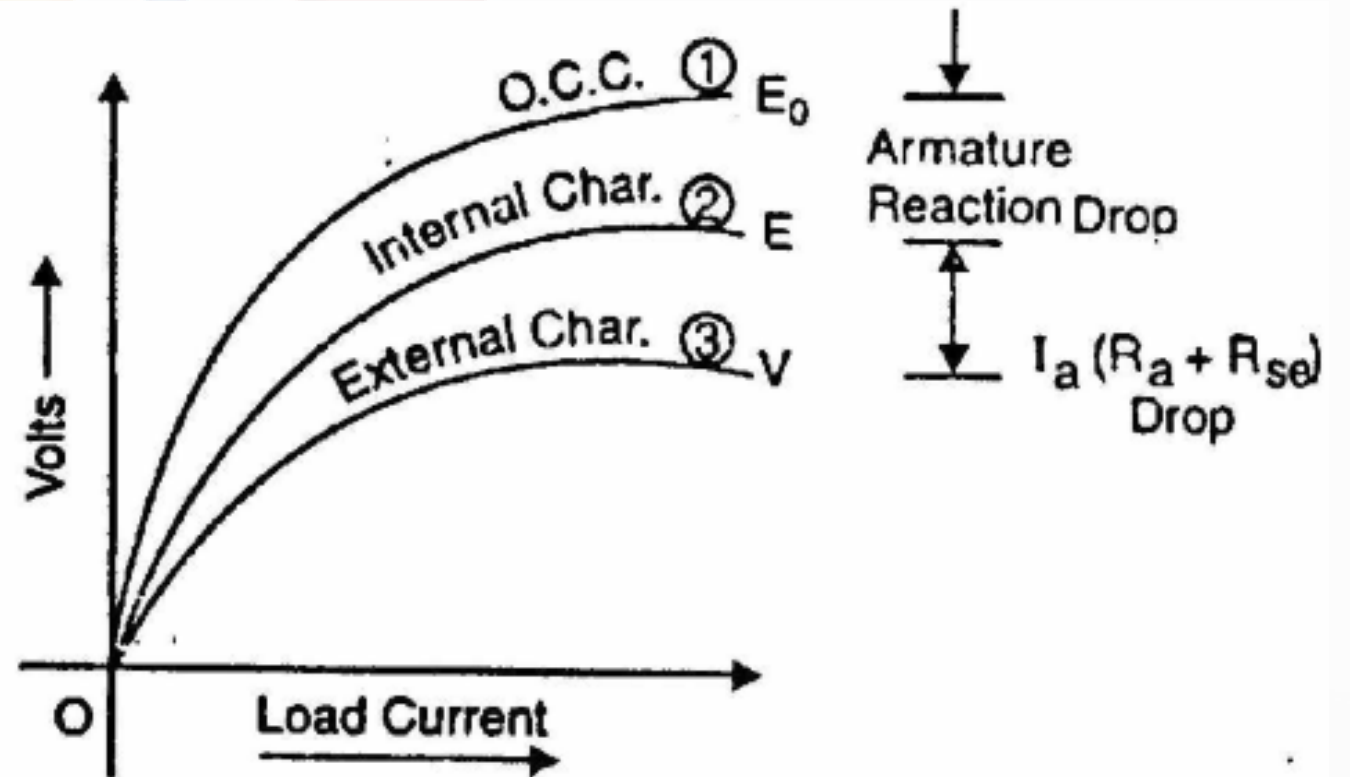
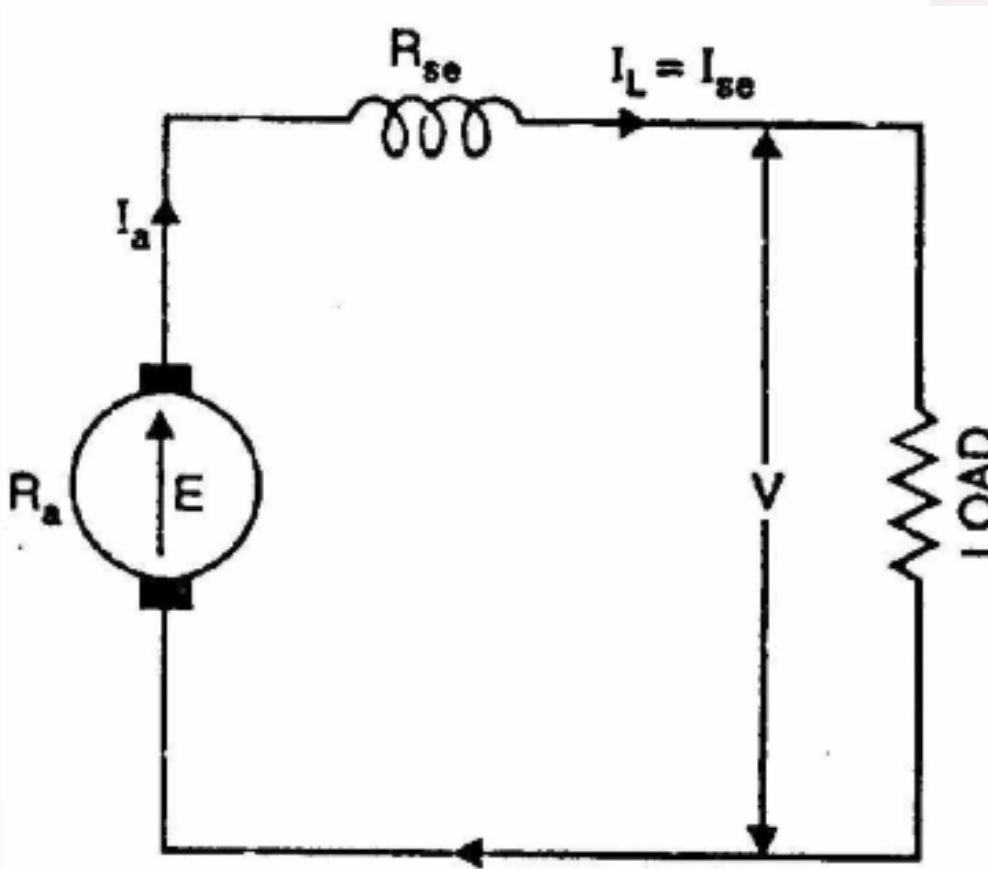






# DC Generator Induced EMF and Classification


## Characteristics of Compound Generator

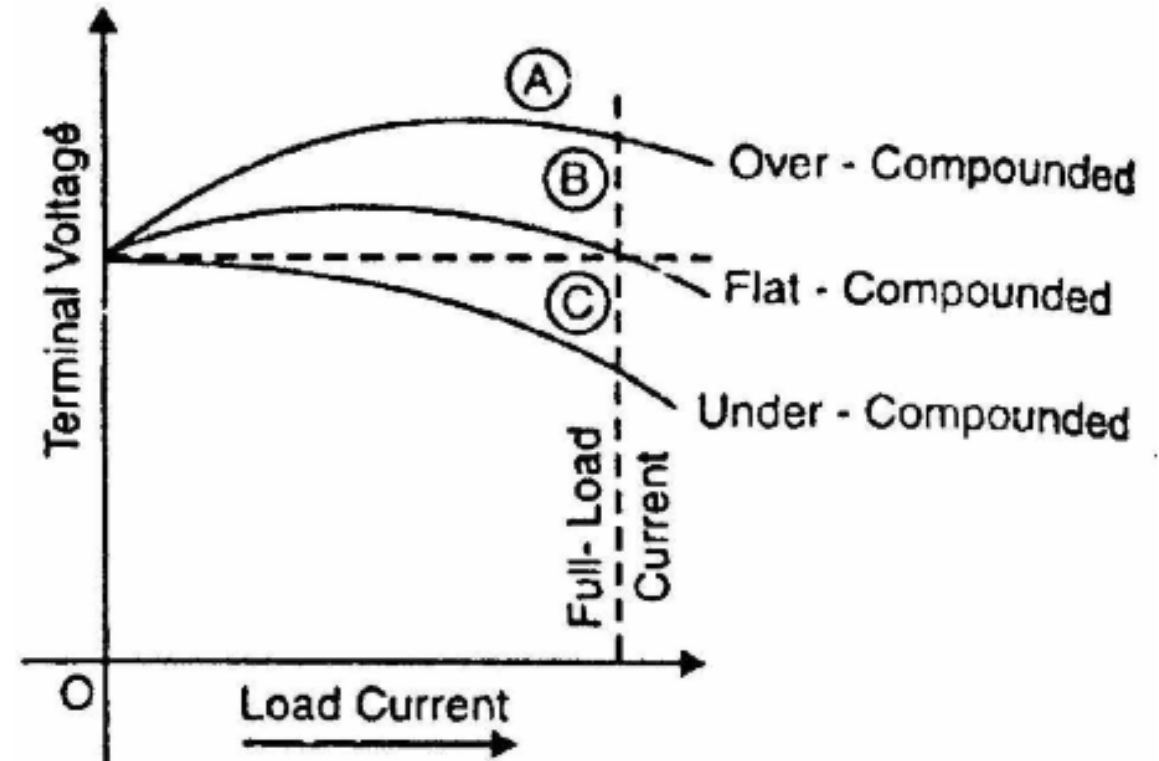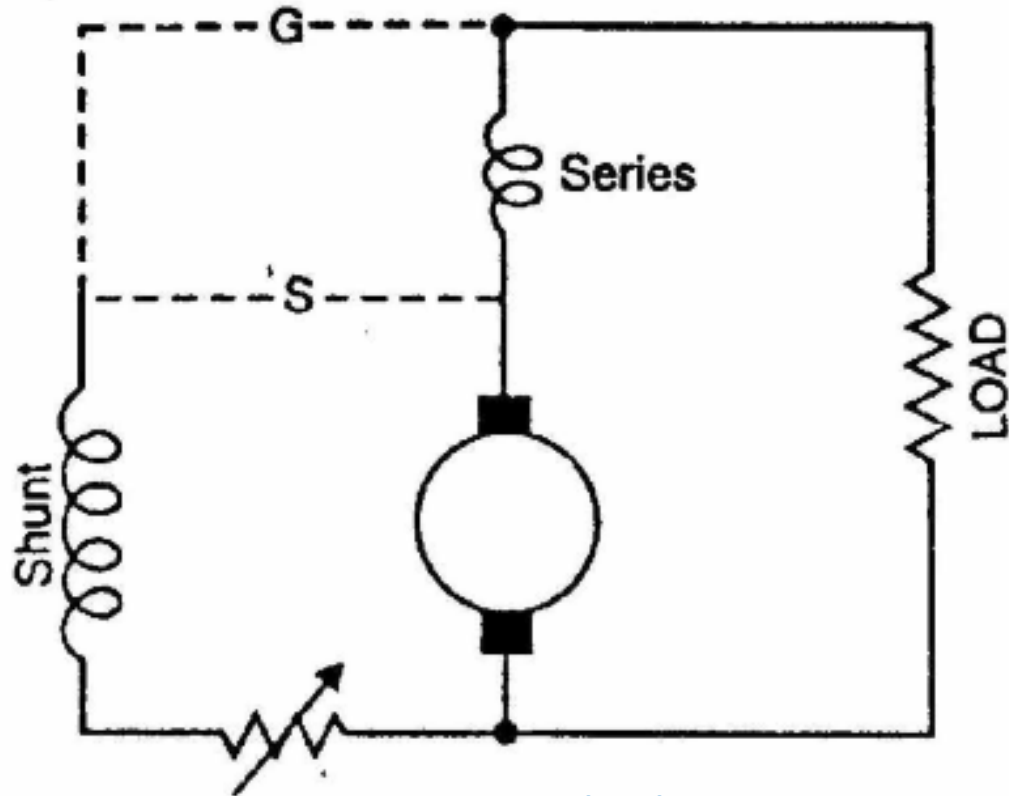

- Over compounded -  $V_t$  increases with increase in  $I_L$ .
- Flat compounded -  $V_t$  remains constant with increase in  $I_L$ .
- Under compounded -  $V_t$  decreases with increase in  $I_L$ .
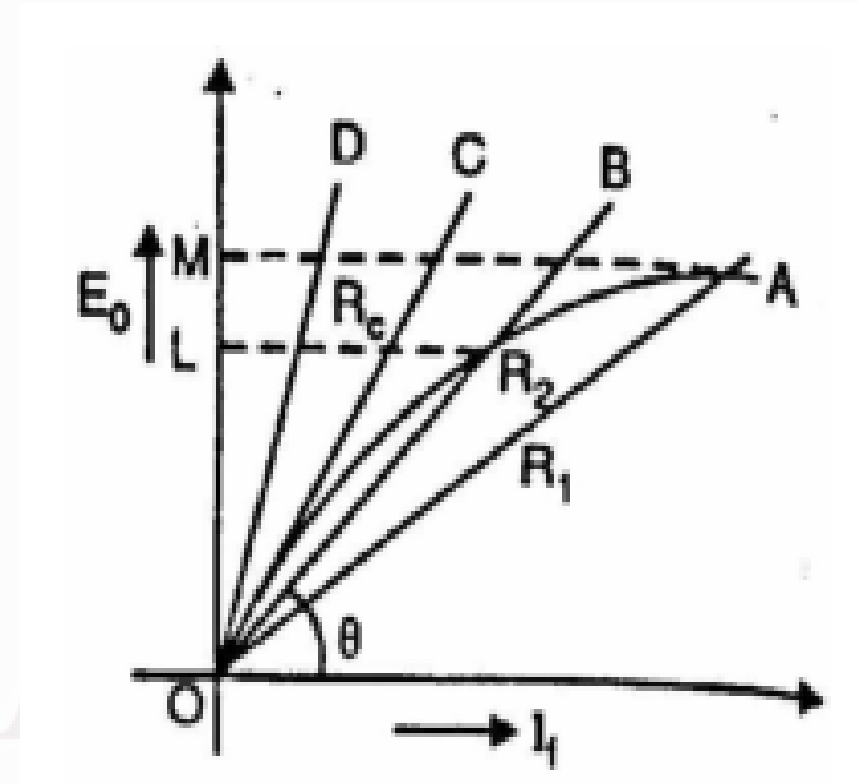
## Critical Field Resistance of Generator

- The maximum field circuit resistance with which the shunt generator would just excite is known as its critical field resistance.
- It should be noted that shunt generator will build up voltage only if field circuit resistance is less than critical field resistance.
- $R_f$  should be less than  $R_c$ .



## Critical Speed of Generator

- The minimum speed below which the generator fails to excite.
- It is the speed for which the given shunt field resistance represents the critical resistance.

GALGOTIAS  
UNIVERSITY

# DC Generator Induced EMF and Classification

## Summary

- Induced EMF
- Generating mode and motoring mode
- Methods of excitation
- Classification of DC machines

GALGOTIAS  
UNIVERSITY