

The logo of Galgotias University is a circular emblem with a stylized 'G' in the center. The 'G' is composed of several curved, overlapping bands in shades of yellow, orange, and blue. The background of the emblem is a light, textured grey.

# **Single-phase Transformer**

## **Losses and Test**

*Acknowledgement: The materials presented in this lecture has been taken from open source, reference books etc. This can be used only for student welfare and academic purpose.*

# Recap

- Transformer definition and its need
- Constructional details
- Its classifications and applications
- Its cooling
- Induced EMF in secondary and primary winding

GALGOTIAS  
UNIVERSITY

# Single-phase Transformer Losses and Test

## Lecture-5 Objectives

- Losses in the transformer
- Equivalent circuit of the transformer
- Testing of the transformer
- Example

GALGOTIAS  
UNIVERSITY

# Single-phase Transformer Losses and Test

## Losses in a Transformer

- The power losses in a transformer are of two types, namely;
  - Core or Iron losses
  - Copper losses

GALGOTIAS  
UNIVERSITY

# Single-phase Transformer Losses and Test

## Core or Iron losses ( $P_i$ )

- This loss consists of hysteresis and eddy current loss and occur in the transformer core due to the alternating flux.
- These losses can be determined by open-circuit test.

$$\text{Hysteresis loss, } P_h = K_h B_{\max}^{1.6} f v \text{ watts}$$

$$\text{Eddy current loss, } P_e = K_e B_{\max}^2 f^2 t^2 v \text{ watts}$$

- Both the above losses depend on  $B_m$  and frequency which are constant.
- Hence, core or iron losses are practically the same at all loads.

# Single-phase Transformer Losses and Test

## Copper losses ( $P_C$ )

- These losses occur in both the primary and secondary windings due to their ohmic resistance.
- These losses can be determined by short-circuit test.

$$P_C = I_1^2 R_1 + I_2^2 R_2 = I_1^2 R_{01} = I_2^2 R_{02}$$

- Copper losses vary as the square of load current.
- Copper losses account for about 90% of the total losses.

# Single-phase Transformer Losses and Test

## Summary

### Core loss

- ✓ It is the Constant loss
- ✓ Does not change even as the load current changes
- ✓ Proportional to supply voltage and frequency

### Copper loss or $I^2R$ loss

- ✓ It is a variable loss
- ✓ Also called as  $I^2R$  loss
- ✓ Proportional to square of the load current
- ✓ Occurs in the winding resistances
- ✓ It is dissipated as heat

GALGOTIAS  
UNIVERSITY

# Single-phase Transformer Losses and Test

## Impedance Ratio


$$Z_2 = \frac{V_2}{I_2}$$

$$Z_1 = \frac{V_1}{I_1}$$

$$\therefore \frac{Z_2}{Z_1} = \left( \frac{V_2}{V_1} \right) \times \left( \frac{I_1}{I_2} \right)$$

$$\frac{Z_2}{Z_1} = K^2$$

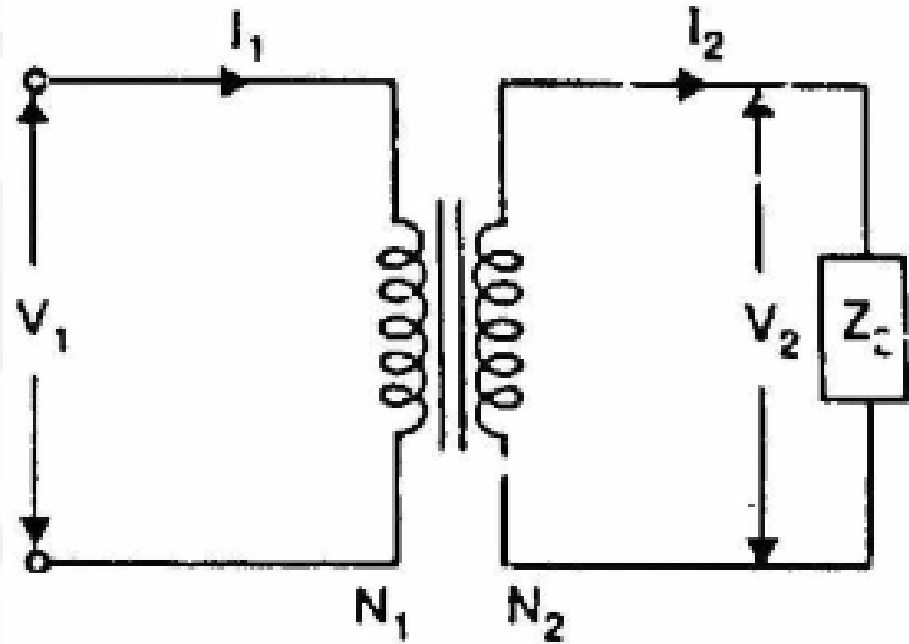
Similarly,  $\frac{R_2}{R_1} = K^2$        $\frac{X_2}{X_1} = K^2$





# Single-phase Transformer Losses and Test


## Shifting Impedances

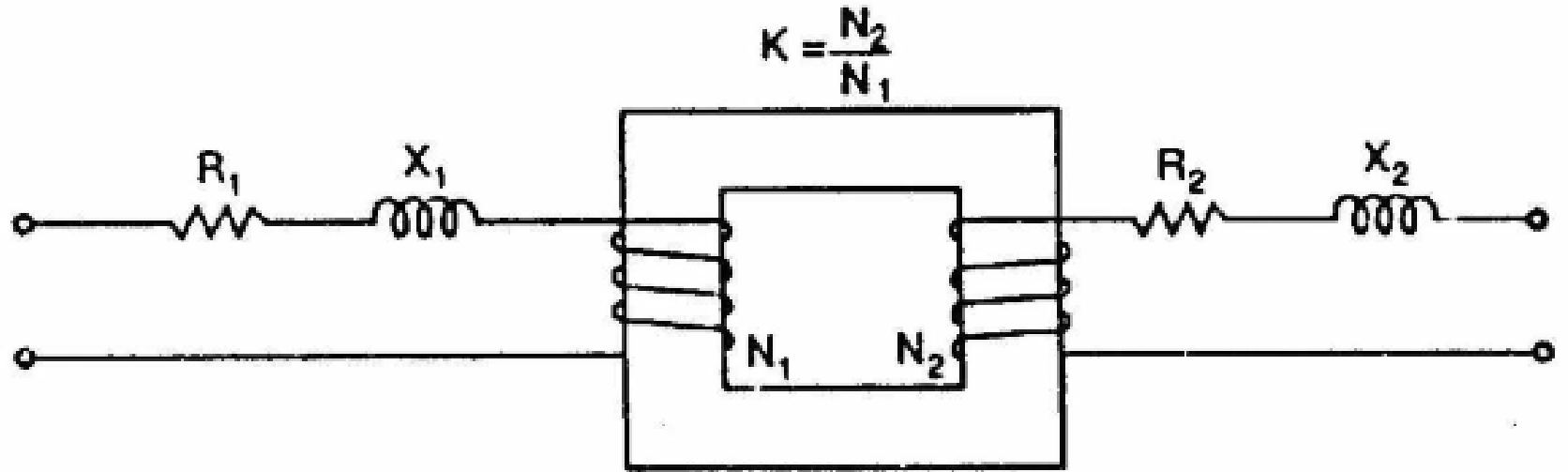

- When transferring resistance or reactance from primary to secondary, multiply it by  $K^2$ .
- When transferring resistance or reactance from secondary to primary, divide it by  $K^2$ .


# Single-phase Transformer Losses and Test

## Equivalent Circuit of a Transformer

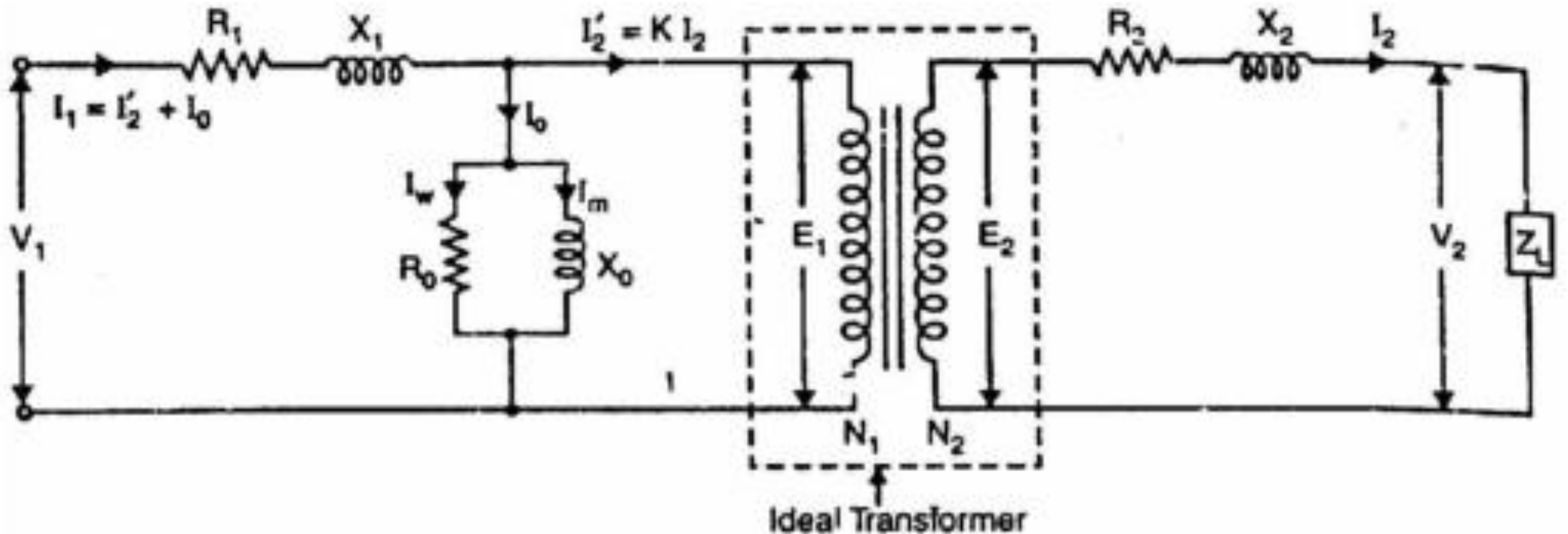


# Single-phase Transformer Losses and Test
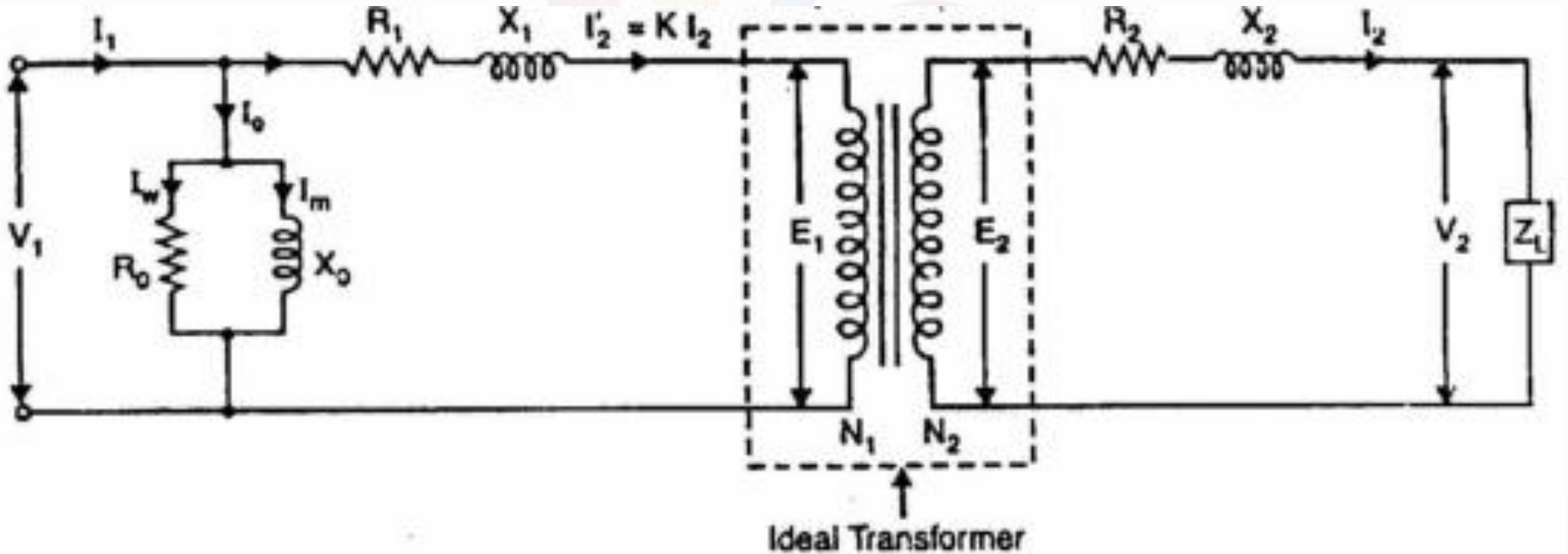
## Simplified Equivalent Circuit of a Transformer



# Single-phase Transformer Losses and Test

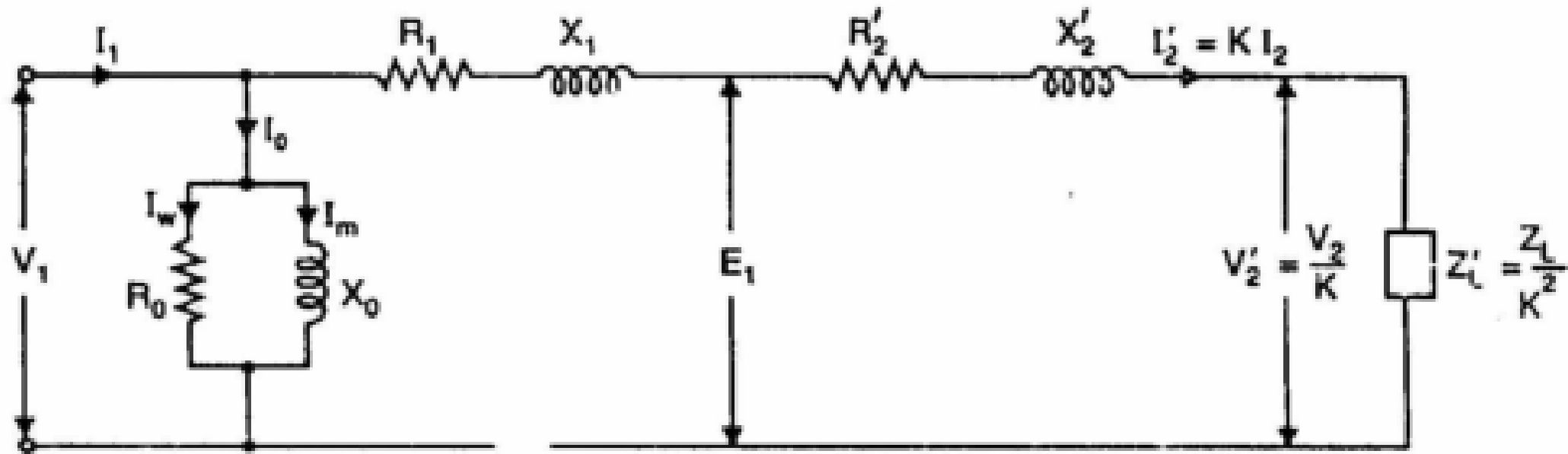
## Equivalent Circuit Referred to Primary Side



$$R'_2 = \frac{R_2}{K^2}; \quad X'_2 = \frac{X_2}{K^2}; \quad Z'_L = \frac{Z_L}{K^2}; \quad V'_2 = \frac{V_2}{K}; \quad I'_2 = K I_2$$

# Single-phase Transformer Losses and Test
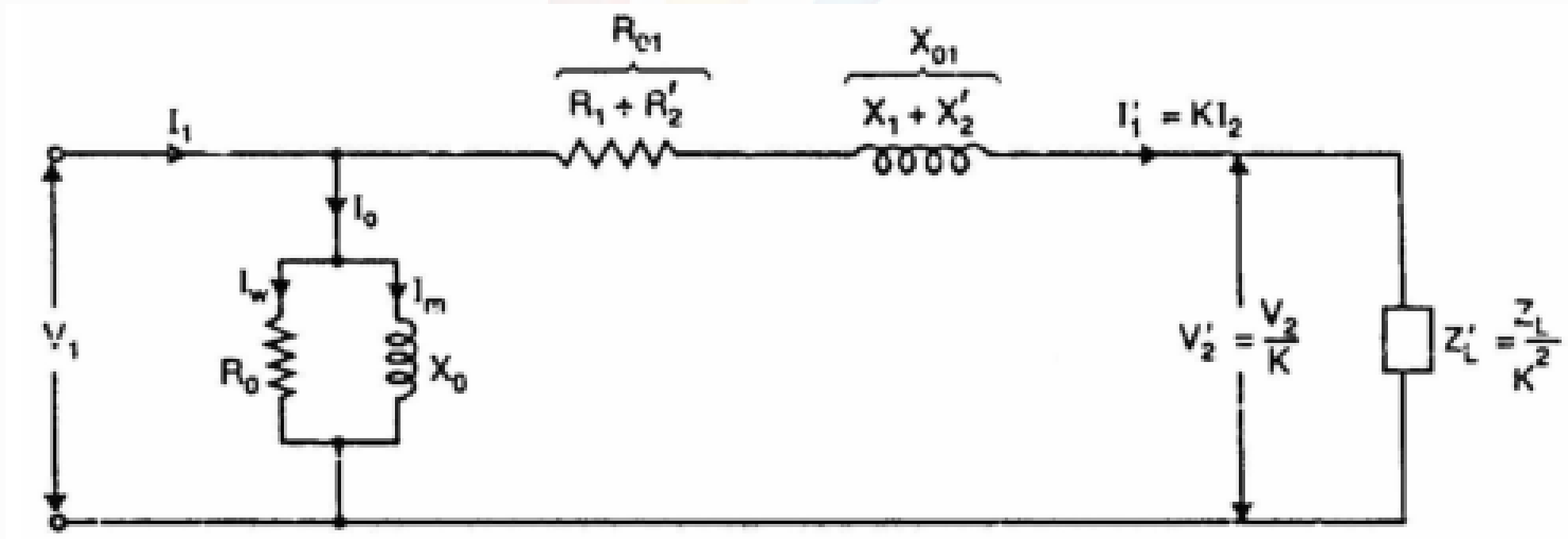
## Equivalent Circuit Referred to Primary Side




$$R_{01} = R_1 + R'_2;$$

$$X_{01} = X_1 + X'_2$$

# Single-phase Transformer Losses and Test
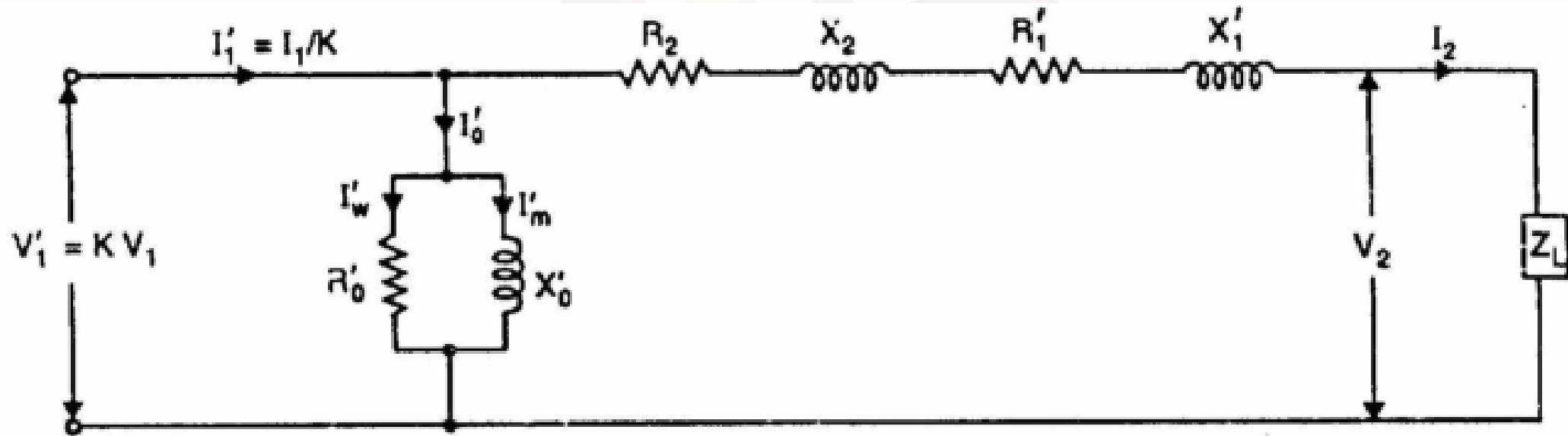
## Equivalent Circuit Referred to Secondary Side




$$R'_1 = K^2 R_1;$$

$$X'_1 = K^2 X_1;$$

$$V'_2 = K V_1; \quad I'_1 = \frac{I_1}{K}$$

# Single-phase Transformer Losses and Test
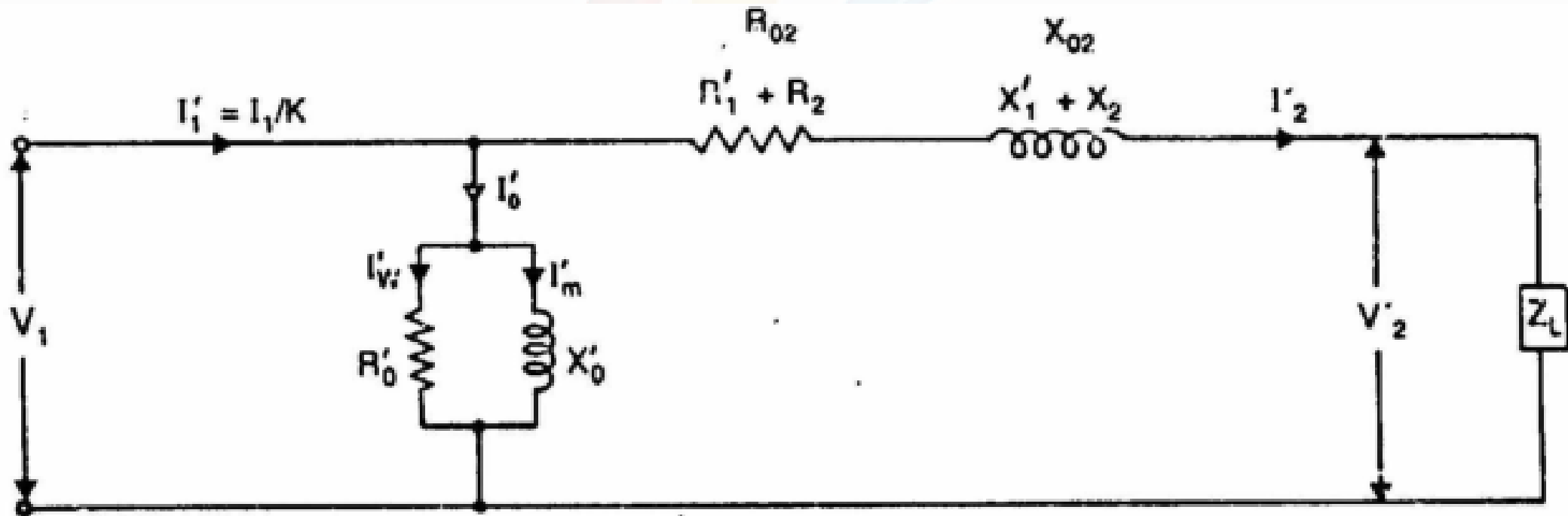
## Equivalent Circuit Referred to Secondary Side



$$R_{02} = R_2 + R'_1;$$

$$X_{02} = X_2 + X'_1$$

# Single-phase Transformer Losses and Test

## Testing of Transformers

- The circuit constants, efficiency and voltage regulation of a transformer can be determined by two simple tests.
  - (i) Open-circuit test
  - (ii) Short-circuit test


GALGOTIAS  
UNIVERSITY



# Single-phase Transformer Losses and Test
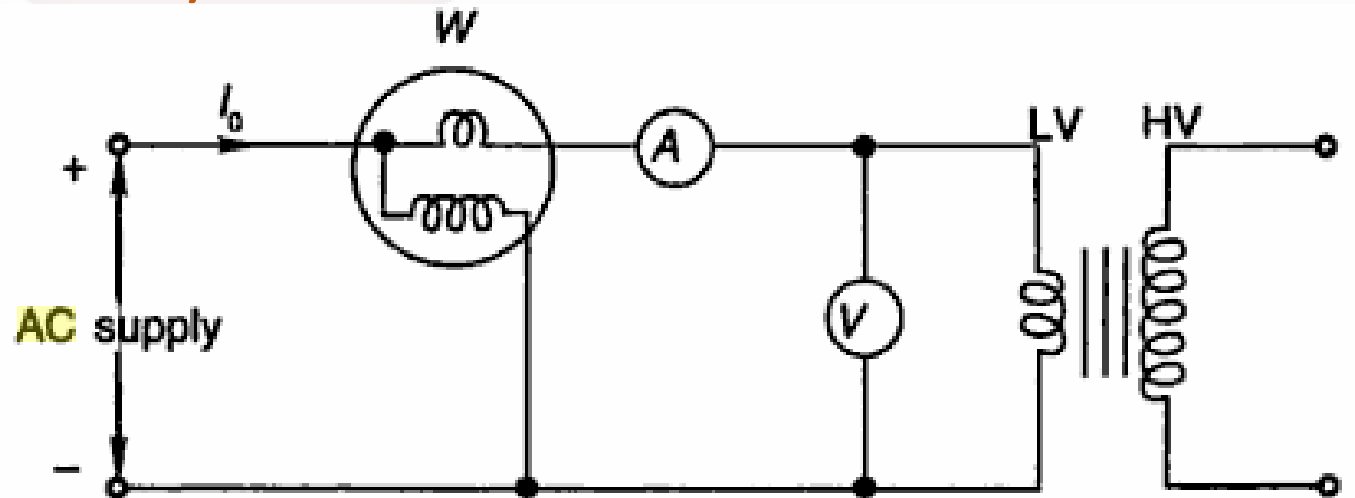
## Open Circuit Test

- This test is conducted to determine  $R_0$  &  $X_0$
- Rated voltage is applied on LV side & HV side is kept open.
- At no load, current taken by the transformer is 3-5% of full load current. So  $I^2R$  loss is negligible.
- Therefore power consumed by the transformer on no load is considered as core loss.



# Single-phase Transformer Losses and Test

## Data observed from the test

- Supply voltage =  $V_0$  volts
- No load current =  $I_0$  amps
- Iron losses =  $W_0$  watts

$$W_0 = V_0 I_0 \cos \Phi_0$$

$$\cos \Phi_0 = W_0 / (V_0 I_0)$$

$$I_w = I_0 \cos \Phi_0$$

$$I_m = I_0 \sin \Phi_0$$

$$R_0 = V_1 / I_w$$


$$X_0 = V_1 / I_m$$

GALGOTIAS  
UNIVERSITY

# Single-phase Transformer Losses and Test
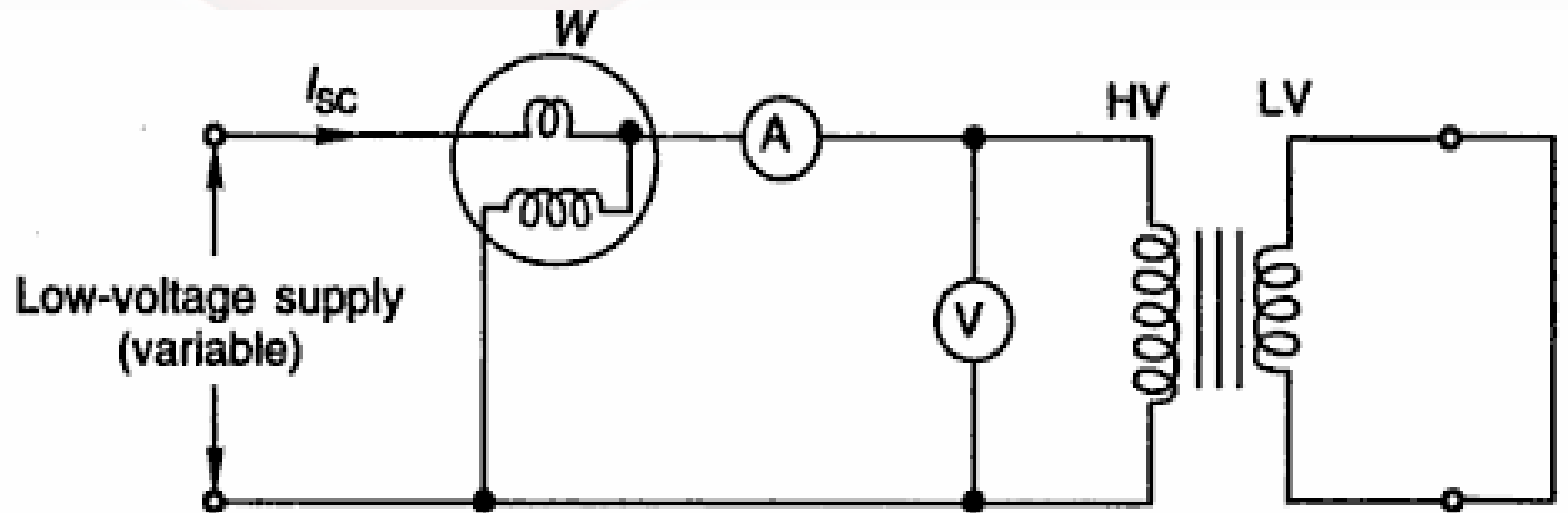
## Short Circuit Test

- This test is conducted to determine  $R_{02}$  &  $X_{02}$
- LV side of the Tfr is short circuited & the test is conducted on HV side.
- A low voltage is applied on the HV side to circulate the rated current on both the windings.
- Power drawn during this test is considered as copper loss.



# Single-phase Transformer Losses and Test

## Data observed from the test

- Applied voltage =  $V_{sc}$  volts
- Short circuit current =  $I_{sc}$  amps
- Copper losses =  $W_{sc}$  watts

$$W_{sc} = I_{sc}^2 R_{02}$$

$$R_{02} = W_{sc} / I_{sc}^2$$

$$Z_{02} = V_{sc} / I_{sc}$$

$$X_{02} = [Z_{02}^2 - R_{02}^2]^{1/2}$$

GALGOTIAS  
UNIVERSITY

# Single-phase Transformer Losses and Test

Obtain the equivalent circuit of a 200 / 400 V, 50 Hz, 1 phase transformer from the following test data:

O.C. test: 200 V, 0.7 A, 70 W – on L.V side.

S.C. test: 15 V, 10 A, 85 W – on H.V side.

Calculate the secondary voltage when delivering 5 kW at 0.8 p.f lagging, the primary voltage being 200 V.

CALCOTIAS  
UNIVERSITY

# Single-phase Transformer Losses and Test

## From OC Test

$$P_0 = V_0 I_0 \cos \phi_0$$

$$\cos \phi_0 = \frac{P_0}{V_0 I_0} = \frac{70}{200 \times 0.7}$$

$$\cos \phi_0 = 0.5$$

$$\sin \phi_0 = 0.866$$

$$I_w = I_0 \cos \phi_0 = 0.7 \times 0.5 = 0.35A$$

$$I_m = I_0 \sin \phi_0 = 0.7 \times 0.866 = 0.606A$$

$$R_0 = \frac{V_0}{I_w} = \frac{70}{0.35} = 200 \Omega$$

$$X_0 = \frac{V_0}{I_m} = \frac{70}{0.606} = 115.5 \Omega$$

## From SC Test

$$P_{sc} = I_{sc}^2 R_{02}$$

$$R_{02} = \frac{P_{sc}}{I_{sc}^2} = \frac{85}{10^2} = 0.85 \Omega$$

$$Z_{02} = \frac{V_{sc}}{I_{sc}} = \frac{15}{10} = 1.5 \Omega$$

$$X_{02} = \sqrt{(Z_{02}^2 - R_{02}^2)}$$

$$X_{02} = \sqrt{(1.5^2 - 0.85^2)}$$

$$X_{02} = 1.235 \Omega$$


# Single-phase Transformer Losses and Test

## Equivalent Circuit Referred to Primary Side

$$K = \frac{400}{200} = 2$$

$$R_{01} = \frac{0.85}{2^2} = 0.212 \Omega$$
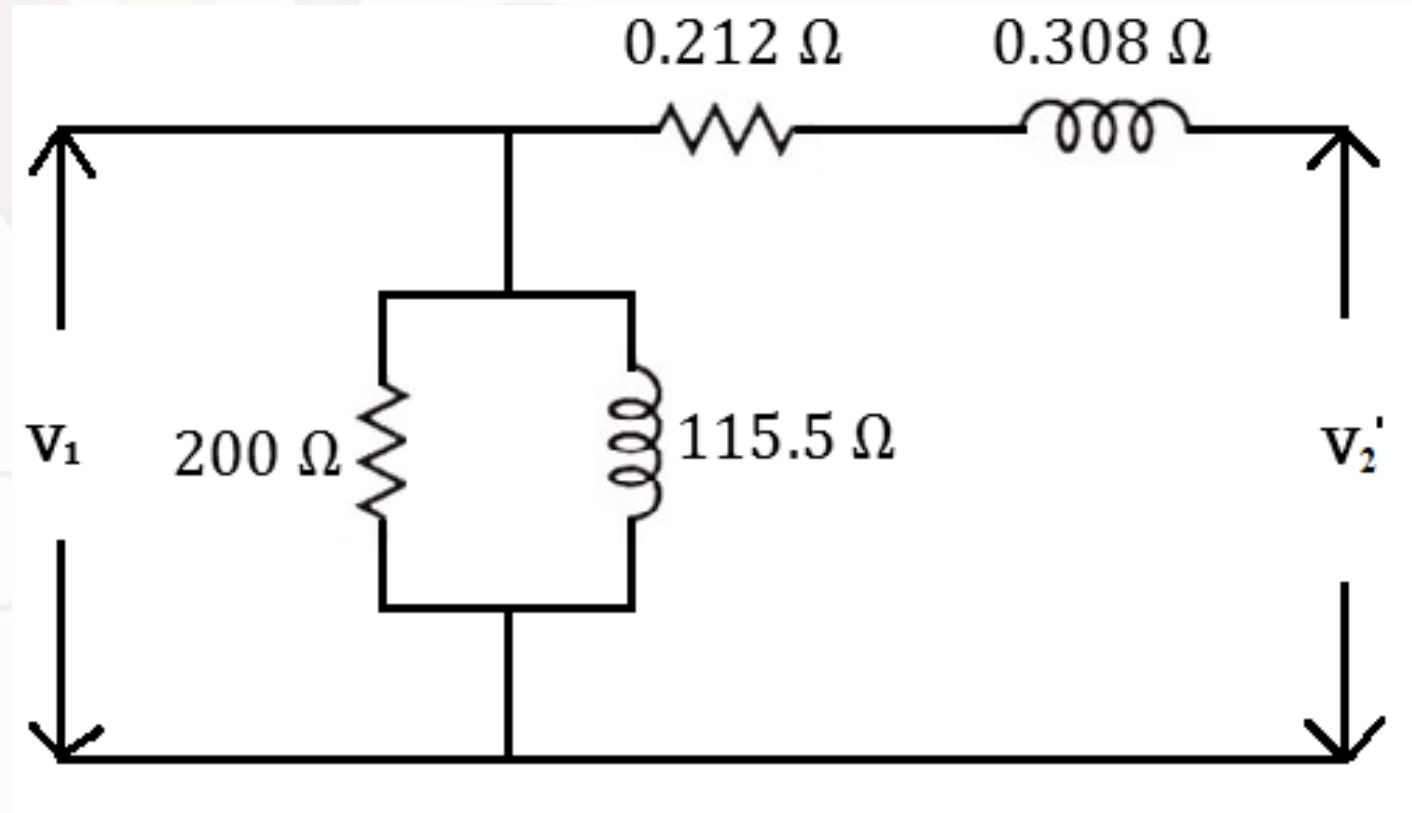
$$X_{01} = \frac{1.235}{2^2} = 0.308 \Omega$$




# Single-phase Transformer Losses and Test

## Equivalent Circuit Referred to Secondary Side

$$K = \frac{400}{200} = 2$$

$$R'_0 = 200 \times 2^2 = 800 \Omega$$

$$X'_0 = 115.5 \times 2^2 = 462 \Omega$$

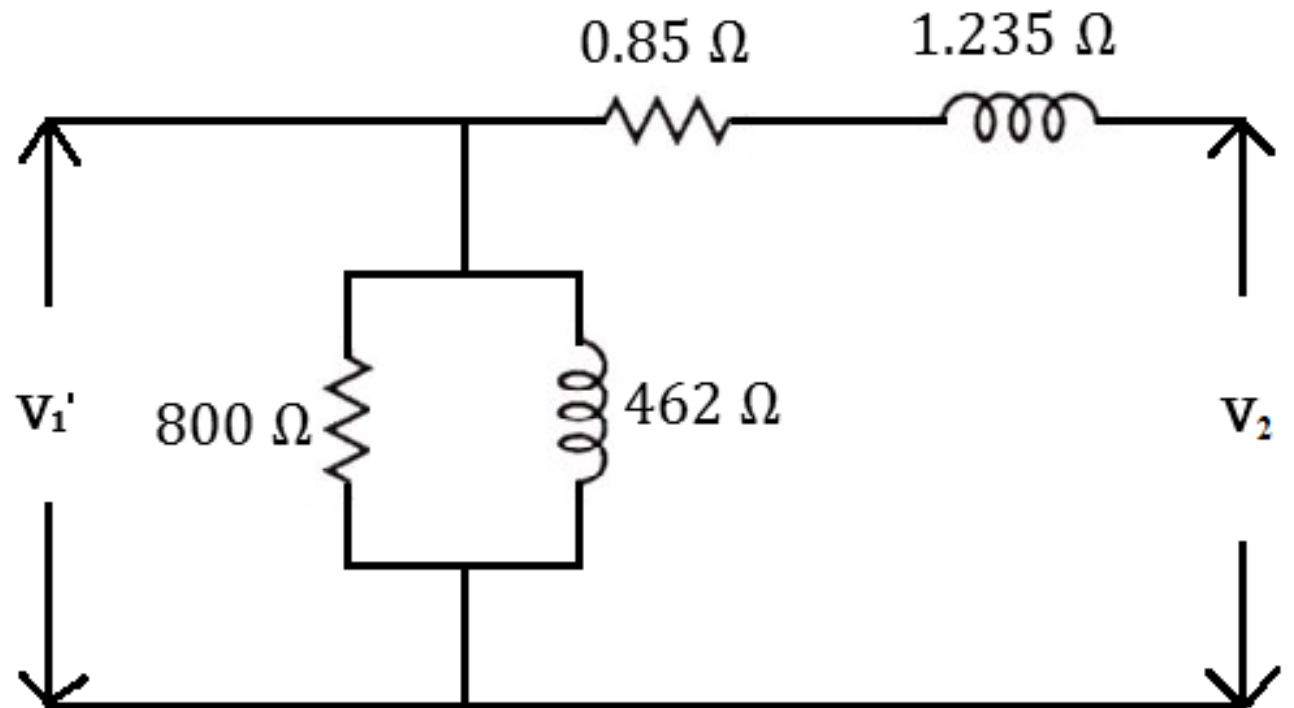



# Single-phase Transformer Losses and Test

- Load kVA corresponding to 5 kW is,

$$= \frac{5000}{0.8} = 6250 \text{ VA}$$

- Load current  $I_2$  while delivering 6250 VA is,

$$= \frac{6250}{400} = 15.625 \text{ A}$$

- Total voltage drop in secondary when it carries 15.625 A is,

$$\begin{aligned} &= I_2(R_{02} \cos \phi_2 + X_{02} \sin \phi_2) \\ &= 15.625(0.85 \times 0.8 + 1.235 \times 0.6) \\ &= 22.20 \text{ V} \end{aligned}$$

- Hence the secondary voltage is,

$$V_2 = 400 - 22.2 = 377.8 \text{ V}$$

# Single-phase Transformer Losses and Test

## Summary

- Losses in the transformer
- Equivalent circuit of the transformer
- Testing of the transformer
- Example



GALGOTIAS  
UNIVERSITY