

# **BTEE3011-Power Electronics**



## **CYCLOCONVERTERS**

**GALGOTIAS**  
**UNIVERSITY**

*Mr. Saravanan D, AP/SEECE, GU*


# Content

- ✓ Single phase cycloconverter
- ✓ Three-phase to single-phase cycloconverters
- ✓ Three-phase to three-phase cycloconverter
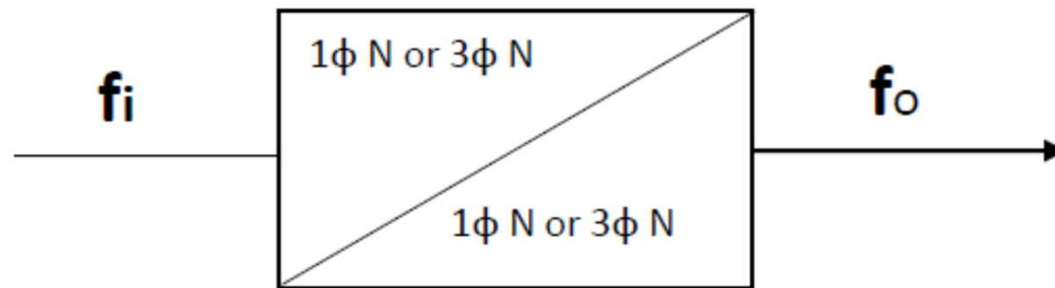
# Cycloconverter

A cycloconverter is a direct-frequency changer that converts ac power at one frequency to ac power at another frequency by ac-ac conversion.


Cycloconverters are used in high power applications driving synchronous and induction motor. They are usually phase controlled and they use thyristors due to their ease of natural (phase) commutation.




Cycloconverter Fig.1
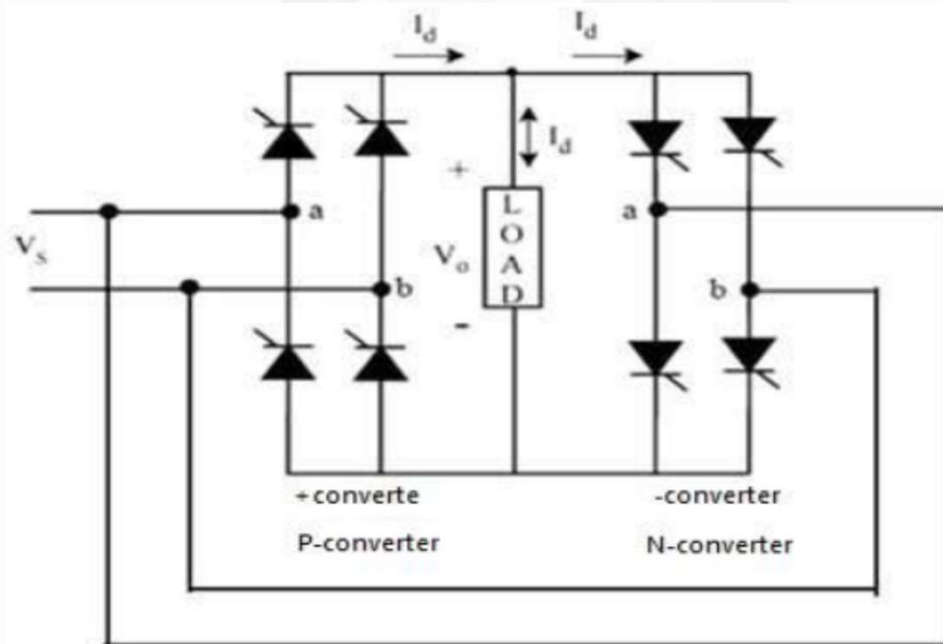
# Single phase cycloconverter

This converter consists of back to back connection of two full-wave bridge rectifier circuits.



# Contd....

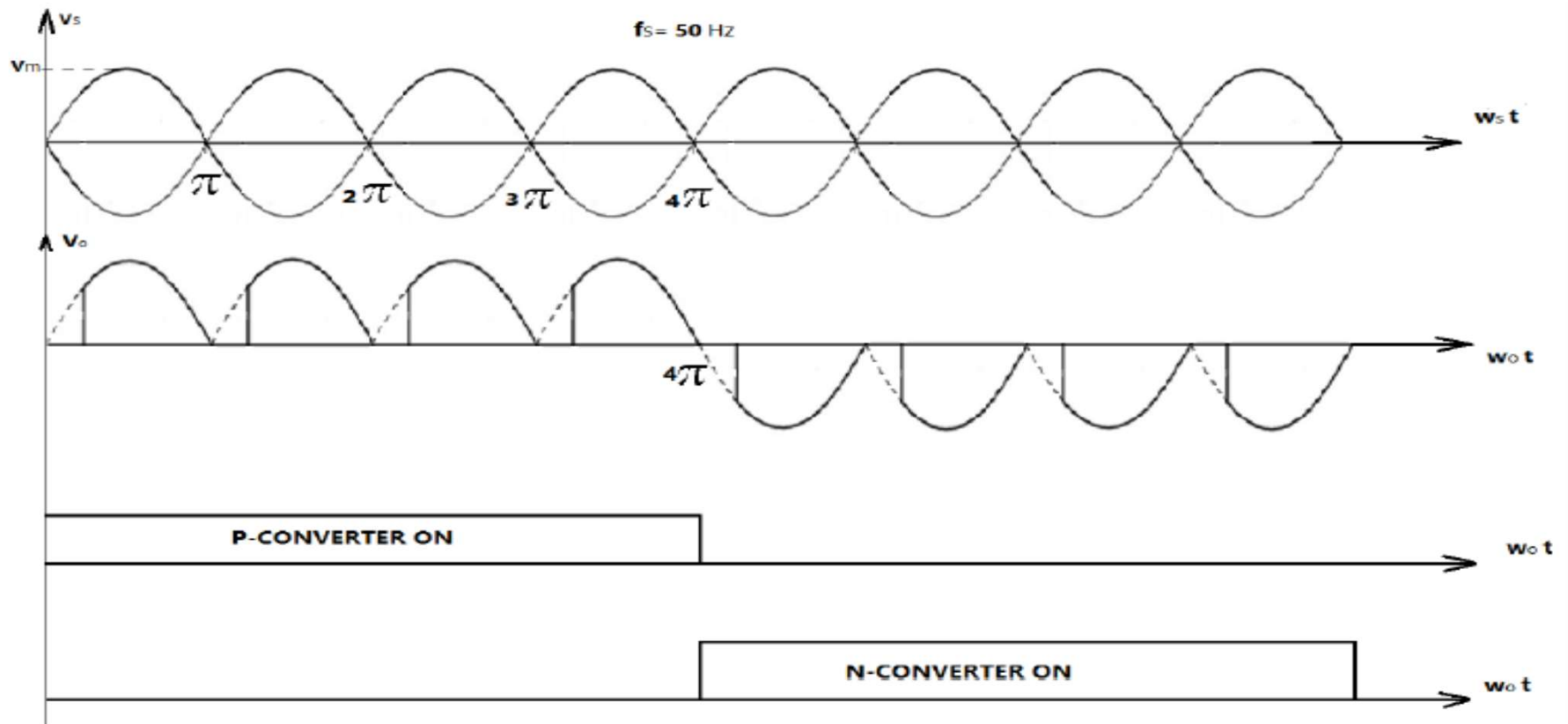

## Contd.....


If input voltage is

$$v_s = V_m \sin \omega_s t$$

The r.m.s output voltage can be found from:

$$\begin{aligned} V_o &= \left\{ \frac{8}{8\pi} \int_{\alpha_p}^{\pi} (\sqrt{2} V_s \sin \omega_s t)^2 d\omega t \right\}^{\frac{1}{2}} \\ &= \left\{ \frac{16V_s^2}{16\pi} \int_{\alpha_p}^{\pi} (1 - \cos 2\omega_s t) d\omega t \right\}^{\frac{1}{2}} \\ &= V_s \left[ \frac{1}{\pi} \left( \pi - \alpha_p + \frac{\sin 2\alpha_p}{2} \right) \right]^{\frac{1}{2}} \end{aligned}$$

Contd.....

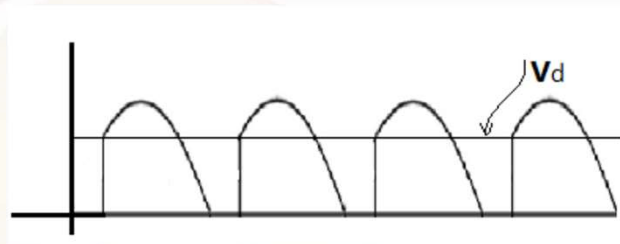

The average output voltage of p-converter alone is given by

$$V_{d1} = \frac{2V_m}{\pi} \cos \alpha$$

GALGOTIAS  
UNIVERSITY

# Three-phase to single-phase cycloconverter

When p-converter operating alone, positive voltage (k) appears across the load, and when N-converter operating alone, negative voltage (L) appears across the load.


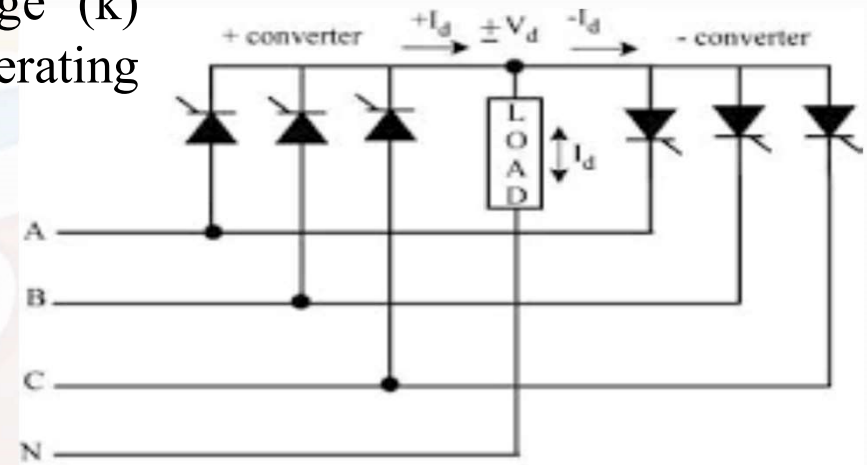


Fig. 4 3 $\phi$ -1 $\phi$  half-wave cycloconverter

GALGOTIAS  
UNIVERSITY

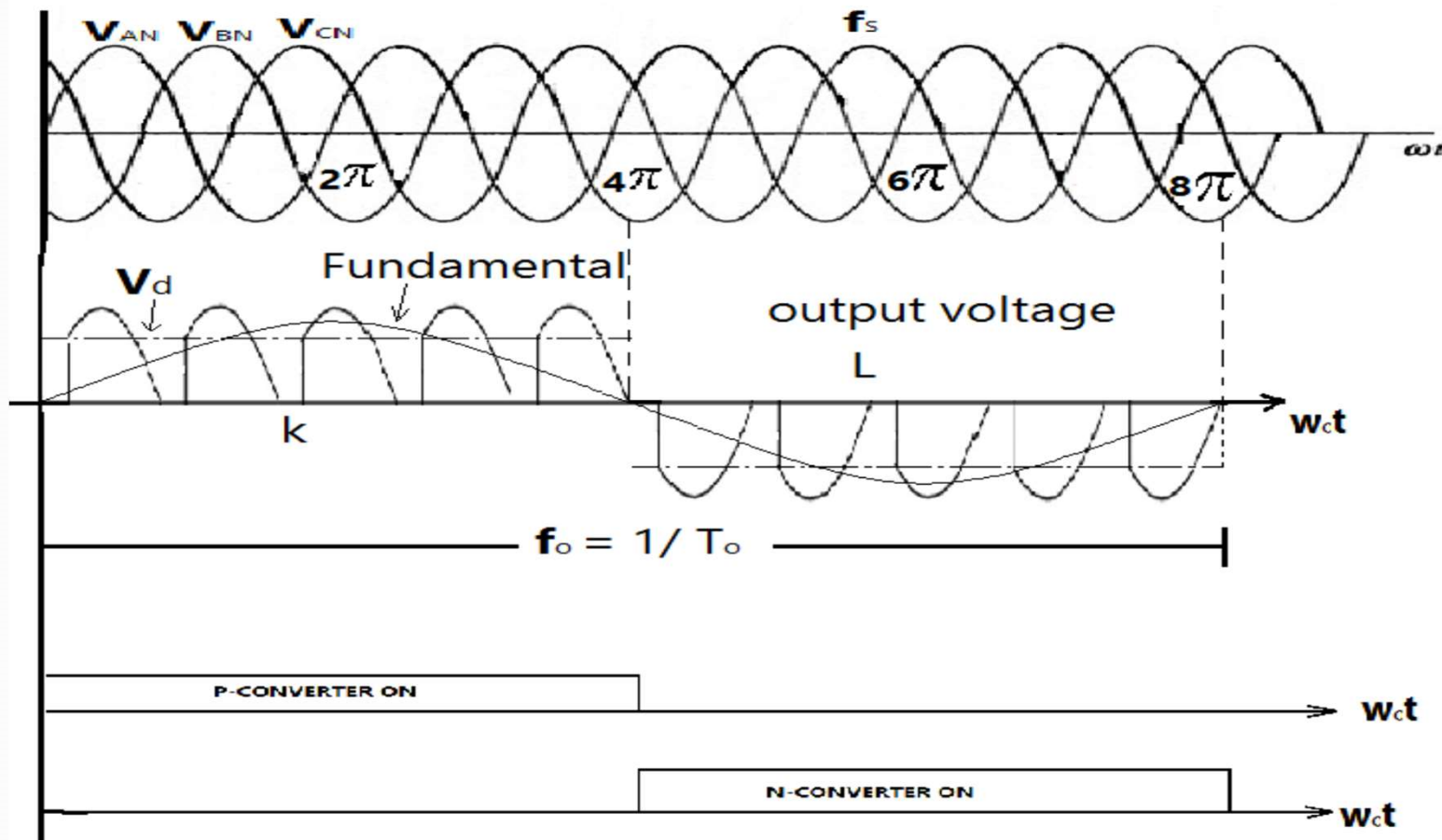

# Three-phase to single-phase cycloconverter



Mr. SARAVANAN D, AP/SEECE, GU

## Contd.....


- For  $\alpha \neq 0$

For the positive group converter:

At point "A" ,  $\alpha = 0$       $V_d = \frac{3\sqrt{3}}{2\pi} V_m = V_{do}$ .


At point "B" ,  $\alpha > 0$       $V_d = V_{do} \cos \alpha$

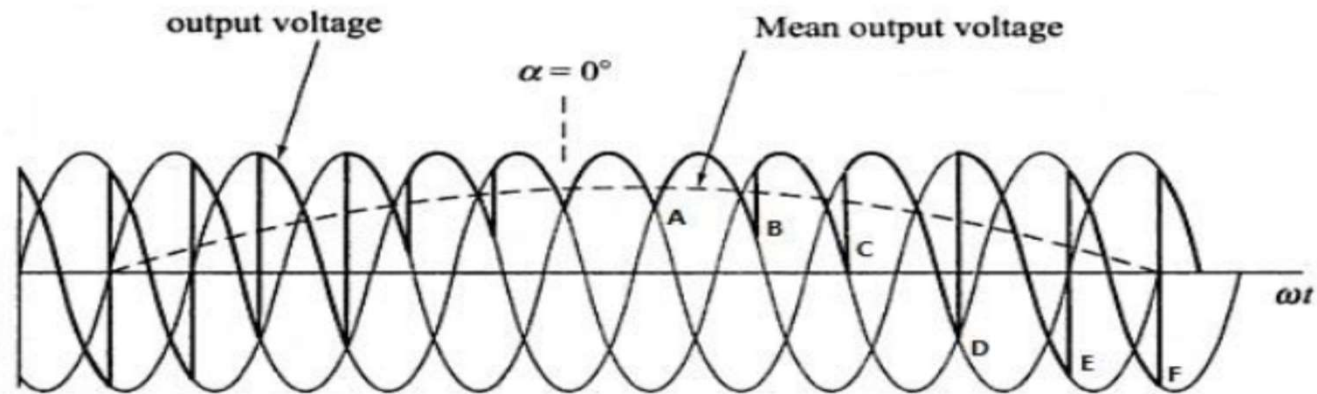At point "F" ,  $\alpha = \frac{\pi}{2}$       $V_d = 0$



Positive group converter operating  
Negative group converter is idling

## Contd.....

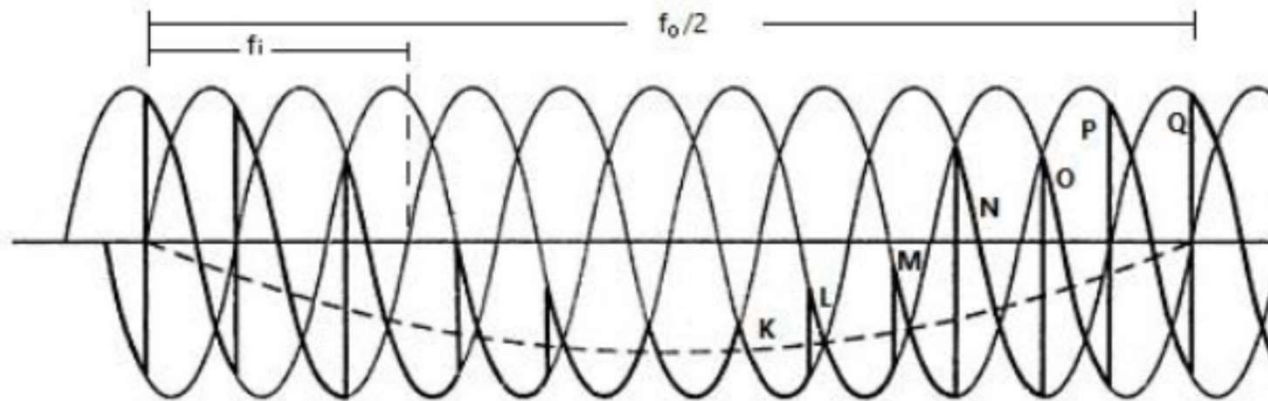

Negative group converter operating

Positive group converter is idling

At point “K” “L” “M” “N” “O” “P” and “Q”


$\alpha > 90^\circ$ ,  $V_d$  is negative [inverting mode]

Change over from positive group converter to negative group converter should be done at points “F” and “Q” where the output of the two converter are zero to avoid short circuit.


Then the condition  $\alpha_p + \alpha_N = \pi$  that should be met.
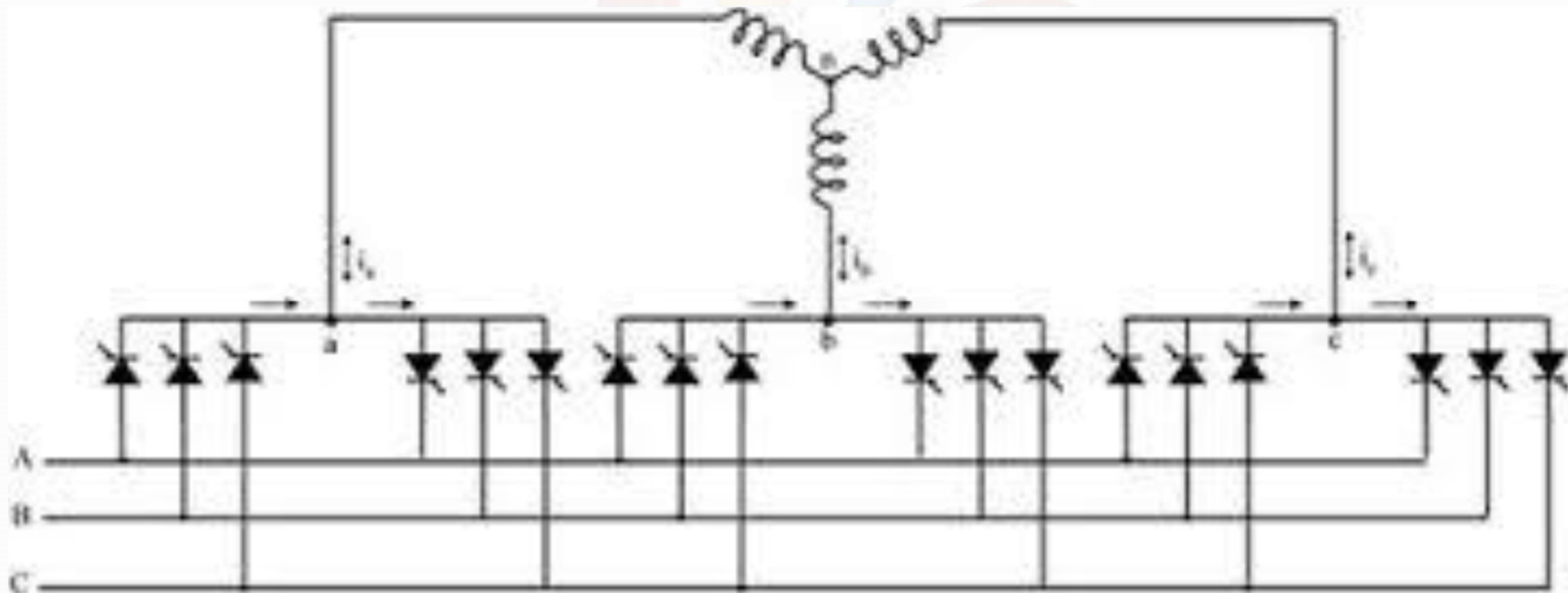
## Three-phase to three-phase cycloconverter

If the output of 3-phase to single-phase converters of the same kind are connected in *Y* or  $\Delta$  and if the output voltages are  $\frac{2\pi}{3}$  radians phase shifted from each other, the resulting converter is a three-phase to three-phase cycloconverter as shown in Fig.5


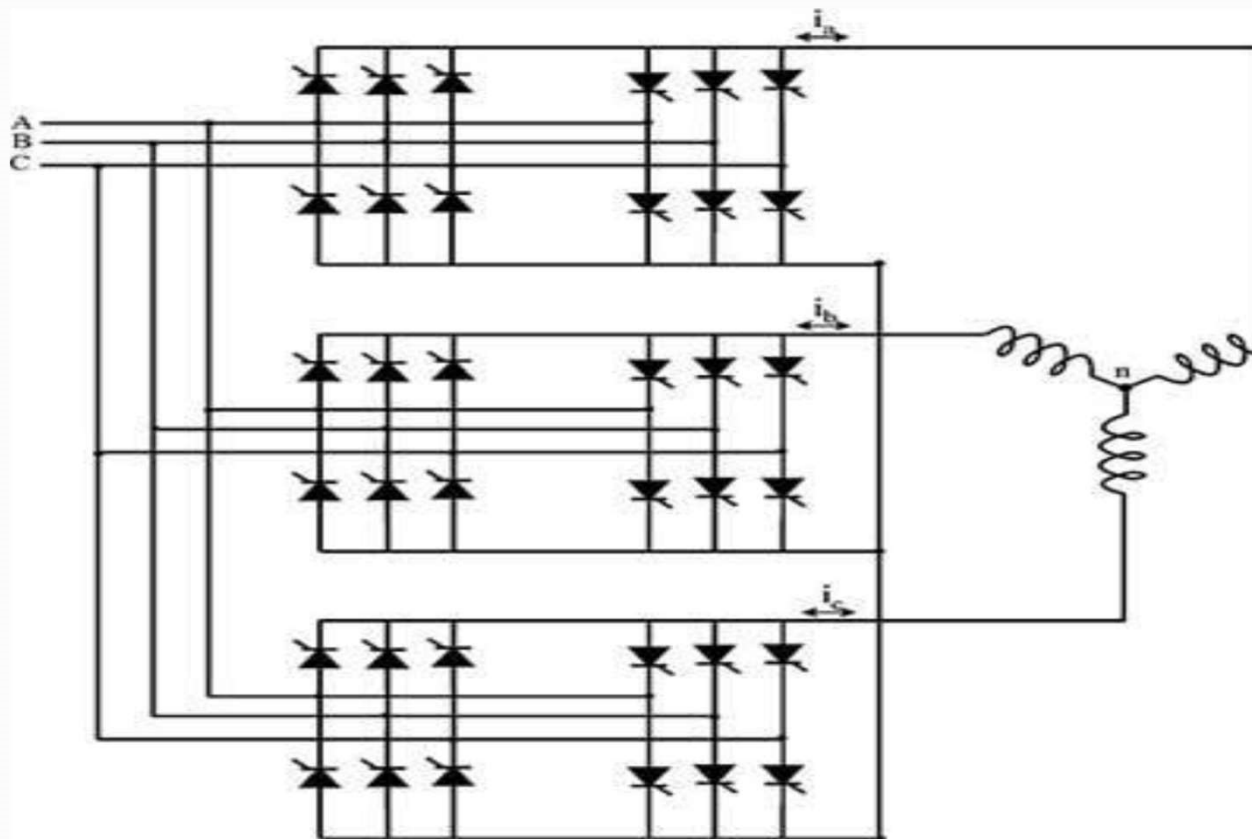
# Three-phase to three-phase cycloconverter



Mr. Saravanan D, AP/SEECE, GU

# Reference

Contents are referred from Open Source

Books:

1. Power electronics by PS Bhimbhar



GALGOTIAS  
UNIVERSITY