

School of Electrical, Electronics and Communication Engineering

Course Code : BTEE3011

Course Name: Power Electronics

The logo of Galgotias University is a circular emblem with a stylized, multi-colored swirl in shades of yellow, orange, and blue. The text "Dual Converter (AC-DC)" is centered over this logo.

Dual Converter (AC-DC)

**GALGOTIAS
UNIVERSITY**

Name of the Faculty: Saravanan D

Program Name: B.Tech-EE/EEE

Introduction


- It is an electronic converter or circuit which comprises of two converter.
- One will perform as rectifier and the other will perform as inverter
- Therefore, we can say that double process will occur at a moment.
- Here, two full converters are arranged in anti-parallel pattern and linked to the same DC load

GALGOTIAS
UNIVERSITY

School of Electrical, Electronics and Communication Engineering

Course Code : BTEE3011

Course Name: Power Electronics

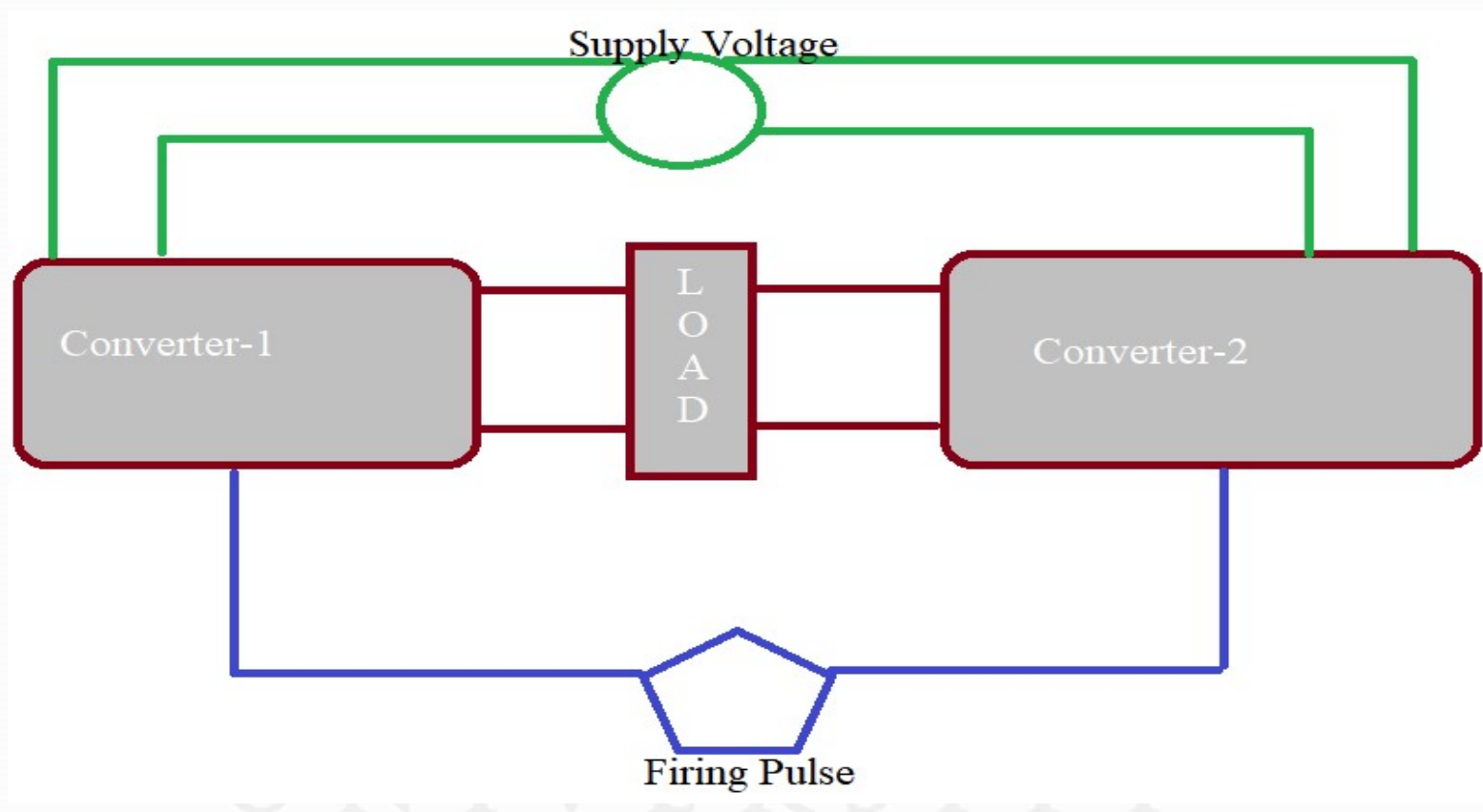

Modes of Operation

There are two functional modes:

1. Non-Circulating Current Mode
2. Circulating Current Mode

GALGOTIAS
UNIVERSITY

Non Circulating Current Mode

- One converter will perform at a time. So there is no circulating current between the converters.
- During the converter 1 operation, firing angle (α_1) will be $0 < \alpha_1 < 90^\circ$; V_{dc} and I_{dc} are positive.
- During the converter 2 operation, firing angle (α_2) will be $0 < \alpha_2 < 90^\circ$; V_{dc} and I_{dc} are negative.


Circulating Current Mode

- Two converters will be in the ON condition at the same time. So circulating current is present.
- The firing angles are adjusted such that firing angle of converter 1 (α_1) + firing angle of converter 2 (α_2) = 180° .
- Converter 1 performs as a controlled rectifier when firing angle be $0 < \alpha_1 < 90^\circ$ and Converter 2 performs as an inverter when the firing angle be $90^\circ < \alpha_2 < 180^\circ$. In this condition, V_{dc} and I_{dc} are positive.
- Converter 1 performs as an inverter when firing angle be $90^\circ < \alpha_1 < 180^\circ$ and Converter 2 performs as a controlled rectifier when the firing angle be $0 < \alpha_2 < 90^\circ$. In this condition, V_{dc} and I_{dc} are negative.

School of Electrical, Electronics and Communication Engineering

Course Code : BTEE3011

Course Name: Power Electronics

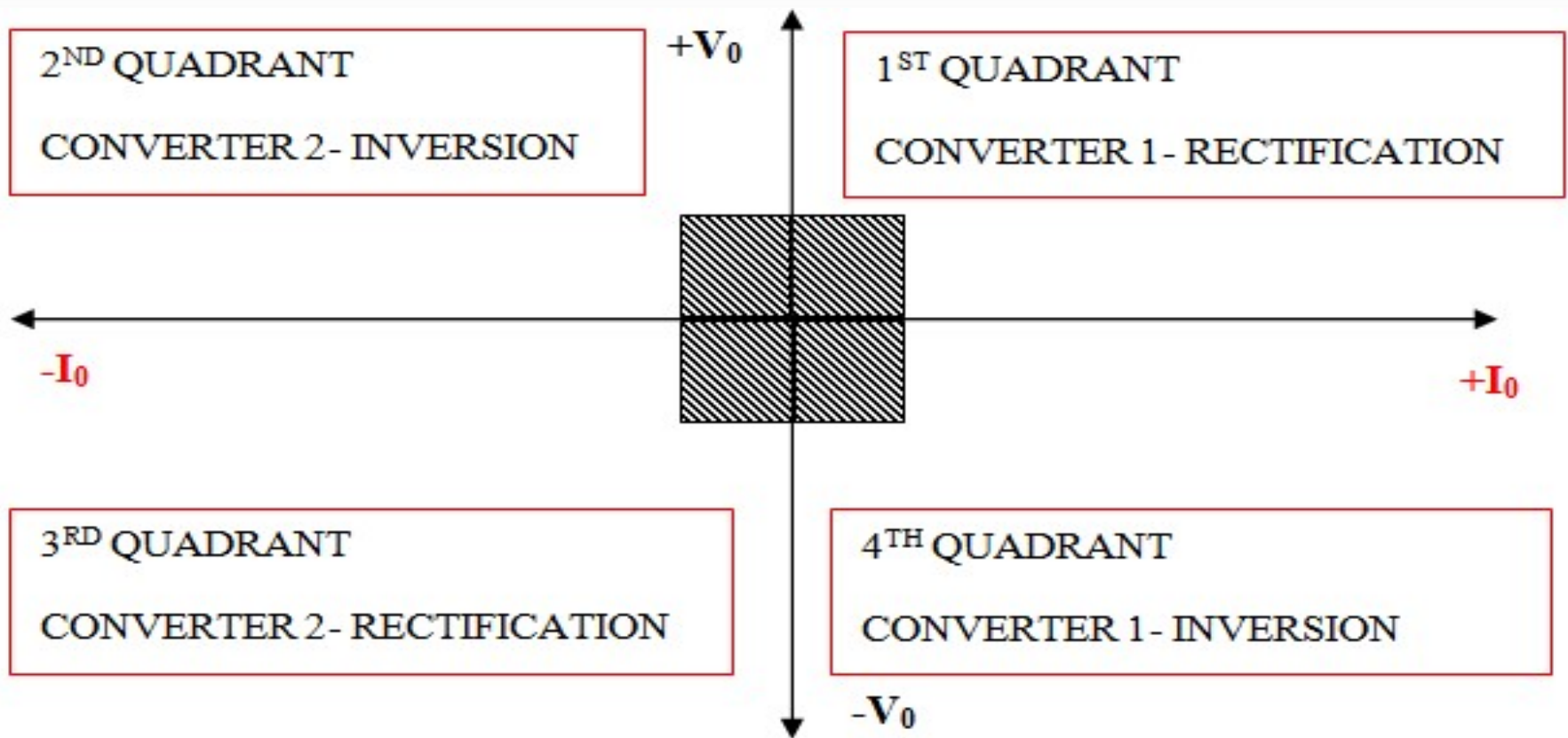


Ideal Dual Converter

- The term 'ideal' refers to the ripple free output voltage. For the purpose of unidirectional flow of DC current, two diodes (D1 and D2) are incorporated between the converters. However, the direction of current can be in any way.
- The average output voltage of the converter 1 is V_{O1} and converter 2 is V_{O2} .
- To make the output voltage of the two converters in same polarity and magnitude, the firing angles of the thyristors have to be controlled.

School of Electrical, Electronics and Communication Engineering

Course Code : BTEE3011

Course Name: Power Electronics

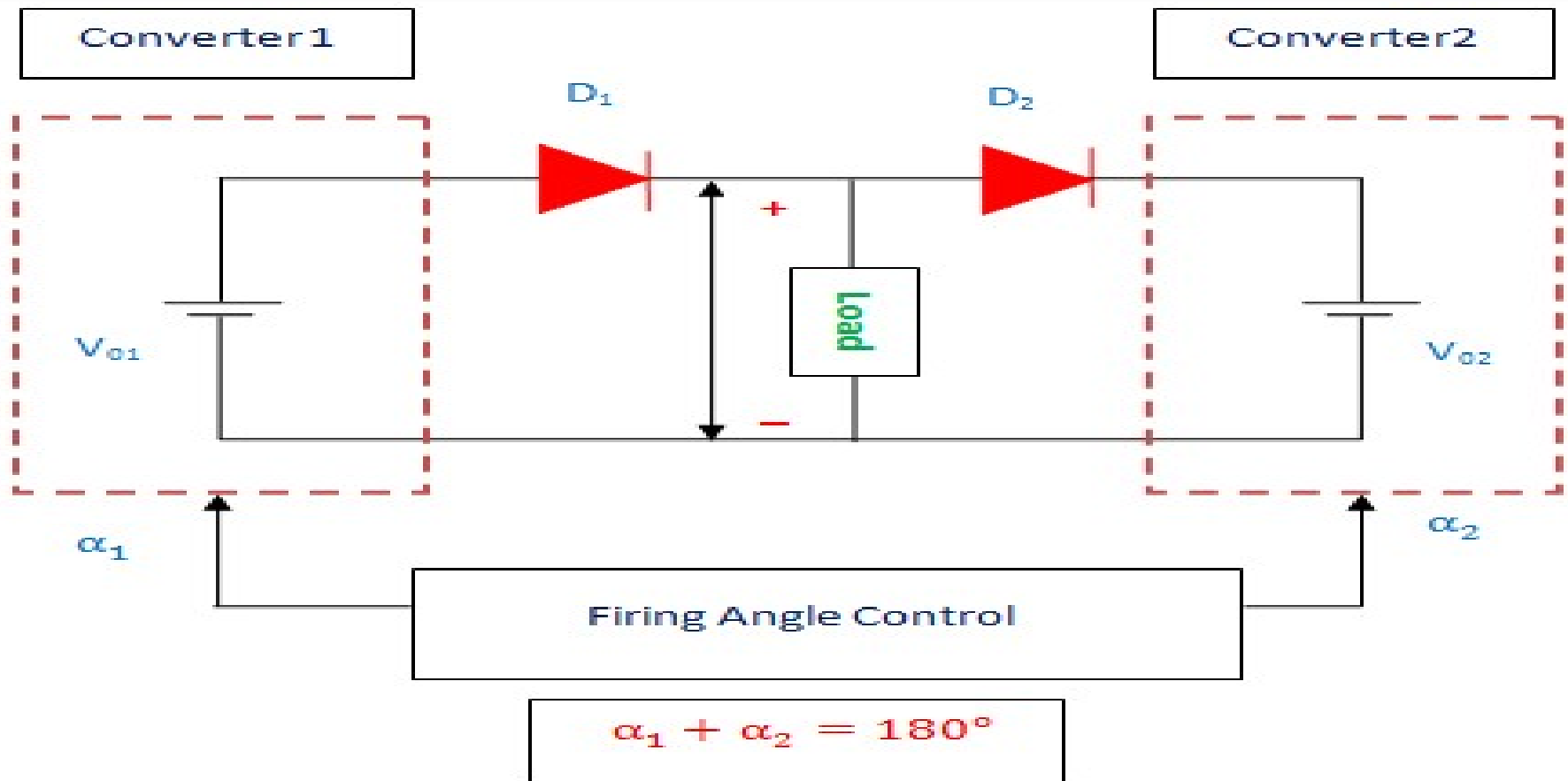

School of Electrical, Electronics and Communication Engineering

Course Code : BTEE3011

Course Name: Power Electronics

$$\text{Average output voltage of Single-phase converter} = \frac{2V_m \cos \alpha}{\pi}$$

$$\text{Average output voltage of Three-phase converter} = \frac{3V_{ml} \cos \alpha}{\pi}$$

For converter 1, the average output voltage,

$$V_{01} = V_{max} \cos \alpha_1$$

For converter 2, the average output voltage,

$$V_{02} = V_{max} \cos \alpha_2$$

GALGOTIAS
UNIVERSITY

School of Electrical, Electronics and Communication Engineering

Course Code : BTEE3011

Course Name: Power Electronics

Output voltage,

$$V_0 = V_{01} = -V_{02}$$

$$V_{max} \cos \alpha_1 = -V_{max} \cos \alpha_2$$

$$\cos \alpha_1 = \cos(180^\circ - \alpha_2) \text{ or } \cos \alpha_2 = \cos(180^\circ + \alpha_2)$$


$$\alpha_1 + \alpha_2 = 180^\circ \text{ And } \alpha_1 - \alpha_2 = 180^\circ$$

The firing angle can never be greater than 180° .


$$\alpha_1 + \alpha_2 = 180^\circ$$

GALGOTIAS
UNIVERSITY

Single phase Dual Converter

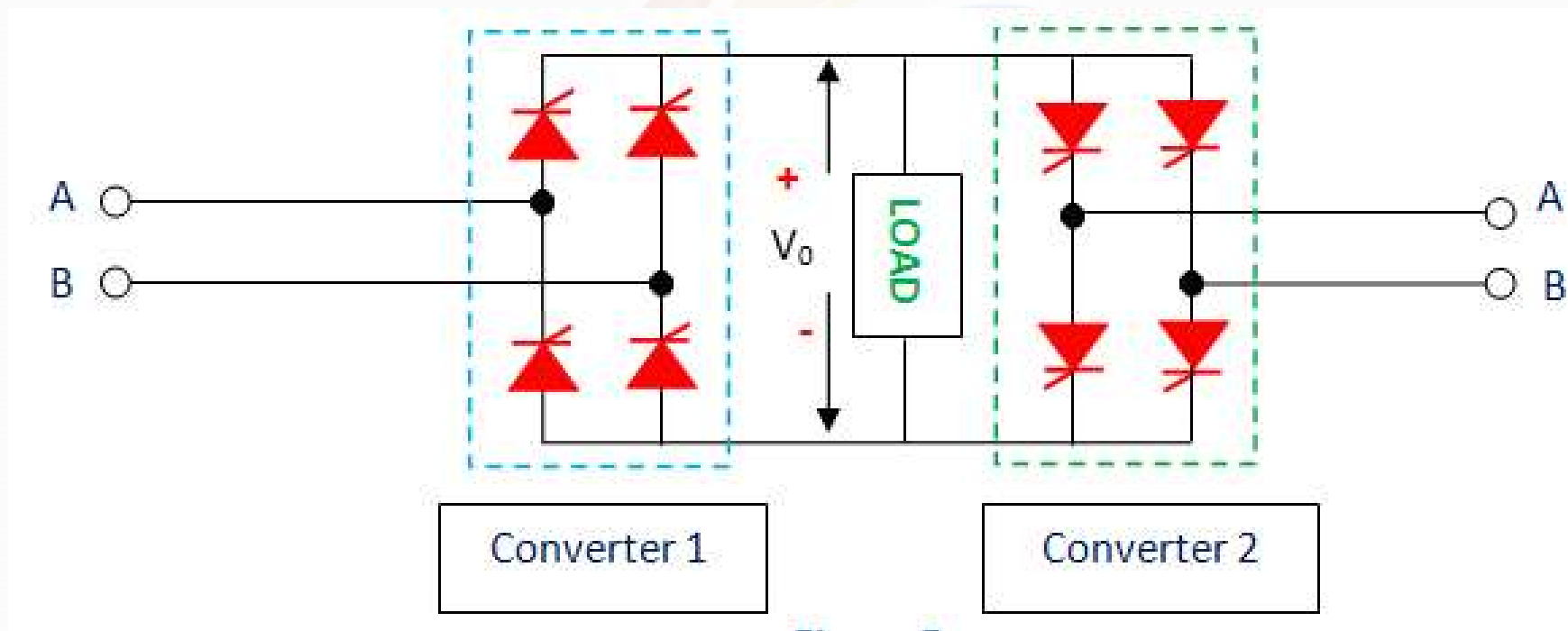

Three Phase Dual Converter

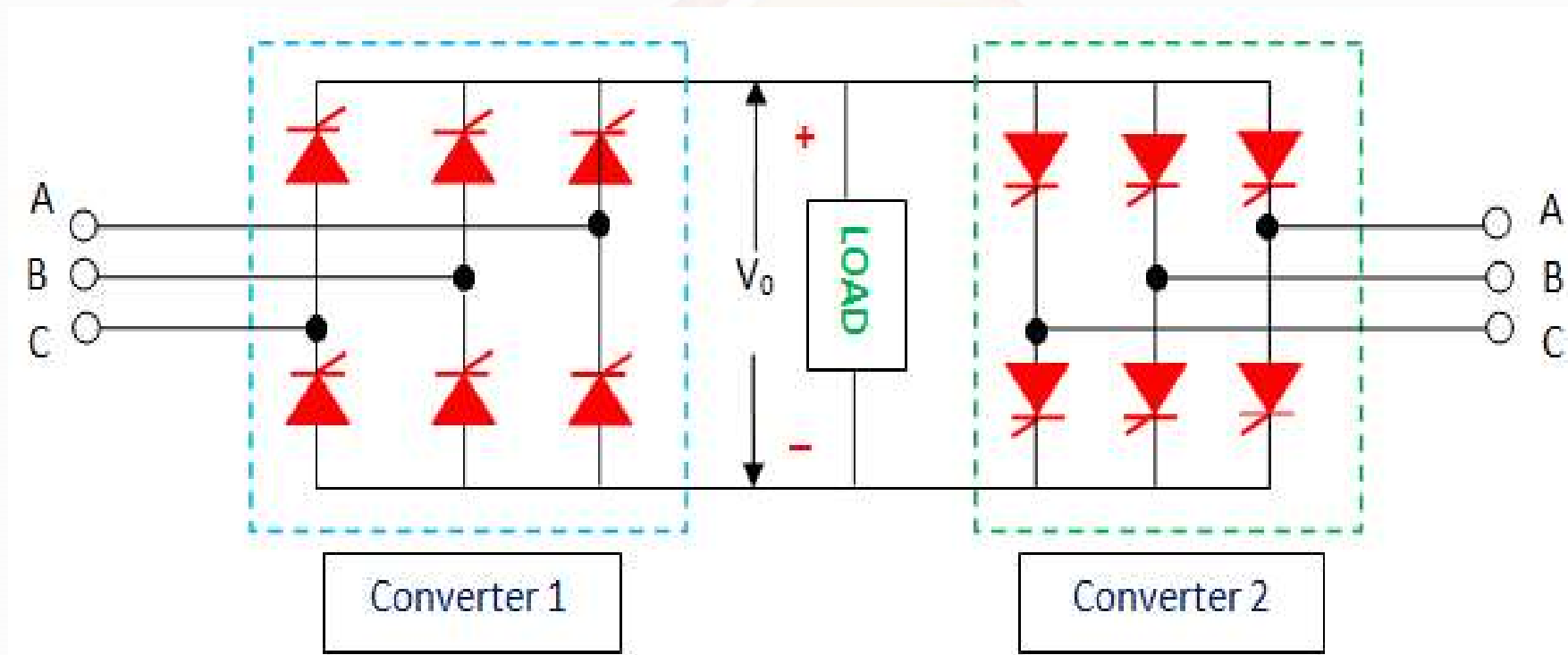

Application of Dual Converter

- Direction and speed control of DC motors.
- Applicable wherever the reversible DC is required.
- Industrial variable speed DC drives.

GALGOTIAS
UNIVERSITY

School of Electrical, Electronics and Communication Engineering

Course Code : BTEE3011

Course Name: Power Electronics

Reference:

All The contents are taken from open Source

GALGOTIAS
UNIVERSITY

Name of the Faculty: Saravanan D

Program Name: B.Tech-EE/EEE